

Transistor is the smallest unit.

↳ Semiconductor device.

dt - 17-09-25.

Number System

1- Decimal - base 10, 0 - 9
10 distinct symbols

$$(45)_{10} = \underbrace{4 \times 10^1}_{\text{weight}} + \underbrace{5 \times 10^0}_{\text{weight}}$$

$$(527)_{10} = 5 \times 10^2 + 2 \times 10^1 + 7 \times 10^0$$

2. Binary number system: 0, 1 (base 2)

0	-0
1	-1
1 0	-2
1 1	-3
1 0 0	-4
1 0 1	-5
1 1 0	-6
1 1 1	-7
1 0 0 0	-8
1 0 0 1	-9

1

1

1

$$\begin{aligned} 2^0 &\rightarrow 1 \\ 2^1 &\rightarrow 2 \\ 2^2 &\rightarrow 4 \\ 2^3 &\rightarrow 8 \end{aligned}$$

Decimal

Binary (4bit)

0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	1000
8	1001
9	1010
10	1011
11	1100
12	1101
13	1110
14	1111
15	

$$\begin{aligned} 2 \text{ bit} &\rightarrow 2^2 = 4 \rightarrow 0 - 3 \\ 3 \text{ bit} &\rightarrow 2^3 = 8 \rightarrow 0 - 7 \\ 4 \text{ bit} &\rightarrow 2^4 = 16 \rightarrow 0 - 15 \\ 5 \text{ bit} &\rightarrow 2^5 = 32 \rightarrow 0 - 31 \end{aligned}$$

8bit \rightarrow 1 byte.

conversion dec to Bi & Binary to decimal.

$$(45)_{10} \rightarrow (101101)_2$$

$$-(97)_{10} \rightarrow (100001)_2$$

$$\begin{array}{r} 100001 \\ 32 16 8 4 2 1 \end{array}$$

$$(97)_{10} \rightarrow (1100001)_2$$

$$(97.25)_{10} = (1100001.01)_2$$

$\begin{array}{r} 0.25 \\ \times 2 \\ \hline 0.5 \end{array}$ $\begin{array}{r} 2^0 \\ | \\ 2^{-1} \\ | \\ 2^{-2} \end{array}$

$\begin{array}{r} \times 2 \\ \hline 1.0 \end{array}$ ↓

$$0 \times 2^{-1} + 1$$

$$(0.32)_{10} = 0.32$$

A hand-drawn binary fraction representation of 0.32. It consists of a horizontal line with a vertical tick mark in the middle. To the left of the tick mark, there is a circled '0'. To the right of the tick mark, there is a circled '1' followed by a circled '0'. Below the line, there is some faint, illegible handwriting.

Octal number system: 0, 1, 2, 3, 4, 5, 6, 7

dt-22-09-25

Base → 8

dec to oct

$$(923)_{10} = (1633)_8$$

$$\begin{array}{r} 8 \longdiv{1923} \\ 8 \longdiv{115} \rightarrow 3 \\ 8 \longdiv{14} \rightarrow 3 \\ 1 \rightarrow 6 \end{array}$$

oct to dec.

$$(1633)_8 =$$

$$= 1 \times 8^3 + 6 \times 8^2 + 3 \times 8^1 + 3 \times 8^0$$

$$= (923)_{10}$$

- decimal to any number system devide by it's base or radix number.
- Any number system to decimal multiply by 10^n weight.

dec to oct

$$(923.25)_{10} =$$

$$\begin{array}{r} 0.25 \\ \times 8 \\ \hline 2.00 \rightarrow 2 \end{array}$$

$$= (1633.2)_8$$

$$\text{Dec to Oct}$$

$$(496.22)_{10} =$$

$\begin{array}{r} 496 \\ \hline 8 62 \end{array}$	$\xrightarrow{0}$	$\begin{array}{r} 7 \end{array}$	$\xrightarrow{6}$
---	-------------------	----------------------------------	-------------------

$\cdot 22$	$\times 8$	$\begin{array}{r} 1.76 \end{array}$	1
------------	------------	-------------------------------------	---

$$\begin{array}{r} \cdot 76 \\ \times 8 \\ \hline 6.08 \end{array} \quad 6$$

$$= (760.160)_8$$

$$\begin{array}{r} \cdot 08 \\ \times 8 \\ \hline 0.64 \end{array} \quad 0$$

$$(3570.45)_8 = \cancel{(51.01)}$$

$$\begin{aligned} &= 3 \times 8^3 + 5 \times 8^2 + \\ &\quad 7 \times 8^1 + 0 \times 8^0 \\ &\quad + 4 \times 8^{-1} + 0 \times 8^{-2} \end{aligned}$$

$$(1912.578)_{10}$$

Octal to Binary :-

$$(1\ 2\ 6)_8 =$$

$$\begin{aligned} &1 \times 8^2 + 2 \times 8^1 + 6 \times 8^0 \\ &= 64 + 16 + 6 \\ &= (86)_{10} \\ &= (1010\ 110)_2 \end{aligned}$$

$$\begin{array}{r} 2 | 86 \\ 2 | 43 - 0 \\ 2 | 21 - 1 \\ 2 | 10 \rightarrow 1 \\ 2 | 5 \rightarrow 0 \\ 2 | 2 \rightarrow 1 \\ 1 \rightarrow 0 \end{array}$$

(ii) Octal \rightarrow Binary directly by representing each octal digit to its corresponding 3 bit binary number.

$$\begin{array}{ccc} (1 & 2 & 6)_8 \\ \downarrow & \downarrow & \downarrow \\ (001 & 010 & 110)_2 \end{array}$$

3 bit - representation.

$$0 \rightarrow 000$$

$$1 \rightarrow 001$$

$$2 \rightarrow 010$$

$$3 \rightarrow 011$$

$$4 \rightarrow 100$$

$$5 \rightarrow 101$$

$$6 \rightarrow 110$$

$$7 \rightarrow 111$$

$$(7 \ 0 \ 3)_8 =$$

$$(111000011)_2$$

$$(405.23)_8$$

$$(100000101.010011)_2$$

Binary \rightarrow octal - directly by representing each 3-bit binary number to its corresponding octal digit.

$$\text{e.g. } (10110101)_2$$

$$= (2 \ 6 \ 5)_8$$

$$(1011101.0101)$$

$$= (135.24)_8$$

$$10101100 \cdot 10101 \\ = (254 \cdot 52)_8$$

HexaDecimal numbers:-

↓	0	0000
↓	1	0001
↓	2	0010
↓	3	0011
↓	4	0100
↓	5	0101
↓	6	0110
↓	7	0111
↓	8	1000
↓	9	1001
↓	10	A 1100
↓	11	B 1011
↓	12	C 1100
↓	13	D 1101
↓	14	E 1110
↓	15	F 1111

- decimal → Hexa

$$(1493)_{10} = (5D5)_{16}$$

$$\begin{array}{r} 16 \mid 1493 \\ \hline 16 \mid 93 \rightarrow 5 \\ \hline 5 \rightarrow 13-D \end{array}$$

$$(5D5)_{16} = (1493)_{10}$$

$$5 \times 16^2 + D \times 16^1 + 5 \times 16^0 \\ = (1493)_{10}$$

$$- (2763.22)_{10} = (A\text{CB}.38)_{16}$$

~~2763~~

$$\begin{array}{r} 16 \mid 2763 \\ 16 \quad | 172 \rightarrow B \\ 16 \quad | 10 \rightarrow C \\ 4 \end{array}$$

0.22

$\times 16$

~~0.32~~

3.52 $\rightarrow 3$

0.52

$\times 16$

$\frac{8.32}{8.32} \rightarrow 8$

Hexa \rightarrow Decimal.

$$- (1A2.(3))_{16} =$$

$$(418.761)_{10}$$

$$(1A2.1B)_{16} = 1 \times 16^2 + 10 \times 16^1 + 2 \times$$

Hexa \rightarrow Binary -

$$(A2)_{16} = (10100010)_2$$

$$A \times 16^1 + 2 \times 16^0$$

$$= (160 + 2)_{10} = (162)_{10}$$

$$\begin{array}{r} 2 \mid 162 \\ 2 \quad | 81 \quad 0 \\ 2 \quad | 40 \quad 1 \\ 2 \quad | 20 \quad 0 \\ 2 \quad | 10 \quad 0 \\ 2 \quad | 5 \quad 0 \\ 2 \quad | 2 \quad 1 \end{array}$$

Hexa \rightarrow Binary \rightarrow directly
Representing each hexa digit to its 4 bit binary number.

$$\begin{array}{c} A \ 2 \\ \downarrow \\ (1010 \ 0010)_2 \end{array}$$

$$\begin{aligned} (.10B.2C)_{16} &= \\ &= (100001011.00101100)_2 \end{aligned}$$

- Binary \rightarrow hexa \rightarrow directly by representing each 4 bit binary number to hexa digit.

$$\begin{array}{c} 101011001.11101 \\ 0(159.E8)_{16} \end{array}$$

$$(1011010.01011)_2$$

$$(5A.58)_{16}$$

Hexa \rightarrow octal

(1) Hexa \rightarrow decimal \rightarrow octal.

(2) Hexa \rightarrow Binary \rightarrow octal.

$$(1934.12)_{16} =$$

$$(1100100111010.00010010)_2$$

$$(14472.044)_8$$

$$(AF.0B)_{16} =$$

$$= (101011110.00001011)_2$$

$$\underline{(537 \cdot 026)_8}$$

$$(257.026)_8$$

Octal \rightarrow Hexa

(1) Octal \rightarrow decimal \rightarrow hexa

(2) Octal \rightarrow binary \rightarrow hexa

$$(127.15)_8 =$$

$$= (001010111.001101)_2$$

$$= (57.34)_{16}$$

$$(5432.75)_8 =$$

$$(101100011010.111101)_2$$

$$(432.75)_{16}$$

$$(B1A.F4)_{16}$$

Ex. $\frac{40}{3} = 13$ if it is correct then find the base.
→ Let the base is 'b'

$$\rightarrow \frac{4 \times b^1 + 0 \times b^0}{3 \times b^0} = 1 \times b^1 + 3 \times b^0$$

$$\Rightarrow \frac{4b + 0}{3} = b + 3$$

$$\Rightarrow 4b = 3b + 9$$

$$\Rightarrow \boxed{b = 9}$$

$$12 + 21 = 33$$

- Let the base is 'b'

$$1 \times b^1 + 2 \times b^0 + 2 \times b^1 + 1 \times b^0 = 3 \times b^1 + 3 \times b^0$$

$$\Rightarrow b + 2 + 2b + 1 = 3b + 3$$

$$\Rightarrow 3b + 3 = 3b + 3$$

∴ valid for any value of b.

→ b can be greater than 4 ↴

$$\boxed{\underline{\underline{b \geq 4}}}.$$

Binary Addition

dt-24-09-28

$$\begin{array}{r}
 1101 \\
 1111 \\
 \hline
 \overline{11100}
 \end{array}$$

$$\begin{aligned}
 0+1 &= 1 \\
 1+0 &= 1 \\
 0+0 &= 0 \\
 1+1 &= 10
 \end{aligned}$$

$$\begin{array}{r}
 1011 \\
 1001 \\
 \hline
 \overline{10000} \\
 10100
 \end{array}$$

$$\begin{array}{r}
 1001 \\
 -011 \\
 \hline
 0110
 \end{array}$$

Representation of -ve numbers.

(1) Signed magnitude representation.

→ In this representation an extra bit is added at the MSB to represent sign.

0 → +ve
1 → -ve

ex ~~sign~~ $\frac{0 \ 101}{\text{magnitude}} = +5$

$\frac{1 \ 101}{\text{magnitude}} = -5$

* (1) 111 → -7

. 1001 = -1

② complement system

2's complement representation.

→ In 2's complement representation change all 0's to 1's and all 1's to 0's.

$$- \quad 110010$$

$$1's - 001101$$

→ 1 is added to it's 1's complement to get 2's complement.

$$\begin{array}{r} \text{exm.} & 0110 \\ \text{1's} & 1001 \\ +1 & \\ \hline \text{2's comp} & 1010 \end{array}$$

$$\begin{array}{r} 0000 & 0110 \\ 1's & 1111 \\ +1 & \\ \hline 2's & 11111110 \end{array}$$

$$\begin{array}{r} 6 \\ -3 \\ \hline 3 \end{array}$$

$$\begin{array}{r} 6 \\ +(-3) \\ \hline \end{array}$$

$$\begin{array}{r} +3 \rightarrow 0011 \\ 1's \rightarrow 1100 \\ +1 \\ \hline \end{array}$$

$$\begin{array}{r} \text{2's comp: } 1101 \end{array}$$

$$6 \rightarrow 0110$$

$$+1101$$

$$\overline{1} \overline{0} \overline{0} \overline{1} \overline{0}$$

Carry.

$$\begin{array}{r} 3 \\ -6 \\ \hline \end{array} \quad \begin{array}{r} 011 \\ +010 \\ \hline 101 \end{array}$$

$$\begin{array}{r} +6 \rightarrow 110 \\ 001 \\ +1 \\ \hline 010 \end{array}$$

$$\begin{array}{r}
 3 = 3 \rightarrow 0011 \\
 -6 = -(-6) \rightarrow +1010 \\
 \hline
 1101
 \end{array}$$

$$\begin{array}{r}
 +6 \rightarrow 0110 \\
 1's \rightarrow 1001 \\
 +1 \\
 \hline
 2's \rightarrow 1010
 \end{array}$$

→ If there is no carry then no result
 is negative and is in 2's complement.

- If there is carry then neglect the carry & remaining is the result.

$$\begin{array}{c|c}
 \begin{array}{r}
 5 - 3 \\
 \hline
 0101 \\
 +1101 \\
 \hline
 \text{carry } \underline{\underline{1}} \\
 10010
 \end{array} &
 \begin{array}{r}
 3 - 5 \quad \text{in 2's comp. method} \\
 \hline
 0011 \\
 +1011 \\
 \hline
 1110
 \end{array} \\
 \end{array}$$

result But in -ve
 & 2's complement.

$$\begin{array}{r}
 0010 \\
 1100 \\
 +1 \\
 \hline
 1101
 \end{array}$$

$$\begin{array}{r}
 0101 \\
 1010 \\
 +1 \\
 \hline
 1011
 \end{array}$$

LOGIC GATES:

dt - 26-09-25


Basic gate:- AND gate :- The O/P is '1' when all the inputs are '1'. otherwise the O/P is '0'.

0 - False
1 - True

Truth Table :

I/P		$y = A \cdot B$ (O/P)
A	B	
0	0	0
0	1	0
1	0	0
1	1	1

Symbol :

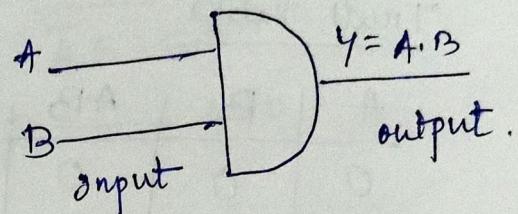


OR GATE - The O/P is '1' when any one input is '1'. The O/P is '0' when all the inputs are '0'.

Truth Table :

I/P		$y = A + B$
A	B	
0	0	0
0	1	1
1	0	1
1	1	1

Symbol :

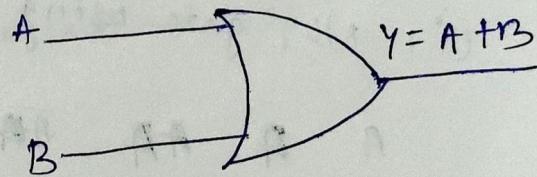


NOT GATE :

Truth Table :

A	\overline{A} or A'
0	1
1	0

\overline{A} or A' \rightarrow A bar over A or A complement.

Symbol :

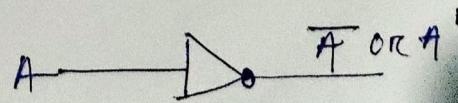

Universal Gate :-


→ NAND and NOR are known as universal gates.
 why? All the gates can be designed by using
 NAND or NOR gates only.

1. NAND gate (AND → complement → NAND)

Truth Table

A	B	AB	\overline{AB}
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

Symbol :-

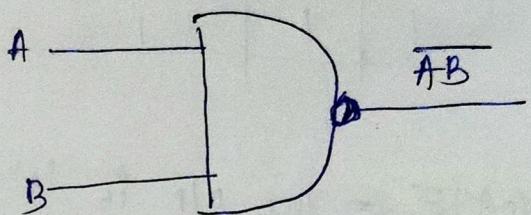


2. ~~NOR gate~~

(i) NOT gate using NAND.


$$A \# AB \quad \overline{A} \#$$

Symbol :-


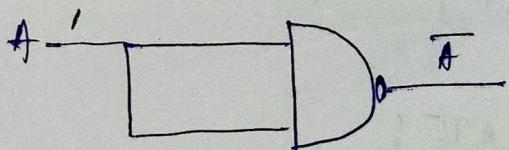


AND gate using NAND.

$$A \# B \# AB'$$

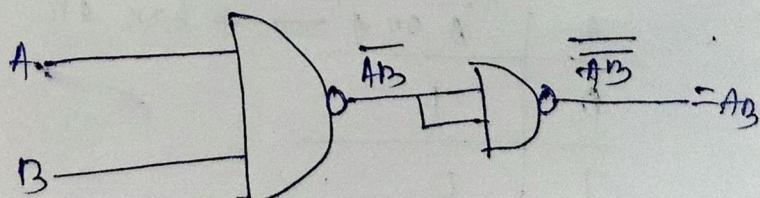

OR gate using NAND

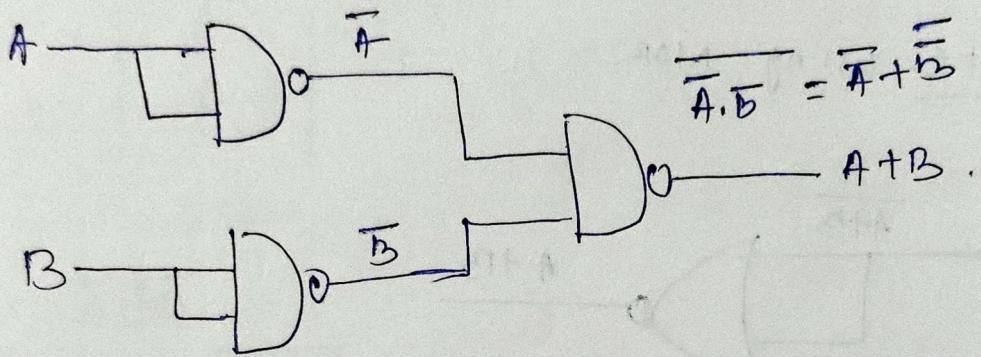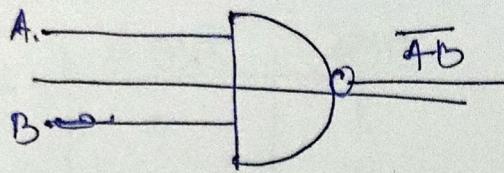

Demorgan's Law

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$


$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

NOR gate : - OR \rightarrow complement \rightarrow NOR.


Truth Table.

A	B	$A+B$	$\overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0


Symbol,

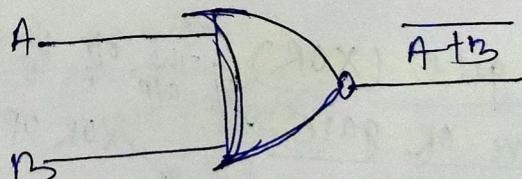


NOT gate using NOR

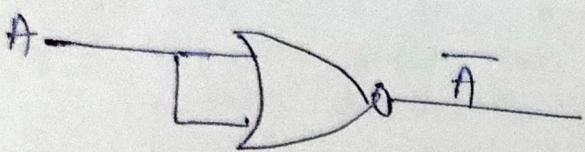

OR gate using NOR

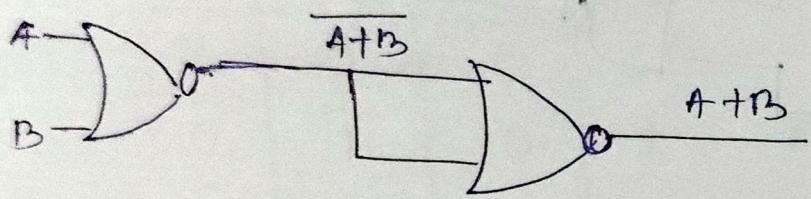


AND gate using NOR.

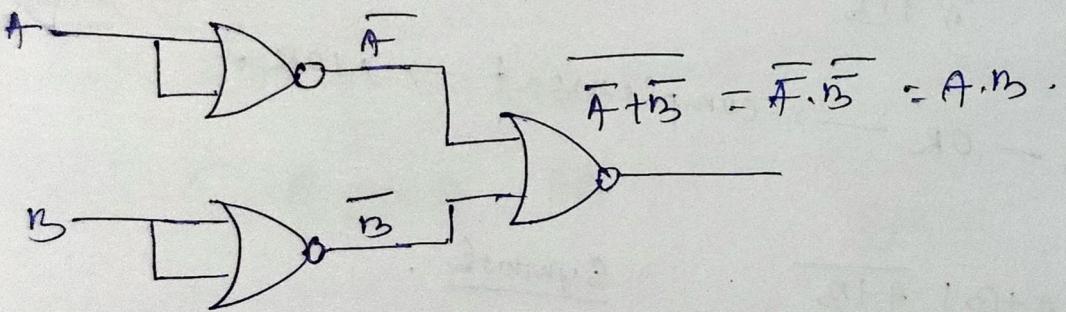

EXOR gate (XOR) ; The op is '1' when inputs are different, the op is '0' when inputs are same.
Exclusive OR gate . XOR operation

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

Symbol:

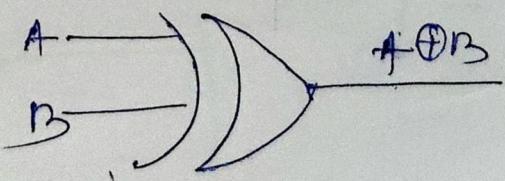

ExNOR \rightarrow XNOR

A	B	$A \oplus B$	$A \otimes B$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

$$A \otimes B = \overline{A \oplus B}$$

$$A \oplus B = \overline{A}B + A\overline{B}$$

$$A \otimes B = AB + \overline{A}\overline{B}$$

Boolean Algebra:

In boolean algebra the variables do not have any numerical significance.

- It has only logical values.

Ex $A + A = A$ ($0+0=0/1+1=1$)
 $A \cdot A = A$ ($0 \cdot 0=0/1 \cdot 1=1$)

Laws in Boolean Algebra (and axioms)

AND LAWS

- (i) $A \cdot 0 = 0$
- (ii) $A \cdot 1 = A$
- (iii) $A \cdot A = A$
- (iv) $A \cdot \overline{A} = 0$

OR LAWS

$$\boxed{\begin{aligned} A + 0 &= A \\ A + 1 &= 1 \\ A + \overline{A} &= 1 \\ A + A &= A \end{aligned}}$$

NOT LAWS

$$\begin{aligned} \overline{1} &= 0 \\ \overline{0} &= 1 \\ \overline{\overline{A}} &= A \end{aligned}$$

Imp

Denyorgan's Laws

$$\begin{aligned} (\overline{A+B}) &= \overline{A} \cdot \overline{B} \\ (\overline{A \cdot B}) &= \overline{A} + \overline{B} \end{aligned}$$

Ex $\overline{A \oplus B}$

$$\begin{aligned} &= \overline{\overline{AB} + A \cdot \overline{B}} \\ &= \overline{AB} \cdot \overline{A \cdot \overline{B}} \\ &= \end{aligned}$$

Ex $\overline{A \oplus B}$

$$\begin{aligned} &= \overline{\frac{\overline{A}B + A\overline{B}}{2}} \\ &= \overline{\overline{A}B} \cdot \overline{A\overline{B}} \\ &= (\overline{\overline{A}+B})(\overline{\overline{A}+\overline{B}}) \\ &= (A+B)(\overline{A}+\overline{B}) \\ &= 0 + AB + \overline{A}\overline{B} + 0 \end{aligned}$$

$$\overline{A \oplus B} = AB + \overline{A}\overline{B}$$

$$\Rightarrow \text{AOR} = AB + \overline{A}\overline{B}$$

$$\text{Eq} \quad AB + BC + A\bar{B}C \rightarrow \text{minimize}$$

Minimization

{ Minimum number of terms with minimum number of variables }


dt - 07/10/25

Digital Mantra

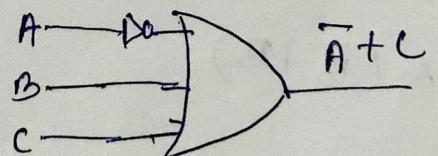
- (1) LSI \rightarrow Low power
 \rightarrow Less space
 \rightarrow Low cost

dt - 08/10/25



$$\begin{aligned}
 Q) & AB + \bar{A} + A\bar{B}C \\
 &= AB + A\bar{B}C + \bar{A} \\
 &= A(C + \bar{B}) + \bar{A} \\
 &= AC + \bar{A} \\
 &= A(\bar{C} + C) \\
 &= (\bar{A} + A) \cdot (\bar{C} + C) \\
 &= 1 \cdot (\bar{A} + C) \\
 &= \bar{A} + C
 \end{aligned}$$



$$ABC + \bar{A} + A\bar{B}C$$

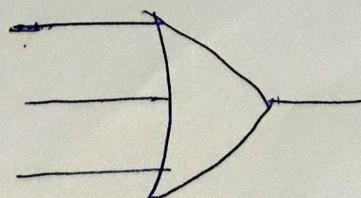

$$ABC + \overline{A} + \overline{B}C$$

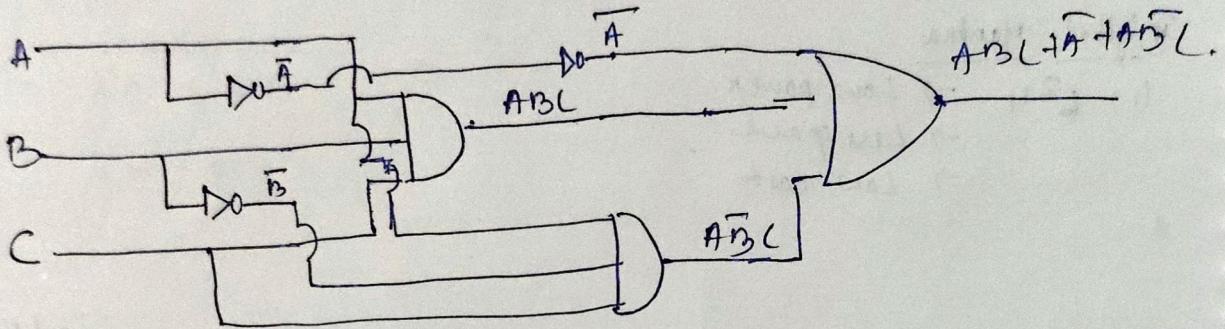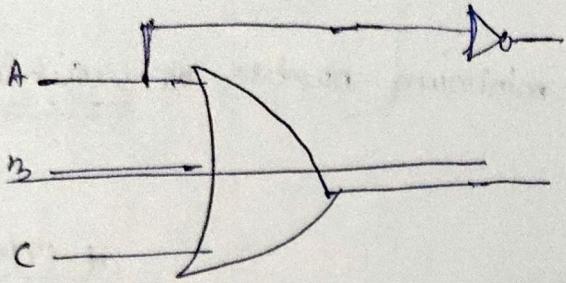

$$\overline{AB} + (\overline{A} + \overline{B} + C \cdot \overline{C})$$

$$\Rightarrow \overline{AB} + \overline{\overline{A} + \overline{B} + 0}$$

$$\Rightarrow \overline{AB} + (\overline{\overline{A}} + \overline{\overline{B}})$$

$$\Rightarrow \overline{AB} + \overline{A} \cdot \overline{B}$$

$$\Rightarrow A\overline{B} + A\overline{B}$$

$$= \cancel{A} \cancel{B} + A(\overline{B} + B)$$

$$= A \cdot 1$$

$$= A.$$

Truth table

A	B	C	\bar{A}	\bar{B}	\bar{C}	$C \cdot \bar{C}$	$A \cdot \bar{B}$
T	T	T	F	F	T	F	F
T	T	F	F	T	F	F	T
T	F	T	F	F	T	F	F
F	T	F	T	T	F	F	F
F	F	F	T	F	T	F	T

Truth table

A	B	C	\bar{A}	\bar{B}
0	0	0	1	1
0	0	1	1	0
0	1	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	0	0

A	B	C	\bar{A}	\bar{B}	\bar{C}	$A \cdot \bar{B}$	$C \cdot \bar{C}$	$\bar{A} + \bar{B}$	$\bar{A} + \bar{B} + C \cdot \bar{C}$
0	0	0	1	1	1	0	0	1	1
0	0	1	1	1	0	0	0	1	1
0	1	0	1	0	1	0	0	1	1
0	1	1	1	0	0	0	0	1	1
1	0	0	0	1	1	1	0	1	1
1	0	1	0	1	0	1	0	0	0
1	1	0	0	0	1	0	0	0	0
1	1	1	0	0	0	0	0	0	0

$\bar{A} + \bar{B} + C \cdot \bar{C}$

$A \bar{B} + (\bar{A} + \bar{B} + C \cdot \bar{C})$

0
0
0
0
0
0
1
1
1

$$Q. A(A + \bar{B}C) + A(\bar{B} + C)$$

$$= A \cdot A + A\bar{B}C + A\bar{B} + AC$$

$$= A + A\bar{B}C + A\bar{B} + AC$$

$$= A(1 + \bar{B}C + \bar{B} + C)$$

$$= A \cdot 1$$

$$= A$$

$$\begin{aligned}
 Q) & A(C+D'B) + A' \\
 &= AC + A'D'B + A' \\
 &= AC + A' + AD'B \\
 &= (A+A')(C+A') + AD'B \\
 &= C + A' + \cancel{AD'}B \\
 &= C + (A'+A)(A'+D'B) \\
 &= C + A' + D'B
 \end{aligned}$$

dt-10-10-25

SOP → Sum of Product

- When more than one product terms are sum together then it is known as SOP.

Ex. $\overline{ABC} + \overline{ABC} + \overline{ABC} \rightarrow \underline{\underline{\text{SOP}}}$.

- In case of SOP an overbar (-) can't extend to more than one variable.
 \overline{ABC} (not included in SOP).
 \overline{ABC} (SOP).

Standard SOP & Canonical SOP :-

If in SOP expression all the variables is present in each term (Either complemented or non complemented) then it is known as standard SOP.

$$\rightarrow Y_1 = A\overline{B}\overline{C} + A\overline{B}\overline{C} + \overline{A}\overline{B}C \rightarrow \text{standard SOP}.$$

$$\rightarrow Y_2 = AB + AB\overline{C} + \overline{B}\overline{C} \rightarrow \text{non standard SOP}.$$

Ex. $AB + A\overline{B}\overline{C} + \overline{B}\overline{C} \rightarrow$ convert to standard SOP.

$$= AB(C+\overline{C}) + A\overline{B}\overline{C} + (A+\overline{A})\overline{B}\overline{C}$$

$$= ABC + A\overline{B}\overline{C} + A\overline{B}\overline{C} + A\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C} (A\overline{B}\overline{C} + A\overline{B}\overline{C}) = A\overline{B}\overline{C}$$

$$= A\overline{B}\overline{C} + A\overline{B}\overline{C} + A\overline{B}\overline{C} + A\overline{B}\overline{C}$$

Standard SOP.

A non standard SOP can be converted to standard SOP by multiplying missing variable plus its complement and rearranging it [more than one same term can be taken as one term]

$$\underline{\text{ex. }} \underline{AB\bar{C} + A\bar{B}\bar{C}} \\ = \underline{\underline{A\bar{B}\bar{C}}}.$$

$$\underline{\text{Ex. }} \underline{A + BC}$$

$$= A(B + \bar{B}) \cdot (C + \bar{C}) + (A + \bar{A})BC \\ = ABC + A\bar{B}\bar{C} + A\bar{B}C + \bar{A}BC \\ = ABC + A\bar{B}\bar{C} + \bar{A}BC.$$

~~$$= AB + A\bar{B} (C + \bar{C}) + (A + \bar{A})BC.$$~~

~~$$= ABC + A\bar{B}\bar{C} +$$~~

~~$$= \underline{A + BC ->}$$~~

$$= A(B + \bar{B}) (C + \bar{C}) + (A + \bar{A})BC$$

~~$$= ABC + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C + \bar{A}BC.$$~~

~~$$= ABC + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + \bar{A}BC$$~~

$$\underline{\text{Ex. }} \underline{A\bar{B}\bar{C} + AB\bar{C}\bar{D} + A\bar{B}\bar{D}}$$

$$= A\bar{B}\bar{C}(D + \bar{D}) + AB\bar{C}\bar{D} + A\bar{B}(C + \bar{C})\bar{D}$$

$$= A\bar{B}\bar{C}D + \underline{A\bar{B}\bar{C}\bar{D}} + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D} + \underline{A\bar{B}C\bar{D}}$$

$$= A\bar{B}\bar{C}D + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D} + A\bar{B}CD$$

$\therefore \underline{\underline{\text{SSOP}}}$

Ex. $A + BCD$.

$$A(B+\bar{B})(C+\bar{C})(D+\bar{D}) + (A+\bar{A})BCD$$

$$\cancel{ABC} + A\bar{B}(\cancel{C+C}) + \cancel{ABC} + \cancel{A\bar{B}\bar{C}} + A$$

$$\cancel{ABC} + A\bar{B}\bar{C} + \cancel{A}$$

$$\cancel{ABC} + A$$

$$= \{ABC + A\bar{B}\bar{C} + A\bar{B}C + \cancel{A\bar{B}\bar{C}}\} (D+\bar{D}) + \cancel{ABC}D + \cancel{\bar{ABC}D}$$

$$= \frac{ABC\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + A\bar{B}\bar{C}\bar{D} + A\bar{B}CD + A\bar{B}\bar{C}D}{x} + \cancel{ABC}D + \cancel{\bar{ABC}D}$$

$$= \text{SOP}.$$

Binary value assignment

In a standard SOP each variable is taken as '1' and variable complement is taken as '0'.

$$+ \rightarrow 1$$

$$\bar{+} \rightarrow 0$$

Ex. $\bar{A}BC + A\bar{B}\bar{C} + ABC \rightarrow$ Assign binary values to it.

Assign binary values:

$$- A + BC$$

$$\Rightarrow A(B+\bar{B})(C+\bar{C}) + (A+\bar{A})BC$$

$$\Rightarrow \cancel{ABC} + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + \cancel{ABC} + \cancel{A\bar{B}C}$$

$$\Rightarrow \cancel{ABC} + \cancel{A\bar{B}\bar{C}} + \cancel{A\bar{B}C} + \cancel{A\bar{B}\bar{C}}$$

$$\rightarrow AB + A\bar{B}C + \bar{A}\bar{C}$$

→

$$\begin{matrix} A & B & C \\ 1 & 1 & 0 \end{matrix}$$

$$A\bar{B}C$$

$$1 \ 0 \ 1$$

$$1 \ 1 \ 1$$

$$\begin{matrix} A & B & \bar{C} \\ 1 & 1 & 0 \end{matrix}$$

$$1 \ 0 \ 0$$

$$0 \ 1 \ 0$$

$$0 \ 0 \ 0$$

$$ABC + A\bar{B}C + A\bar{B}C + A\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}BC + \bar{A}B\bar{C}$$

$$= ABC + A\bar{B}C + A\bar{B}C + A\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}BC + \bar{A}B\bar{C}$$

dt-13-10-25

SOP.

$$F_1 = ABC + A\bar{B}C + A\bar{B}\bar{C}$$

$$111 \quad 101 \quad 110$$

- Minterm: Each term in a standard SOP is called a minterm.
- It is represented by 'm' with subscript decimal numbers.

$$F_1 = ABC + A\bar{B}C + A\bar{B}\bar{C}$$

$$\text{Binary} = 111 \quad 110 \quad 100$$

$$\text{Decimal} = 7 \quad 6 \quad 4$$

$$\text{Minterm} \quad m_7 \quad m_6 \quad m_4$$


Eg $A\bar{B} + \bar{A}\bar{B} + AB$ → Represent in sum of minterms.

$$= A\bar{B} + \bar{A}\bar{B} + AB$$

Binary = 10 00 11

Dec = 2 0 3

minterm = m_2 m_0 m_3

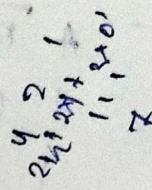

$$F_2 = \sum_m (0, 2, 3)$$

sum of minterms

$F_3 = A\bar{B} + BC + AB\bar{C}$ → represent in Σm .

~~$= \bar{B}C\bar{A} + \bar{A}\bar{B}C + A\bar{B}\bar{C}$~~

1	0	1	0
0	1	0	0
1	0	1	0
0	1	0	0

$$= A\bar{B} C \quad A\bar{A}BC \quad AB\bar{C}$$

$$\quad \quad \quad 1 \quad 0 \quad 0 \quad 0 \quad 1 \quad 1 \quad 0 \quad 0$$

$$= A\bar{B}C + \bar{A}BC + A\bar{B}\bar{C}$$

$$\begin{array}{r} 1 \ 0 \ 1 \rightarrow 5 \\ 1 \ 0 \ 0 \rightarrow 4 \\ \quad \quad \quad 0 \end{array} \quad \begin{array}{r} 1 \ 1 \ 1 \rightarrow 7 \\ \quad \quad \quad 0 \end{array} \quad \begin{array}{r} 1 \ 1 \ 0 \rightarrow 6 \\ 1 \ 1 \ 1 \rightarrow 3 \end{array}$$

$$= A\bar{B}C + \bar{A}\bar{B}\bar{C} + A\bar{B}C + \bar{A}$$

$$= 5 \ 4 \ 7 \ 3 \ 6$$

$$= m_5 \ m_4 \ m_7 \ m_3 \ m_6$$

$$= \sum m(3, 4, 5, 6, 7)$$

$$F_4 = \sum m(0, 1, 3)$$

$$= \bar{A}\bar{B} + \bar{A}B + AB$$

$$F_5 = \sum m(0, 7, 8, 12, 14)$$

$$= 0000 \quad 0111 \quad 1000 \quad 1100 \quad 1110$$

$$= \bar{A}\bar{B}\bar{C}\bar{D} \quad \bar{A}B\bar{C}D \quad A\bar{B}\bar{C}\bar{D} \quad \bar{A}\bar{B}CD$$

$$F_6 = A\bar{B}\bar{C} + B\bar{C} + \bar{B}CD -$$

$$11101 \quad 1110 \quad 110 \quad 010 \quad 1111 \quad 0111$$

=

$$= 1101 \rightarrow 13 \quad 110 \rightarrow 14 \quad 110 \rightarrow 15$$

$$1100 \rightarrow 12 \quad 0100 \rightarrow 4 \quad 0111 \rightarrow 7$$

$$0110 \rightarrow 6$$

$$1100 \rightarrow 12$$

$$\Rightarrow \Sigma_m(4, 7, 12, 13, 14, 15)$$

$$F_6 = \Sigma_m(4, 6, 7, 12, 13, 14, 15)$$

$$F_7 = A \bar{B} \bar{C} + \bar{A} \bar{B} \bar{D} + \bar{B} \bar{D} + \bar{B} C$$

$$= A \bar{B} \bar{C} D \quad \bar{A} \bar{B} \bar{C} \bar{D} \quad A \bar{B} C \bar{D} \quad A \bar{B} C D$$

$$13 \leftarrow 1101 \quad 00 \quad 10 \rightarrow 2 \quad 000 \rightarrow 2 \quad 1101 \rightarrow 15$$

$$12 \leftarrow 1100 \quad 00 \quad 00 \rightarrow 0 \quad 000 \rightarrow 0 \quad 101 \rightarrow 14$$

$$1010 \rightarrow 10 \quad 0111 \rightarrow 7$$

$$0000 \rightarrow 8 \quad 0110 \rightarrow 6$$

Σ

2 variable

	A	B	Dec	Minterm
0	0	0	0	$m_0 \rightarrow \bar{A}\bar{B}$
0	1	1	1	$m_1 \rightarrow \bar{A}B$
1	0	0	2	$m_2 \rightarrow A\bar{B}$
1	1	0	3	$m_3 \rightarrow AB$

3 variable

	A	B	C	Dec	Minterm
0	0	0	0	0	$m_0 \rightarrow \bar{A}\bar{B}\bar{C}$
0	0	1	1	1	$m_1 \rightarrow \bar{A}B\bar{C}$
0	1	0	0	2	$m_2 \rightarrow \bar{A}B\bar{C}$
0	1	1	0	3	$m_3 \rightarrow \bar{A}B\bar{C}$
1	0	0	1	4	$m_4 \rightarrow A\bar{B}\bar{C}$
1	0	1	1	5	$m_5 \rightarrow A\bar{B}C$
1	1	0	0	6	$m_6 \rightarrow AB\bar{C}$
1	1	1	1	7	$m_7 \rightarrow ABC$

4 variable.

A	B	C	D	Dec
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15

minterm

- $m_0 \rightarrow \bar{A} \bar{B} \bar{C} \bar{D}$
- $m_1 \rightarrow \bar{A} \bar{B} \bar{C} D$
- $m_2 \rightarrow \bar{A} \bar{B} C \bar{D}$
- $m_3 \rightarrow \bar{A} \bar{B} C D$
- $m_4 \rightarrow \bar{A} B \bar{C} \bar{D}$
- $m_5 \rightarrow \bar{A} B \bar{C} D$
- $m_6 \rightarrow \bar{A} B C \bar{D}$
- $m_7 \rightarrow \bar{A} B C D$
- $m_8 \rightarrow A \bar{B} \bar{C} \bar{D}$
- $m_9 \rightarrow A \bar{B} \bar{C} D$
- $m_{10} \rightarrow A \bar{B} C \bar{D}$
- $m_{11} \rightarrow A \bar{B} C D$
- $m_{12} \rightarrow A B \bar{C} \bar{D}$
- $m_{13} \rightarrow A B \bar{C} D$
- $m_{14} \rightarrow A B C \bar{D}$
- $m_{15} \rightarrow A B C D$

POS → product of sum

dt-14-10-25

Ex $(A+B)(A+\bar{B})(\bar{A}+B)$

→ when more than one sum terms are product together then it is called POS.

Ex $(A+B+C)(A+\bar{B}+\bar{C})(\bar{A}+\bar{B}+\bar{C}) \rightarrow \text{POS}$.

Standard POS → If each product term contains all the variables (either complemented or non complemented).

Ex $(A+B)(A+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C}) \rightarrow \text{convert it to standard POS}$
 $\Rightarrow (A+B+\bar{C} \cdot \bar{C})$
 $\Rightarrow (A+B+C)(A+B+\bar{C})(\bar{A}+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C})$.

→ Standard POS

dt-15-10-25

$$(A+B)(A+C)$$

$$= A \cdot A + A \cdot C + B \cdot A + B \cdot C$$

$$= A + AC + AB + BC$$

$$= A [1 + C + B] + BC$$

$$= A + BC$$

$$(A+B)(A+C) = A + BC \quad \leftarrow$$

$$A + BC = (A+B)(A+C) \quad \leftarrow$$

$$F_3 = (A+B)(A+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C})$$

- convert to standard pos.

$$= (A+B+C\bar{C})(A+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C})$$

$$= (A+B+C)(A+B+\bar{C})(A+\bar{B}+C)(\bar{A}+\bar{B}\bar{C})$$

standard pos

$$F_4 = (A+B+\bar{C})(\bar{A}+\bar{C})(\bar{B}+C)$$

$$= (A+B+\bar{C})(\bar{A}+(B.\bar{B})+\bar{C})(A.\bar{A}+\bar{B}+C)$$

$$= (A+B+\bar{C})(\bar{A}+B+\bar{C})(\bar{A}+\bar{B}+\bar{C})(A+\bar{B}+C)(\bar{A}+\bar{B}+C)$$

Standard pos

→ Binary value assignment →
In standard POS variable is taken as '0' and variable complement is taken as '1'. $\begin{array}{l} A \rightarrow 0 \\ \bar{A} \rightarrow 1 \end{array}$

Ex $(A+B+\bar{C})(\bar{A}+\bar{B}+\bar{C})(\bar{A}+B+C) \rightarrow$

0 0 1 1 1 1 1 0 0

$$F_5 = (A+B)(A+\bar{B}+\bar{C})(A+C)$$

$$\begin{matrix} A & B & C \\ 0 & 0 & 0 \\ 0 & 0 & 1 \end{matrix}$$

$$\begin{matrix} A & \bar{B} & \bar{C} \\ 0 & 1 & 1 \end{matrix}$$

$$\begin{matrix} A & B & \bar{C} \\ 0 & 0 & 1 \\ 0 & 1 & 1 \end{matrix}$$

~~$F_5 = (A+B+C)(A+B+\bar{C})(A+\bar{B}+\bar{C})$~~

Maxterm \rightarrow Each term in a standard POS is called a maxterm.

It is represented by 'M' with subscript decimal numbers.

Ex. $F_6 = (A+B+C) (A+\bar{B}+C) (\bar{A}+\bar{B}+\bar{C})$.

Represent is product of Maxterms.

Binary = 0 0 1 0 1 1 1 1 1

Decimal = 1 3 7

Maxterms =

$$M_1, M_3, M_7$$

(~~12~~)

$$F_6 = \prod M(1, 3, 7)$$

$$F_7 = (A+\bar{B}) (\bar{A}+\bar{B}+C+\bar{D}) (A+\bar{D}) \rightarrow \text{represent is Product of Max terms.}$$

	$A \bar{B} C \bar{D}$	$\bar{A} \bar{B} C \bar{D}$	$A B C \bar{D}$	
Y \leftarrow	0 1 0 0 1 2	1 1 1 0 0	0 0 0 1 $\rightarrow 1$	
C \leftarrow	0 1 1 0		0 0 1 1 $\rightarrow 3$	
S \leftarrow	1 0 1		0 1 0 1 $\rightarrow 5$	
7 \leftarrow	0 1 1 1		0 1 1 1 $\rightarrow 7$	

$$\prod M(1, 3, 4, 5, 6, 7, 12)$$

$$= (A+\bar{B}+C+\bar{D}) (A+\bar{B}+C+\bar{D}) (A+\bar{B}+C+\bar{D}) (A+\bar{B}+C+\bar{D}) \\ (A+\bar{B}+C+\bar{D}) (A+\bar{B}+C+\bar{D}) (A+\bar{B}+C+\bar{D})$$

2 variables

A	B	dec	Maxterm	M ₀
0	0	0	$A + B$	M ₀
0	1	1	$A + \bar{B}$	M ₁
1	0	2	$\bar{A} + B$	M ₂
1	1	3	$\bar{A} + \bar{B}$	M ₃

3 variables

A	B	C	dec	Maxterm	Ex.
0	0	0	0	M ₀	$A + B + C$
0	0	1	1	M ₁	$A + B + \bar{C}$
0	1	0	2	M ₂	$A + \bar{B} + C$
0	1	1	3	M ₃	$A + \bar{B} + \bar{C}$
1	0	0	4	M ₄	$\bar{A} + B + C$
1	0	1	5	M ₅	$\bar{A} + B + \bar{C}$
1	1	0	6	M ₆	$\bar{A} + \bar{B} + C$
1	1	1	7	M ₇	$\bar{A} + \bar{B} + \bar{C}$

4 variables

0
0
0
0
0
1
1
1
1
1

4 variable

A	B	C	D	<u>dec</u>	
0	0	0	0	0	$A + B + C + D$
0	0	0	1	1	$A + B + C + \bar{D}$
0	0	0	1	2	$A + B + \bar{C} + D$
0	0	1	0	3	$A + B + \bar{C} + \bar{D}$
0	0	1	1	4	$A + \bar{B} + C + D$
0	1	0	0	5	$A + \bar{B} + C + \bar{D}$
0	1	1	0	6	$A + \bar{B} + \bar{C} + D$
0	1	1	1	7	$\bar{A} + \bar{B} + \bar{C} + D$
1	0	0	0	8	$\bar{A} + B + C + D$
1	0	0	1	9	$\bar{A} + B + C + \bar{D}$
1	0	1	0	10	$\bar{A} + B + \bar{C} + D$
1	0	1	1	11	$\bar{A} + B + \bar{C} + \bar{D}$
1	1	0	0	12	$\bar{A} + \bar{B} + C + D$
1	1	0	1	13	$\bar{A} + \bar{B} + C + \bar{D}$
1	1	1	0	14	$\bar{A} + \bar{B} + \bar{C} + D$
1	1	1	1	15	$\bar{A} + \bar{B} + \bar{C} + \bar{D}$

K-Map \rightarrow Systematic way of Minimization

\rightarrow Draw the K map?

\rightarrow 2 variable SOP $2^2 = 4$ squares.

		B	0	1
		A	0	1
A	0	$A\bar{B}$	$\bar{A}B$	
	1	$A\bar{B}$	$\bar{A}B$	m_3

		B	0	1
		A	0	1
A	0	$A+B$	$A+\bar{B}$	
	1	$\bar{A}+B$	$\bar{A}+\bar{B}$	M_3

\rightarrow For 3 variable SOP. $2^3 = 8$ terms.

		B	00	01	11	10	
		A	0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}C$	$A\bar{B}\bar{C}$	$A\bar{B}C$
C	0	m_0	m_1	m_2	m_3		
	1	$\bar{A}B\bar{C}$	$\bar{A}BC$	$AB\bar{C}$	ABC	m_4	m_5

		C	00	01
		A	$\bar{A}\bar{B}$	$\bar{A}B$
B	0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}C$	m_0
	1	$\bar{A}B\bar{C}$	$\bar{A}BC$	m_1

\rightarrow For 4 variables $2^4 = 16$ square.

		D	00	01	11	10
		A	$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}\bar{B}\bar{C}D$	$\bar{A}\bar{B}CD$	$\bar{A}\bar{B}C\bar{D}$
C	0	m_0	m_1	m_3	m_2	
	1	$\bar{A}B\bar{C}\bar{D}$	$\bar{A}B\bar{C}D$	$\bar{A}BC\bar{D}$	$\bar{A}BCD$	m_4

→ For a POS '1' is placed for the term which are present, a '0' or no entry for the term which are absent.

→ For a POS '0' is placed for the term which are present, a '1' or no entry for the term which are absent.

Ex. Draw the K-map.

$$(i) F_1 = A\bar{B} + A\bar{B} + \bar{A}\bar{B}$$

		\bar{B}	B
		0	1
\bar{A}	0	1	
	1		1
A		m_0	m_1
		m_2	m_3

$$(ii) F_2 = AB\bar{C} + A\bar{B}C + \bar{A}\bar{B}C + ABC + A\bar{B}\bar{C}$$

		$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
		00	01	11	10
\bar{A}	0		1		
	1	m_0	m_1	m_3	m_2
A		m_4	m_5	m_7	m_6

$$(iii) F_3 = \bar{A}\bar{B}\bar{C}D + AB\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + A\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D}$$

		$\bar{B}\bar{C}D$	$\bar{B}C\bar{D}$	$\bar{B}\bar{C}\bar{D}$	$B\bar{C}D$	$B\bar{C}\bar{D}$	$\bar{B}\bar{C}\bar{D}$
		00	01	11	10		
\bar{A}	0	1	1				
	1						
A							

$$(ii) F_5 = A\bar{B} + BCD + \bar{A}\bar{B}C + AB\bar{C}D$$

$$(iv) F_5 = \sum_m (0, 1, 3, 9, 12, 13)$$

$\bar{A}\bar{B}$	$\bar{C}\bar{D}$	00	01	11	10
00	1	1	1		
01					
11	1	1			
10		1			

$$(v) F_5 = A\bar{B}CD + A\bar{B}CD + \bar{A}\bar{B}CD + AB\bar{C}D$$

1 0 00	1 0 01	0 0 10	1 1 11
1 0 01	0 1 11	0 0 11	
1 0 11	1 0 11	0 0 11	
1 0 10	1 0 11	0 0 10	

$\bar{A}\bar{B}$	$\bar{C}\bar{D}$	00	01	11	10
00				1	1
01				1	
11				1	
10		1	1	1	1

K-map

$$F_1 = \sum m(0, 1, 5, 9, 13, 15)$$

$\bar{A} \bar{B}$	$\bar{A} B$	$A \bar{B}$	$A B$
00	1	1	
01		1	
11		1	1
10		1	



Adjacent squares

→ 2 variable K map

\bar{A}	$B=0$	$B=1$
0	1	1
1	1	1

$$F = 1$$

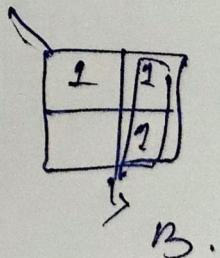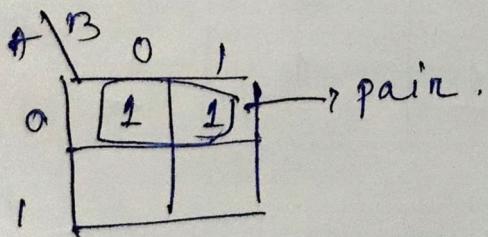- If all the square contains '1' the result is '1'.
- In minimizing we have to include all the ones '1's.
- In case of two variable K map two adjacent '1's (pair) gives a product of 1 variable.
- And a single 1 gives the product of 2 variables.



$$\bar{A}\bar{B} + \bar{A}B$$

$$\Rightarrow \bar{A}(\bar{B} + B) \xrightarrow{1}$$

$$= \bar{A}$$

$$\text{Ans} - \bar{A}$$

	$A \setminus B$	0	1
0	1		
1		1	

$G_1 = 1$

$G_2 = 1$

$$\underline{\bar{A}B + AB}$$

→ For 3 variable K map a group of 8 '1's (octet) gives a product = 1.

	$A \setminus BC$	00	01	11	10
0	1	1	1	1	
1	1	1	1	1	

$$F = 1$$

- a group of four '1's (quad) gives a product of one variable.
- a group of two ones (pairs) gives a product of two variables.
- a single one gives a product of 3 variables.

Adjacent is defined as a single variable change.

	$A \setminus BC$	00	01	11	10
0	1	1	1	1	
1					

quad.
= \bar{A}

E7.

minimize the following expression.

(i) $F_1 = AB + A\bar{B} + \bar{A}\bar{B}$

A	B	0	1
0	1	1	
1		1	1

$$\cancel{AB} + \cancel{A\bar{B}}$$

$$\underline{\bar{B} + A}$$

(ii) $F_2 = AB\bar{C} + ABC + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C}$

		Gm 1		Gm 2			
		00	01	11	10		
A	B	0	1	1			
		1		1	1	— Gm 3	

$$Gm 1 = \bar{A}\bar{B}$$

$$Gm 2 = \bar{A}C$$


$$Gm 3 = AB$$

$$F_2 = \bar{A}\bar{B} + \bar{A}C + AB$$

on. $F_2 = \bar{A}\bar{B} + BC + AB$

Minimum no of terms with minimum of variable.

$$f_3 = \sum m(0, 1, 5, 2, 6, 7)$$

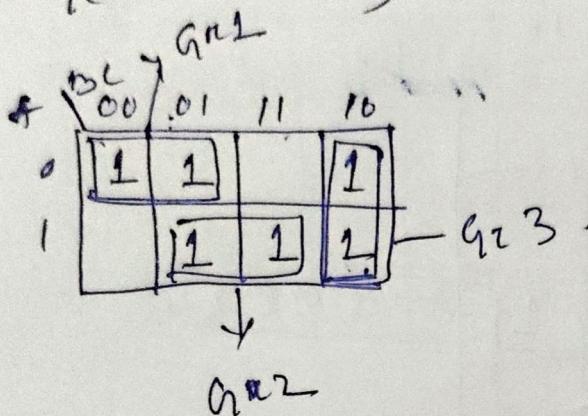

$$f_3 = \overline{AB} + AC + BC$$

dt-22-10-25

4 variable Kmap

		AB		CD			
		00	01	11	10		
00	00	1	1	1	1		
	01	1	1	1	1		
11	11	1	1	1	1		
	10	1	1	1	1		

- If all 16 squares are '1' then the result is 1.
- For Eight ones (octate) the result is the product of one variable.
- For four ones (quad) the result is the product of two variables.
- For two ones (pair) the result is the product of three variables.
- For a single one the result is the product of four variables.

$$F_1 = ABCD + A\bar{B}CD + \bar{A}\bar{B}\bar{C}\bar{D} + A\bar{B}CD + \bar{A}\bar{B}\bar{C}\bar{D}$$

AB \ CD

		Gm 2	
		00	01
00	00	1	1
	01		
01	11		
	10		
11	00		
	01		
10	11	1	1
	10	1	

Gz 3

Gz 2

~~ABC + BCD + ABC~~

$$\bar{A}\bar{B}\bar{C} + BCD + ABC$$

$$f_1 = \bar{A}\bar{B}\bar{C} + A\bar{B}C + \bar{B}CD$$

$$F_2 = \sum_m(2, 5, 6, 9, 12, 13)$$

AB \ CD

		Gm 4	
		00	01
00	00		
	01		
01	11	1	
	10		
11	00		
	01	1	
10	11	1	1
	10	1	

1

2

~~ABC + BCD~~

$$f_2 = \bar{A}C\bar{D} + A\bar{C}D + A\bar{B}\bar{C} + B\bar{C}D$$

$$F_3 = \sum_m (0, 1, 2, 3, 8, 9, 10, 11)$$

Ans	00	01	11	10
00	1	1	1	1
01				
11				
10	1	1	1	1

$$F_3 = \bar{B}$$

$$F_4 = \sum_m (4, 5, 6, 7, 12, 13, 14, 15)$$

Ans	00	01	11	10
00				
01	1	1	1	1
11	1	1	1	1
10				

$F_4 = B$

$$F_5 = \sum_m (2, 6, 8, 9, 10, 11, 14)$$

Ans	00	01	11	10
00				1
01		1		1
11				
10	1	1	1	1

$= A\bar{B} + C\bar{D}$

~~$= \bar{B}C$~~

$F_5 = A\bar{B} + C\bar{D}$

$$d = 24 - 10 - 25$$

$$(i) F_1 = \sum m(0, 1, 4, 5, 8, 9, 10, 11, 14, 15)$$

$$(ii) F_2 = \sum m(0, 2, 5, 7, 8, 10, 13, 15)$$

$$(iii) F_3 = \sum m(1, 3, 4, 6, 9, 11, 12, 14)$$

$$(iv) F_4 = AB + A\bar{B}D + A\bar{B}C\bar{D} + BC$$

$$(v) F_5 = BC + A\bar{C} + AB + BCD$$

(i)

$A\bar{B}\bar{C}\bar{D}$	00	01	11	10
00	1	1		
01	1	1		
11			1	1
10	1	1	1	1

$$\bar{A}\bar{C} + A\bar{B} + AB$$

(ii)

$\bar{A}\bar{B}\bar{C}\bar{D}$	00	01	11	10
00	1			1
01	0	1	1	
11		1	1	
10	1			1

$$\bar{B}\bar{D} + BD$$

(iii)

	00	01	11	10
00		1	1	
01	1			1
11	1			1
10		1	1	

$$F_3 = \overline{B}D + \overline{BD}$$

(iv)

AB ^{CD}	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}B$				
$A\overline{B}$				
\overline{AB}				

ABCD	$\overline{A}\overline{B}CD$	$A\overline{B}CD$	$AB\overline{C}D$
0100	1101	1010	0110
0101	1111	1111	0111
0110			1110
0111			1111

$$\begin{aligned} & \overline{AB}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{ABC}\overline{D} \\ & + \overline{ABC}D + A\overline{BC}D + ABCD \\ & + A\overline{BC}\overline{D} + AB\overline{CD}. \end{aligned}$$

$$f_4 = \overline{AB} + BD + \cancel{ACD}$$

AB ^{CD}	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}B$				
$A\overline{B}$				
\overline{AB}				

$$F_5 = A\overline{C} + BC$$

$\overline{ABC}D$	$\overline{AB}CD$	$A\overline{B}CD$	$AB\overline{C}D$
0110	1000	1100	0111
0111	1001	1101	0111
1110	1100	1110	1111
1111	1101	1111	1111


$$\begin{aligned} & \overline{ABC}\overline{D} + \overline{ABC}D + A\overline{BC}\overline{D} + \\ & A\overline{BC}D + A\overline{B}\overline{C}D + A\overline{B}CD + \\ & A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}D. \end{aligned}$$

Don't Care

- In certain situations the output maybe '0' or '1'.
- These situations are termed as don't care.
- In Kmap we will substitute 'd' or X for don't care combinations.

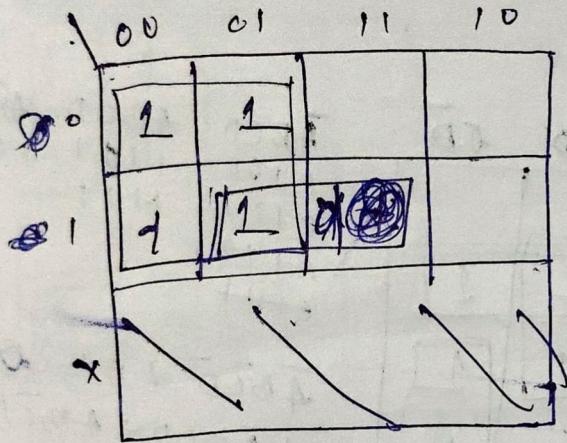Q1


$$F = \Sigma m(0, 1, 5) \cancel{d(4, 7)} + d(4, 7)$$



$\bar{A} \bar{B}$


dt-27-10-25
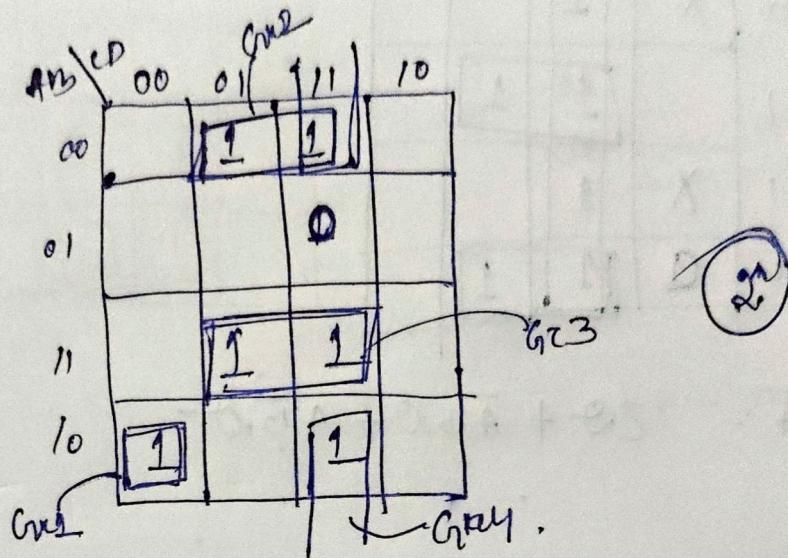
$$F = \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}CD + A\bar{B}CD + A\bar{B}\bar{C}\bar{D} + AB\bar{C}D + AB\bar{C}D$$



$$F = A\bar{B}\bar{C}D + \bar{A}\bar{B}D + AB\bar{D} + \cancel{AB} \cancel{C} \bar{B} \bar{C}D$$
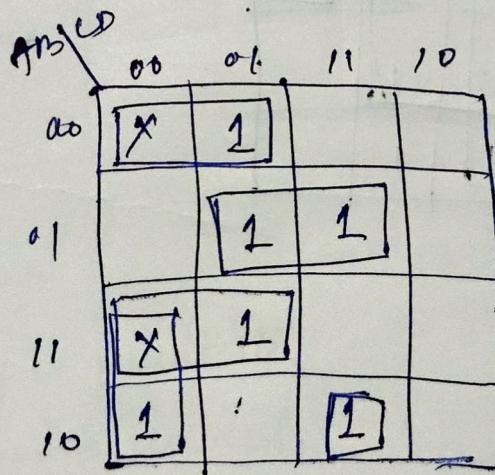
$$f = \sum (1, 5, 7, 11, 13) + \sum q (0, 12)$$



$$F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}D + AB\bar{C} + A\bar{C}\bar{D} + A\bar{B}CD$$

Q-

A B\CD	00	01	11	10
00	X	1		
01		1	1	
11	X	1		
10	0	1	1	

$$F = \bar{C}D + \bar{A}B\bar{D} + A\bar{B}D$$

Q-

A B\CD	00	01	11	10
00	1	X		X
01	1	1	1	X
11		X	1	
10	1	1	1	

Q-

	A ₃ A ₂	A ₁ A ₀	O ₁	O ₀
a ₃	1	x		x
a ₂	1	1	1	x
a ₁	x	1		
a ₀	1	1	1	



N.E.P.I.

Non-essential prime implicants.

EPI
Essential prime implicants.

dt-29-10-25

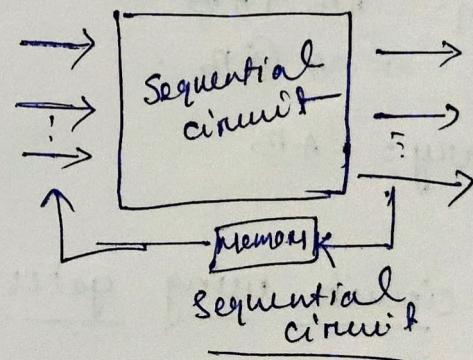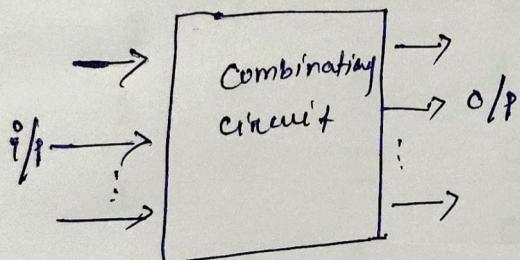Combinational Circuit Vs Sequential Circuit



Combinational Circuit

→ o/p depends only on present i/p.

→ no memory element is required.

→ there is no clock input.

e.g. half adder, Full adder
multiplexer, Deoder

etc.


→ o/p depends on present input and previous output.

→ memory element is required.

→ a clock input is required.
 | → clock.

e.g. counter, Flip flop,
register etc.

Half Adder

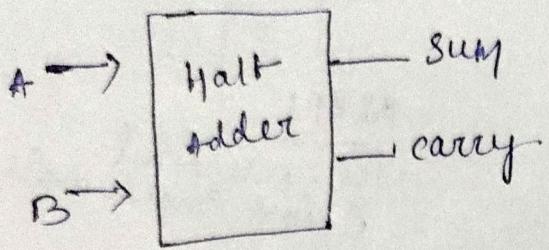


A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


$$\text{sum} = \bar{A}B + A\bar{B}$$
$$= A \oplus B$$

$$\text{carry} = AB$$

Logic circuits using gates:

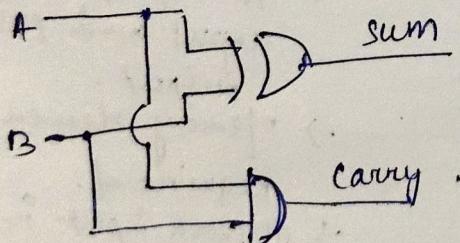

Full Adder

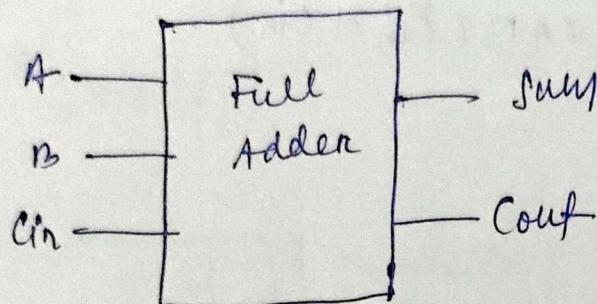

$$\begin{array}{r}
 & \text{Cin} \\
 & 1 \\
 A = & 1 & 1 & 0 & 1 \\
 B = & 1 & 1 & 0 & \\
 \hline
 \text{(1)} & 1 & 0 & 1 & 1 \\
 \downarrow & \text{Cout} \\
 \end{array}$$

Truth Table

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
1	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{aligned}
 \text{sum} &= \bar{A}\bar{B}\text{Cin} + \bar{A}\bar{B}\bar{\text{Cin}} \\
 &\quad + \bar{A}\bar{B}\bar{\text{Cin}} + \bar{A}B\text{Cin} \\
 \text{carry} &= \bar{A}B\text{Cin} + A\bar{B}\text{Cin} \\
 &\quad + A\bar{B}\bar{\text{Cin}} + AB\bar{\text{Cin}}
 \end{aligned}$$

$$\text{sum} = \text{Cin}(\bar{A}\bar{B} + AB) + \bar{\text{Cin}}(A\bar{B} + \bar{A}\bar{B})$$

$$= \text{Cin}(A \oplus B) + \bar{\text{Cin}}(A \oplus B)$$

$$= \text{Cin}(\overline{A \oplus B}) + \bar{\text{Cin}}(A \oplus B)$$

$$= Y\bar{X} + \bar{Y}X$$


$$= X \oplus Y = A \oplus B \oplus \text{Cin}$$

$$A \oplus B = X \\
 \text{Cin} = Y$$

Carry: $\bar{A}B\bar{C}in + \bar{A}\bar{B}Cin + A\bar{B}\bar{C}in + AB\bar{C}in$

$$\begin{aligned}&= Cin(\bar{A}B + \bar{A}\bar{B}) + \cancel{AB}(\bar{C}in + Cin) \\&= Cin(A \oplus B) + AB\end{aligned}$$

Sum:

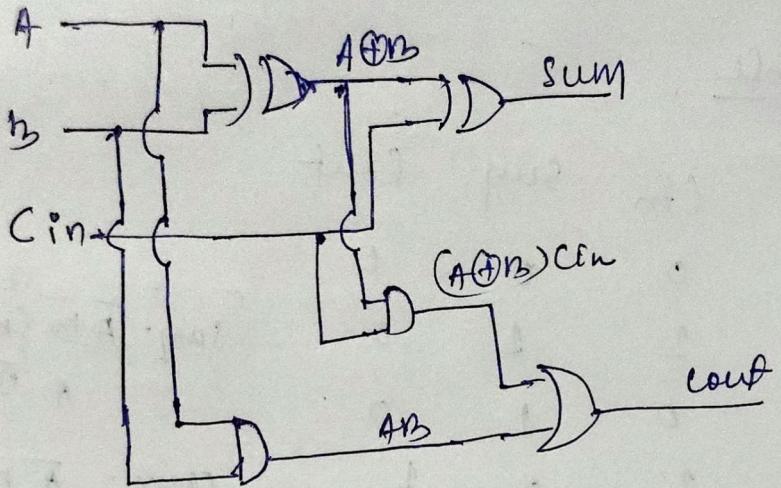

* Design: Full Adder using half adder and any of the logic gate.

HA


$$\text{sum} = A \oplus B$$

$$\text{carry} = AB$$

FA

$$\text{sum} = A \oplus B \oplus \text{cin}$$

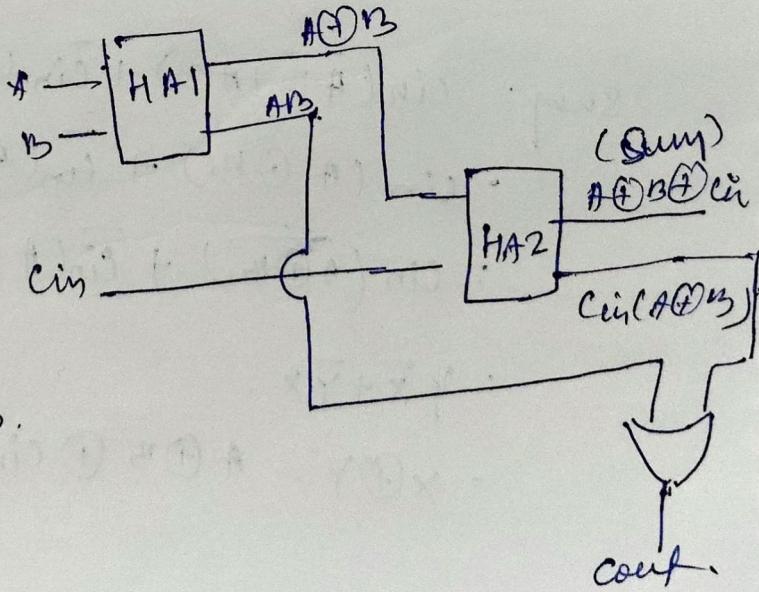
$$\text{cout} = \text{cin}(A \oplus B) + AB$$



combinational circuits



dt-03-11-25

Analysis

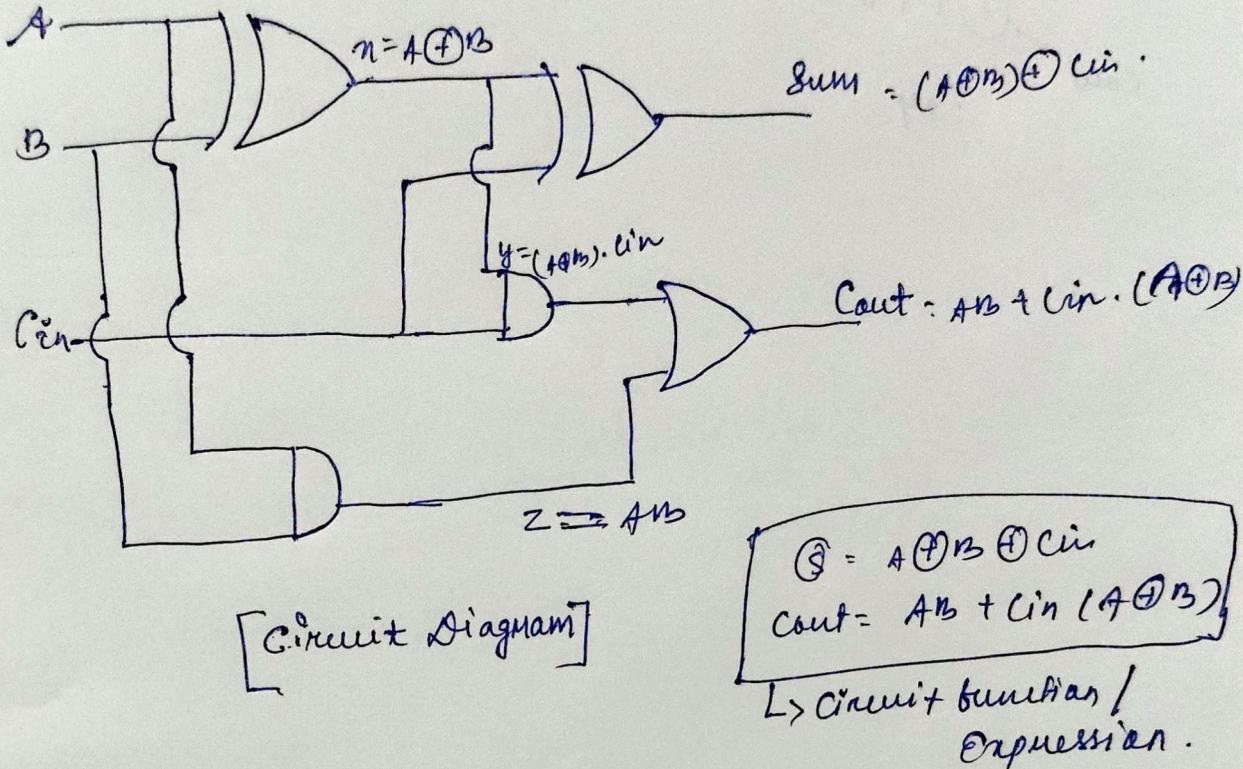

truth table

<u>A</u>	<u>B</u>	<u>C_{in}</u>	<u>S</u>	<u>cout</u>
0 + 0 + 0		0	0	0
0 + 0 + 1		1	0	0
0 + 1 + 0		1	0	0
0 + 1 + 1		0	1	1
1 + 0 + 0		1	0	0
1 + 0 + 1		0	1	1
1 + 1 + 0		0	1	1
1 + 1 + 1		1	1	1

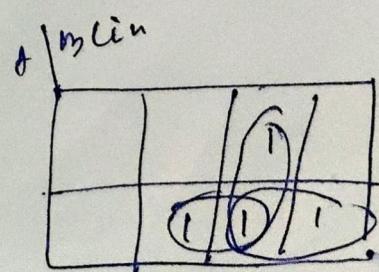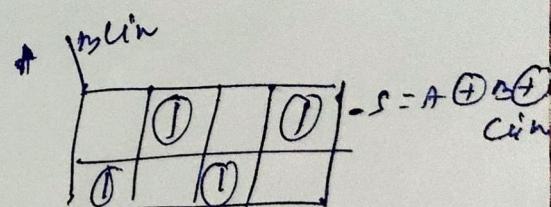

$$Cout = AB + BC_{in} + AC_{in}$$

7+7

+
1
1
1
1

1 HA + 2 FA

1 FA which
 $\sin = 0 \Rightarrow 2 HA$.


cont. ① 110
: 14

Multiplexer

dt-24-11-2025


2ⁿ input 1 output

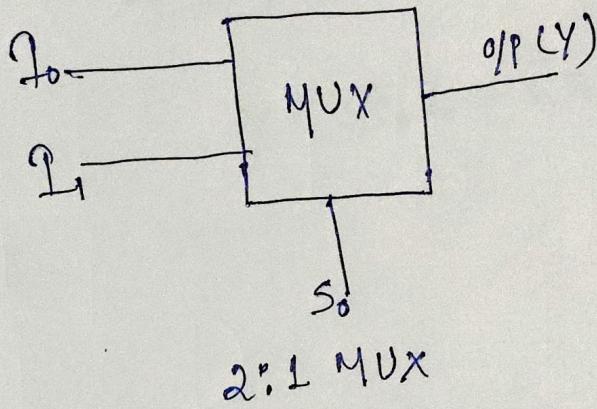\rightarrow address lines / selection lines.




S_0	Y
0	I_0
1	I_1

$$Y = \bar{S}_0 I_0 + S_0 I_1$$

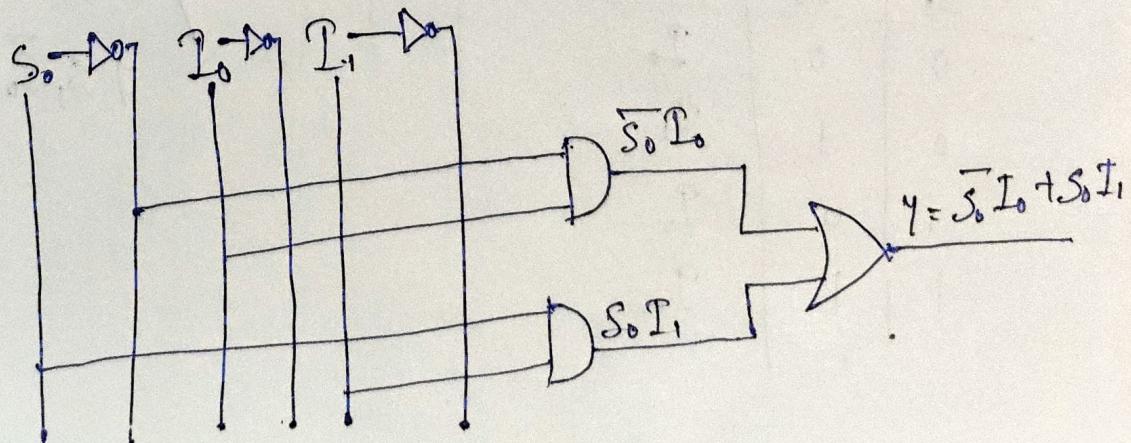


4x1 HUX.

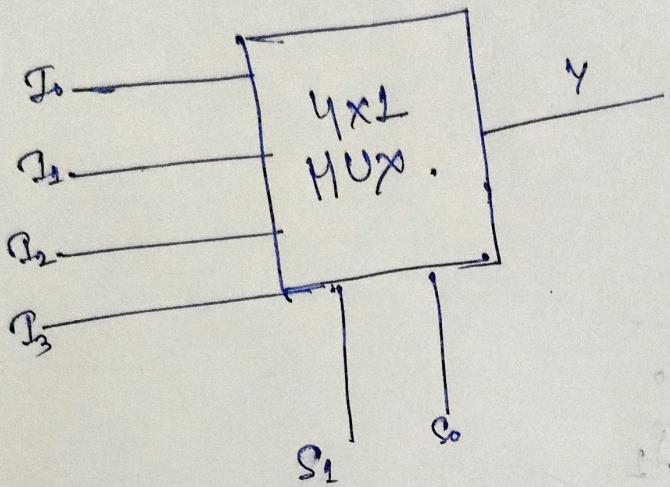

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3


Logical Expression :-
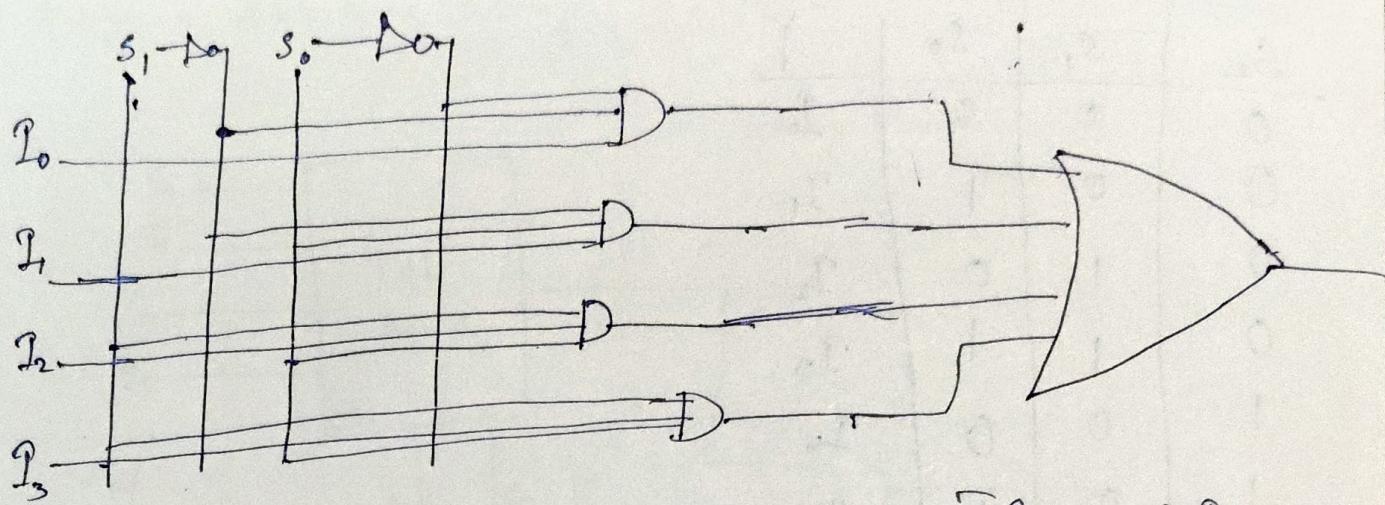
$$Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$



$$Y = \bar{S}_1 \bar{S}_0 P_0 + \bar{S}_1 S_0 P_1 + S_1 \bar{S}_0 P_2 + S_1 S_0 P_3$$

8×1

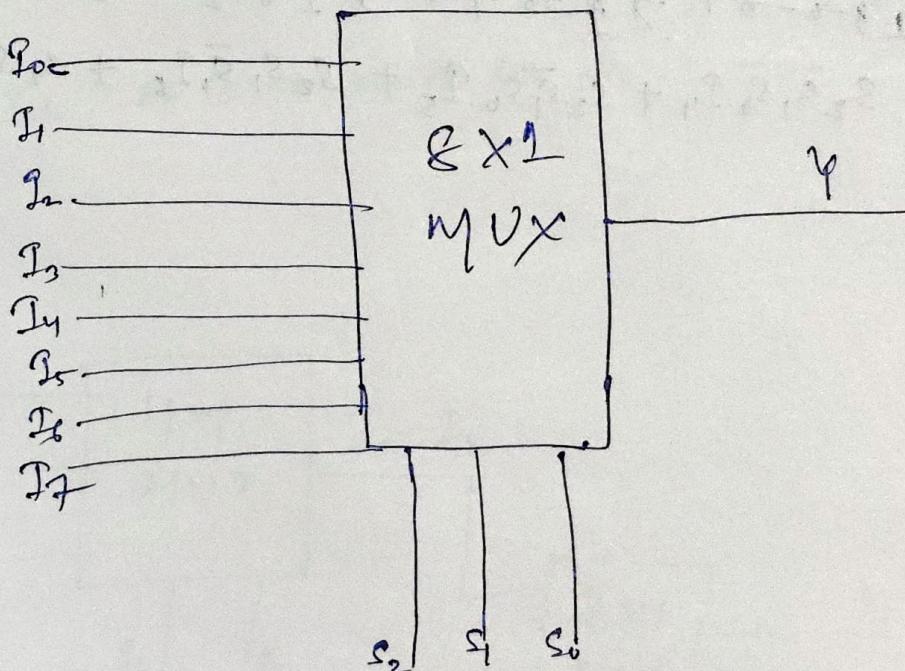


s_2	s_1	s_0	γ
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

Logical Expression:


$$\gamma = \bar{s}_2 \bar{s}_1 \bar{s}_0 I_0 + \bar{s}_2 \bar{s}_1 s_0 I_1 + \bar{s}_2 s_1 \bar{s}_0 I_2 + \bar{s}_2 s_1 s_0 I_3 \\ + s_2 \bar{s}_1 \bar{s}_0 I_4 + s_2 \bar{s}_1 s_0 I_5 + s_2 s_1 \bar{s}_0 I_6 + s_2 s_1 s_0 I_7.$$

→ Design a 8×1 MUX using 4×1 MUX.

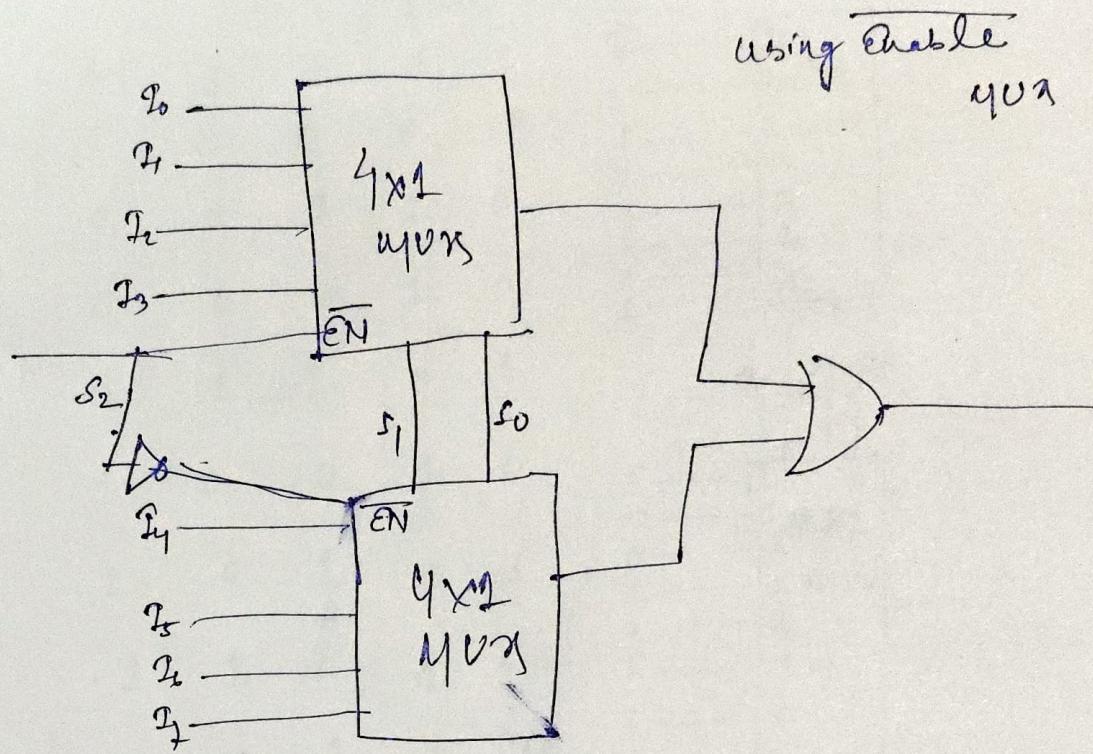


Enable → it is an active low pin.

\overline{EN}

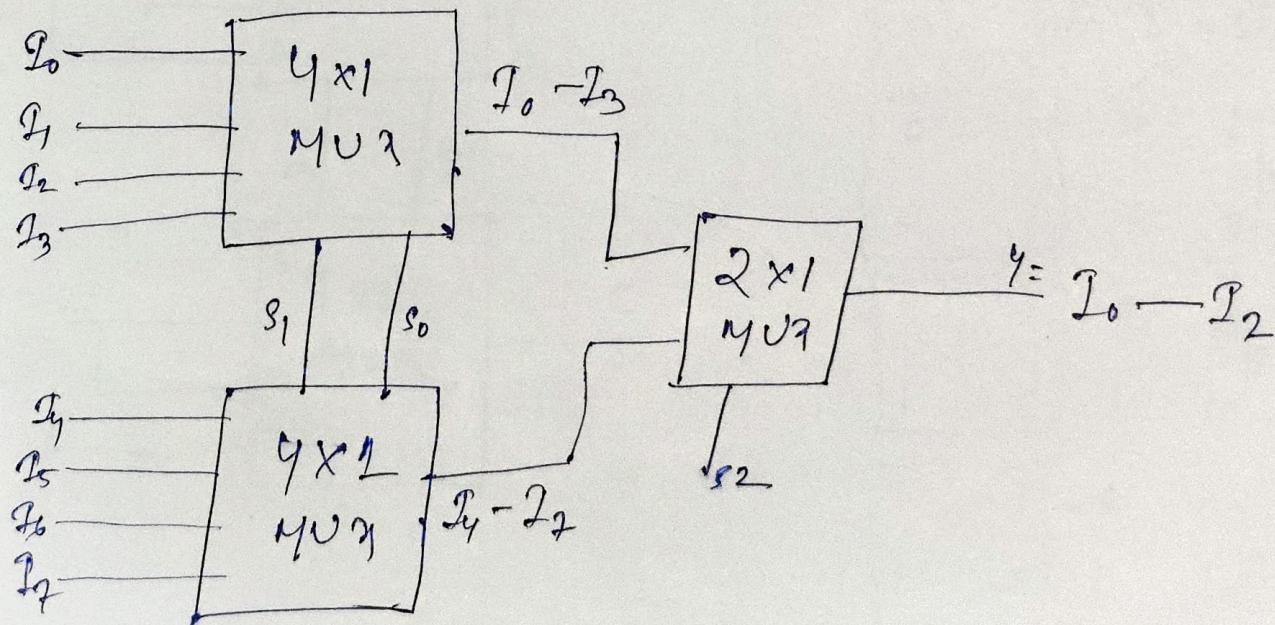


8x1 MUX using 4×1 MUX and 2×1 MUX.

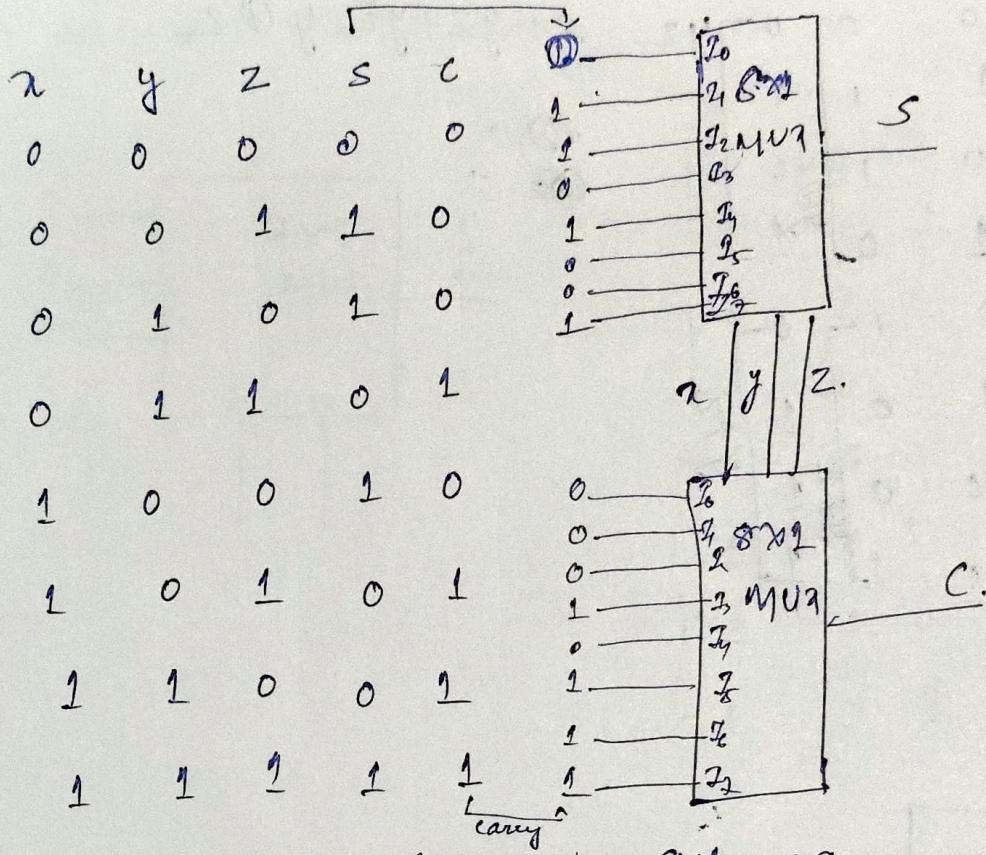En Design a Full Adder using 8×1 MUX, 4×1 MUX, 2×1 MUX



Full adder using 8×1 MUX

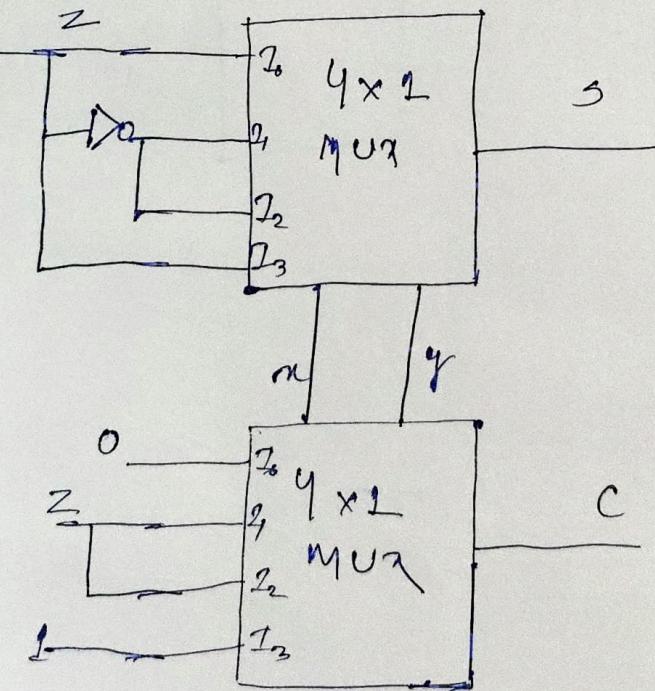



x	y	z	s	c
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full adder using 4×1 MUX

$$\begin{array}{cccccc}
 x & y & z & s & c \\
 \left[\begin{array}{ccccc}
 0 & 0 & 0 & 0 & yz \\
 0 & 1 & 1 & 0 & \\
 1 & 0 & 1 & 0 & \\
 0 & 1 & 0 & 1 & \\
 \end{array} \right] & yz & s = \bar{y}z + y\bar{z} = y \oplus z
 \end{array}$$

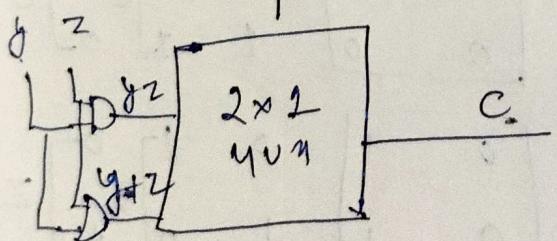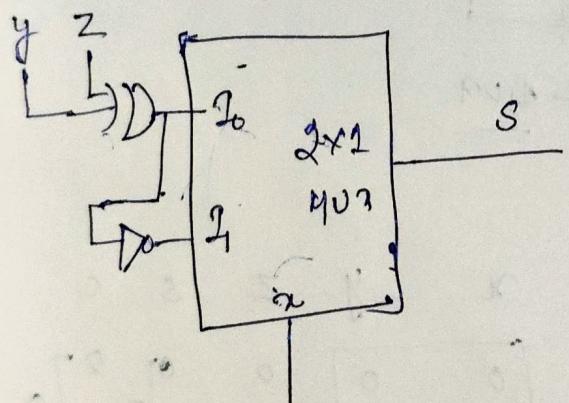
(1) (2)

$$\begin{array}{cccccc}
 1 & 0 & 0 & 1 & 0 & \\
 1 & 0 & 1 & 0 & 1 & \\
 1 & 1 & 0 & 0 & 1 & \\
 1 & 1 & 1 & 1 & 1 & \\
 \end{array}$$



Design the following function using 4×1 MUX.
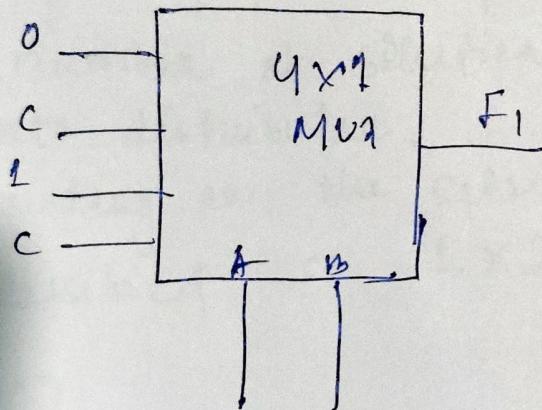
$$F_1 = AB'C + A\bar{B}C + A\bar{B}\bar{C} + \bar{A}BC.$$



$$\begin{matrix} & A & B & C \\ \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 1 \\ 0 & 1 & 0 \\ 1 & 1 & 1 \end{bmatrix} & 0 & 0 \end{matrix} \quad F_1$$

$$\begin{matrix} & A & B & C \\ \begin{bmatrix} 0 & 1 & 0 \\ 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 1 \end{bmatrix} & 0 & 1 \end{matrix} \quad C$$


$$\begin{matrix} & A & B & C \\ \begin{bmatrix} 1 & 0 & 0 \\ 1 & 0 & 1 \\ 0 & 1 & 1 \\ 1 & 1 & 1 \end{bmatrix} & 1 & 1 \end{matrix} \quad 1$$

$$\begin{matrix} & A & B & C \\ \begin{bmatrix} 1 & 1 & 0 \\ 1 & 1 & 1 \end{bmatrix} & 0 & 1 \end{matrix} \quad C$$

dt - 25-11-25

$F_2 = \sum_m(0, 1, 5, 9, 12, 13) \rightarrow 4:1 \text{ MUX}$


A	B	C	D	f_2
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

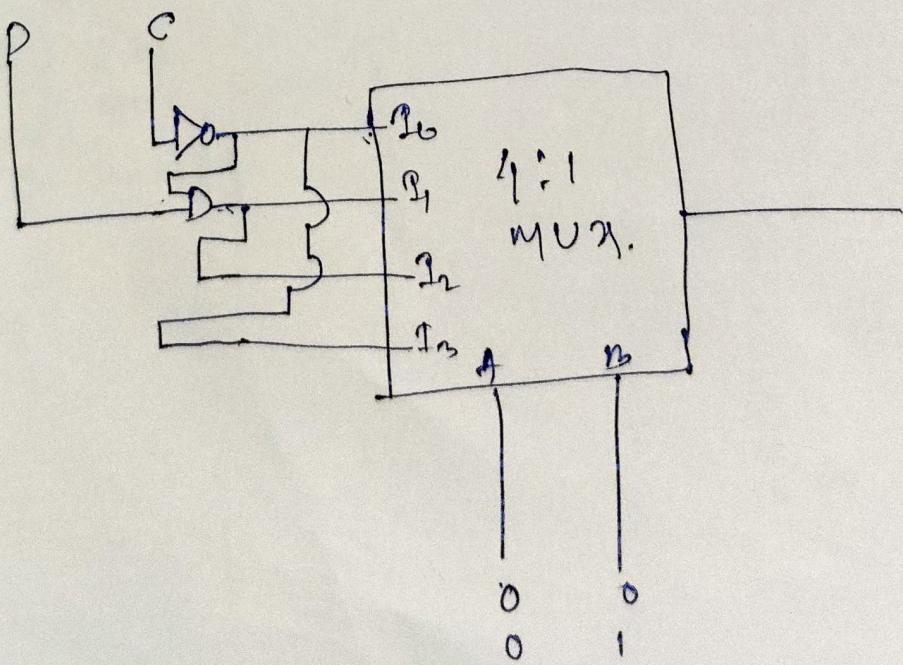

Demultiplexer
or
Demux.

- Single input 2ⁿ output.
- Number of selection line.
- Data distributor.
- Depending on the selection line demux are classified as 1x2, 1x4, 1x8, 1x16 - - -

1x2

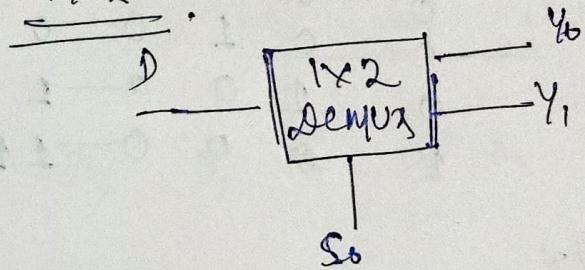


S0	Y ₁	Y ₀
0	0	0
1	0	1

• Table


Expression:

$$Y_0 = \overline{S_0}D$$

$$Y_1 = S_0D$$

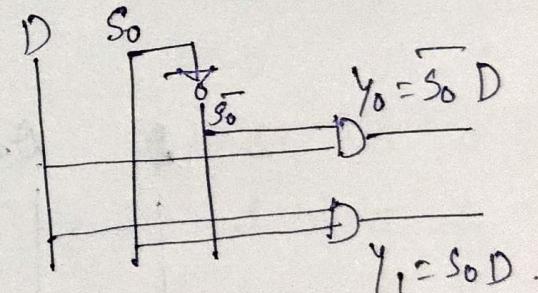

1x4

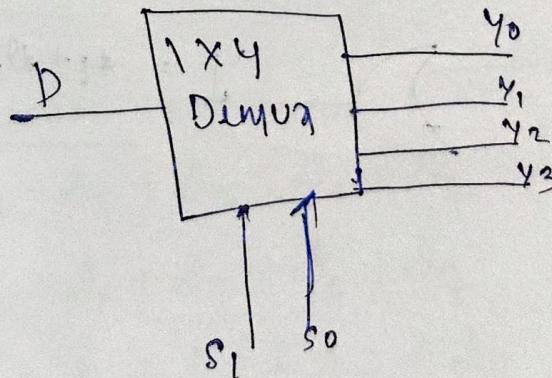

S ₁	S ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	D
0	1	0	0	0	0
1	0	0	0	0	0


Expression:

$$Y_0 = \overline{S_1}\overline{S_0}D$$


$$Y_1 = \overline{S_1}S_0D$$

$$Y_2 = S_1\overline{S_0}D$$


$$Y_3 = S_1S_0D$$

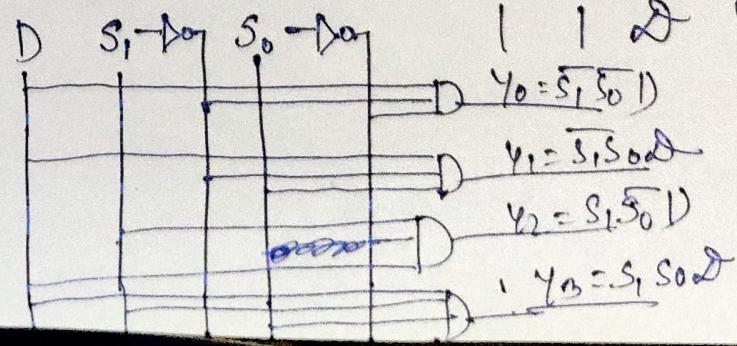

Encoder

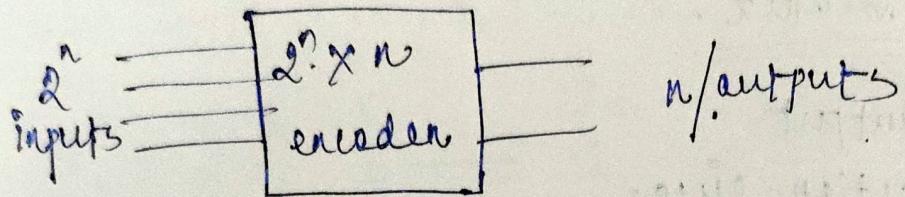


$\rightarrow 2^n$ inputs and n outputs.

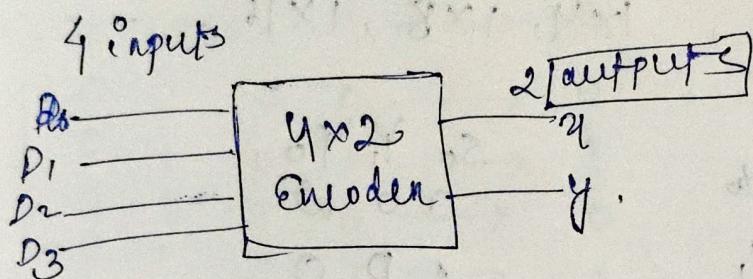


D_0	D_1	D_2	D_3	y_1	y_2
0	0	0	0	1	0
0	0	0	1	0	1
0	1	0	0	0	1
1	0	0	0	0	1

$$y_1 = D_2 + D_3$$

$$y_2 = D_1 + D_3$$

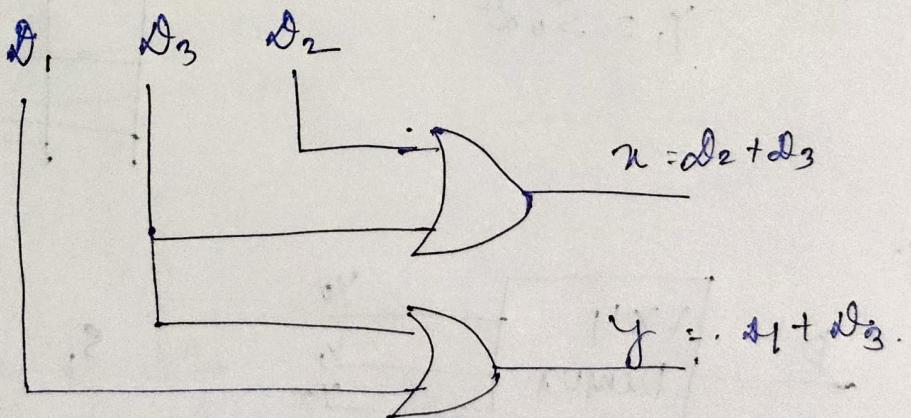

8×3

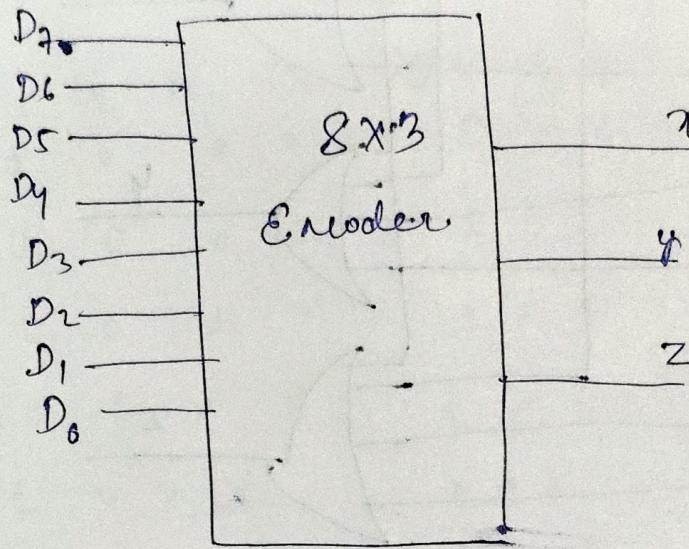


D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	x	y	z
							1	0	0	0
						1		0	0	1
							1	0	1	0
								0	1	1
						1		1	0	0
					1			1	0	1
				1				1	1	0
		1						1	1	1

Expression :

$$x = D_4 + D_5 + D_6 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$z = D_1 + D_3 + D_5 + D_7$$

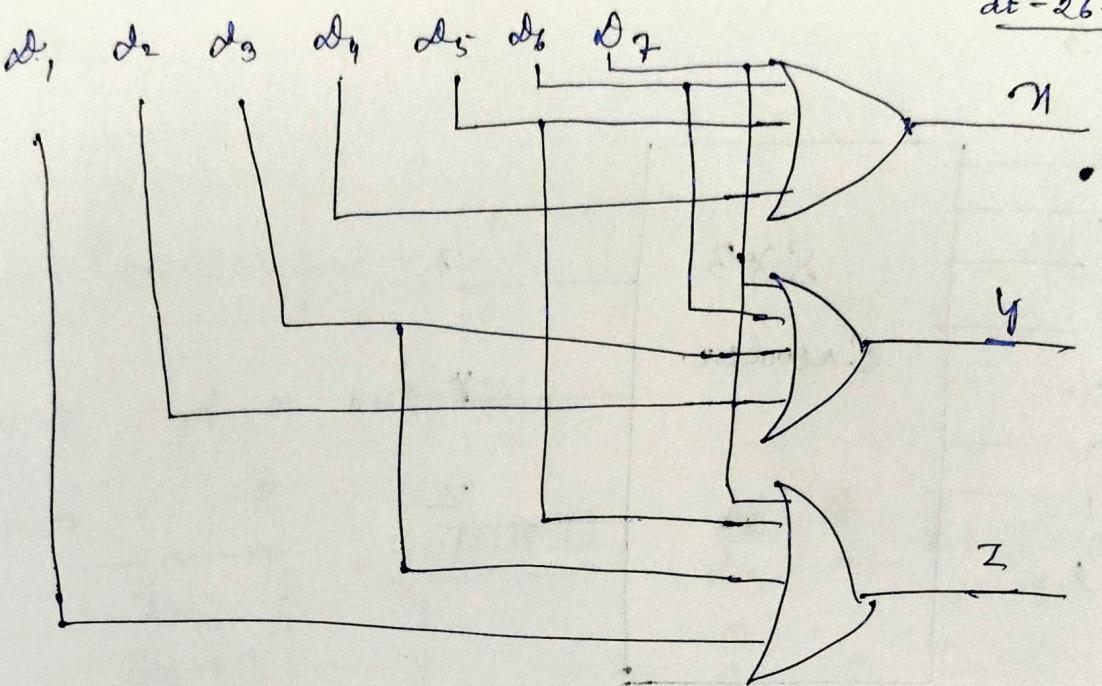

Priority Encoder

→ In normal encoder no bit at the output are present to represent all '0' combinations for the input.

→ If more than one input bits are '1' simultaneously the o/p can not be predicted.

for example: In 8×3 encoder if d_6 and d_7 are '1' simultaneously then the output is neither 110 nor 001 rather the output is 111.

For this reason we will assign priorities to the data bits.

and design priority encoder.

Design a 9×2 priority encoder.

D₃ having priority
D₀ having lowest priority



Design a 4×2 parity encoder.

D_3 having high
 D_0 lowest parity

D_3	D_2	D_1	D_0	Σ	η	y
0	0	0	0	0	0	X
0	0	0	1	1	0	0
0	0	1	X	1	0	1
0	1	X	X	1	1	0
1	X	X	X	1	1	1

K map for Σ

D_3	D_2	D_1	D_0	
00	00	01	11	10
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$$\Sigma = D_3 + D_2 + D_1 + D_0$$

K map for η


D_3	D_2	D_1	D_0
00	X		
01	1	1	1
11	1	1	1
10	1	1	1

$$\eta = D_3 + D_2$$


Kmap-Y

d ₃ d ₂ d ₁ d ₀		00	01	11	10
d ₃	d ₂	00	X	1	1
d ₂	d ₁	01	0	0	a
d ₁	d ₀	11	1	2	2
d ₀		10	1	1	1


$$y = d_3 + \bar{d}_2 d_1.$$

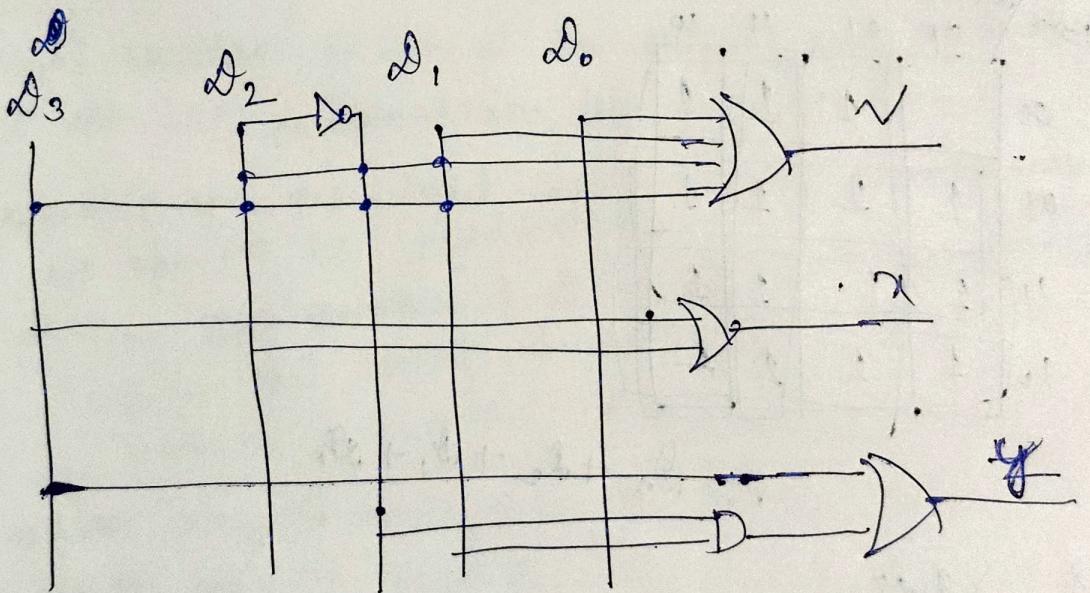

Decoder

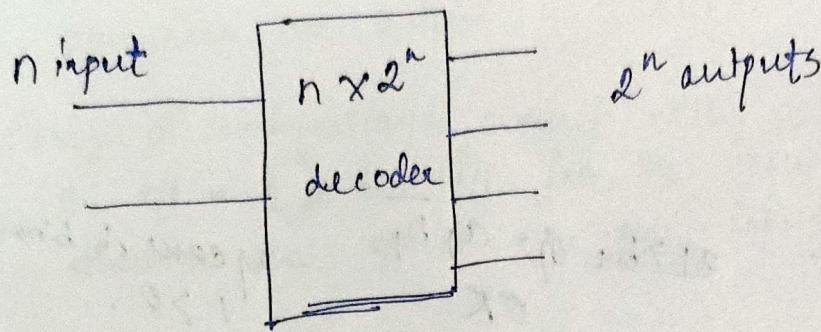

design a 2×4 decoder.

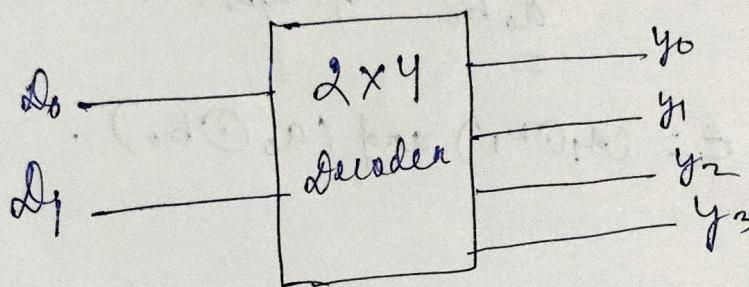


d_1	d_0	y_0, y_1, y_2, y_3
0	0	1
0	1	1
1	0	1
1	1	1

$$y_0 = \bar{d}_1 d_0$$

$$y_1 = \bar{d}_1 d_0$$

$$y_2 = d_1 \bar{d}_0$$

$$y_3 = d_1 d_0$$

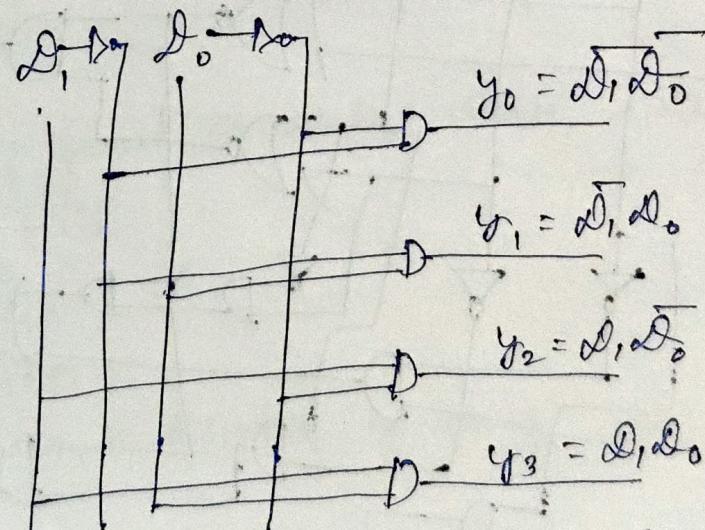

Comparator.

Let

$$A = a_1 a_0$$

$$B = b_1 b_0$$

① (i) $A > B$ $a_1 > b_1$, $\Rightarrow \cancel{G = a_1 \bar{b}_1}$ means in binary
 $a_1 \oplus b_1$
 $a_0 > b_0$ $G = \underline{a_1 \bar{b}_1} + (a_1 \oplus b_1)(a_0 \bar{b}_0)$

$$(ii) \quad a_1 = b_1 \quad a_0 > b_0$$

② Equality

$$a_1 = b_1 \quad a_0 = b_0$$


$$C = (a_1 \oplus b_1) \text{ and } (a_0 \oplus b_0)$$

③ $a_1 < b_1$

$$(iii) \quad a_1 = b_1 \quad a_0 < b_0$$

$$L = \bar{a}_1 b_1 + (a_1 \oplus b_1)(\bar{a}_0 b_0)$$

$C =$

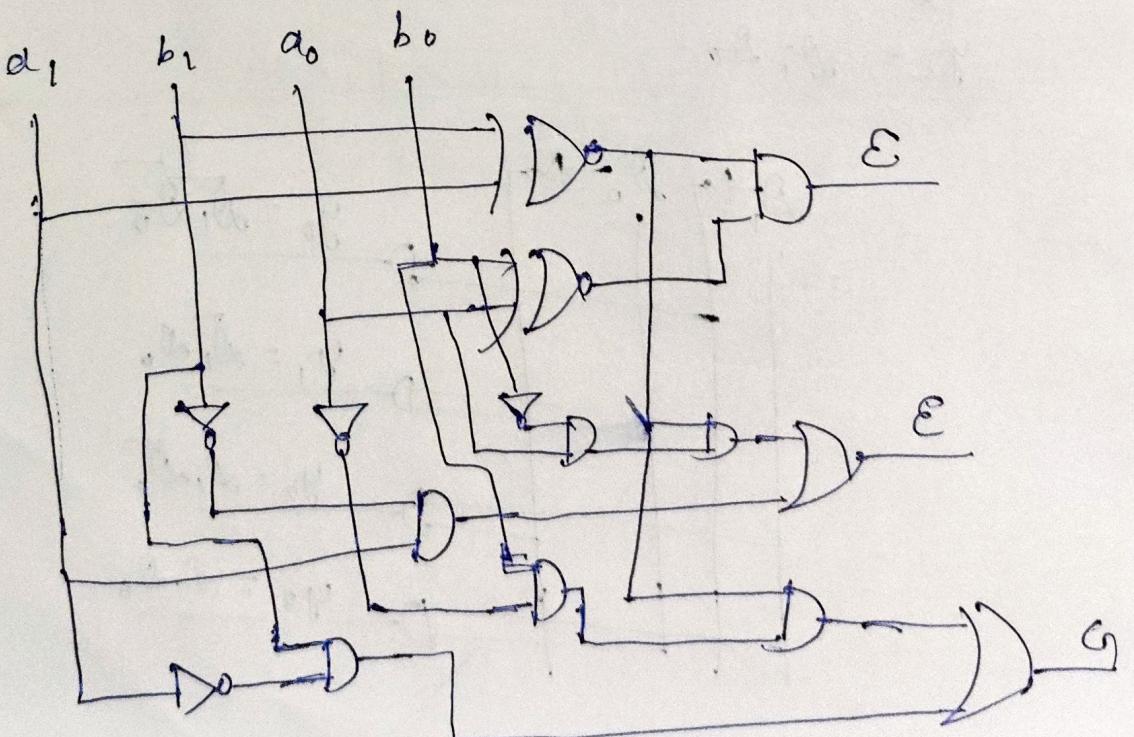

Q Design a combinational circuit that has 3 inputs and 1 output
the output is 1 when the value of the input is < 3
otherwise the output is zero. (^)

Q Design a combinational circuit with 3 i/p and 3 o/p.
the o/p is 1 > the i/p for the inputs 0, 1, 2, 3, 4, 5.
otherwise the o/p is 1 < the inputs.

df - 31/11/25

Difference between combinational circuit and sequential circuit..

Combinational

- The o/p depends upon present values of the inputs only.
- There is no feed back path or memory.
- Ex: Adder, subtractor, MUX, encoder.

sequential



- The o/p depends upon present values of the inputs as well as past values of the o/p's.
- There must be feedback path or memory.
- Ex: Flipflops, calculator, shift register.

Flipflops:

- Basic memory element. It has two stable states.
- S-R Flipflop
- D Flipflop
- J-K Flipflop
- T Flipflop
- flipflops can be designed by using NAND gates or NOR gates.
- Always there is a clock input in the flipflop.

dt-1-12-25

→ S-R Flipflop

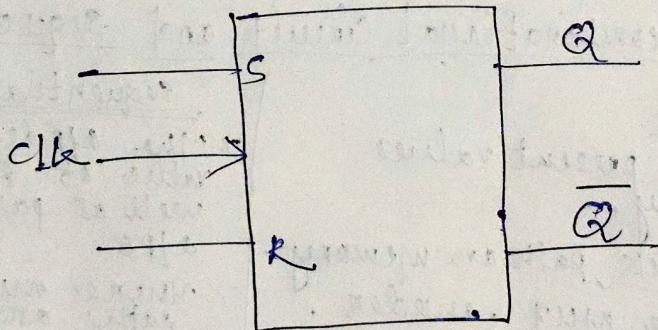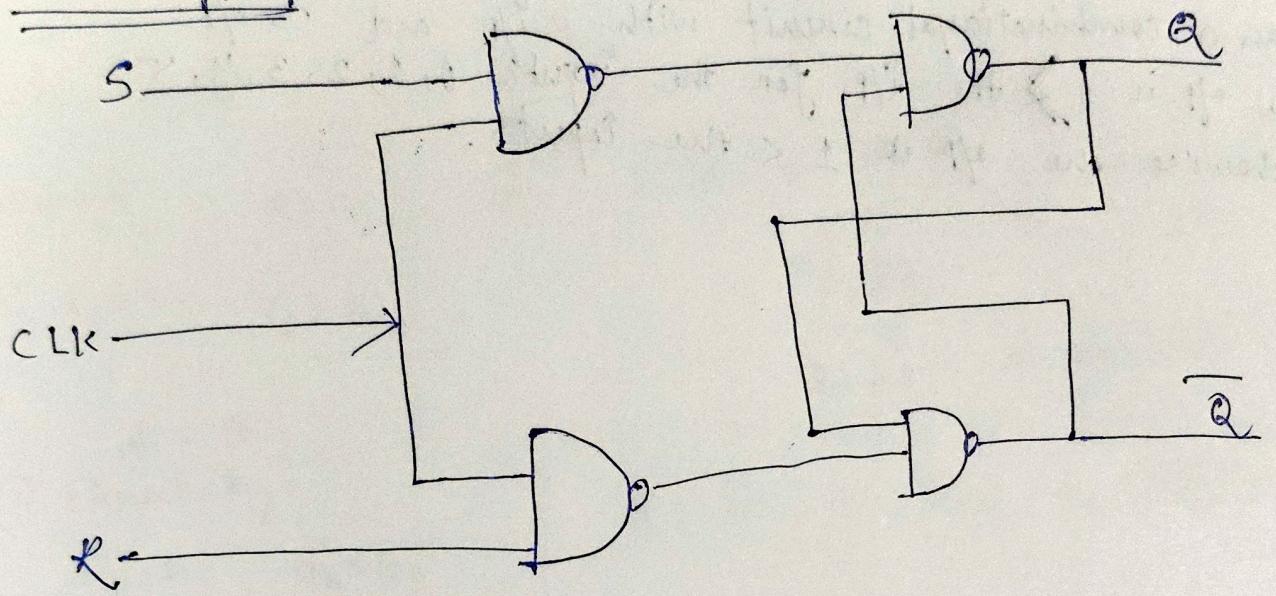

Block diagram



GLK	S	R	Q	\bar{Q}	comment
1	0	0	0/1	1/0 \rightarrow last state	
1	0	1	0	1 \rightarrow Reset	Two stable states of flip flop.
1	1	0	1	0 \rightarrow set	
1	1	1	1	1 \rightarrow invalid	

\therefore That's why S-R flip flop - Set Reset flip flop -

DT-02-12-25

D-FIFPFFOP


(Delay) FF

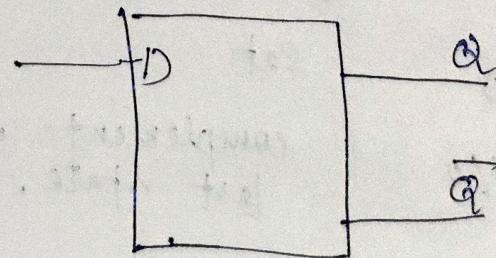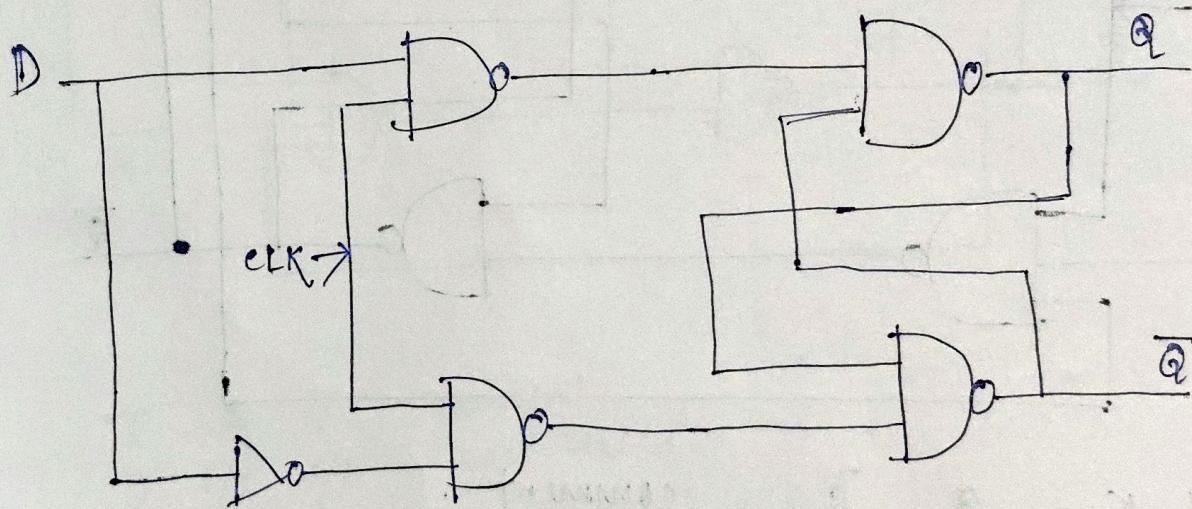


Block Diagram

D	Q	\bar{Q}	comment
0	0	1	→ Reset
1	1	0	→ Set.

JK FLIPFLOP :

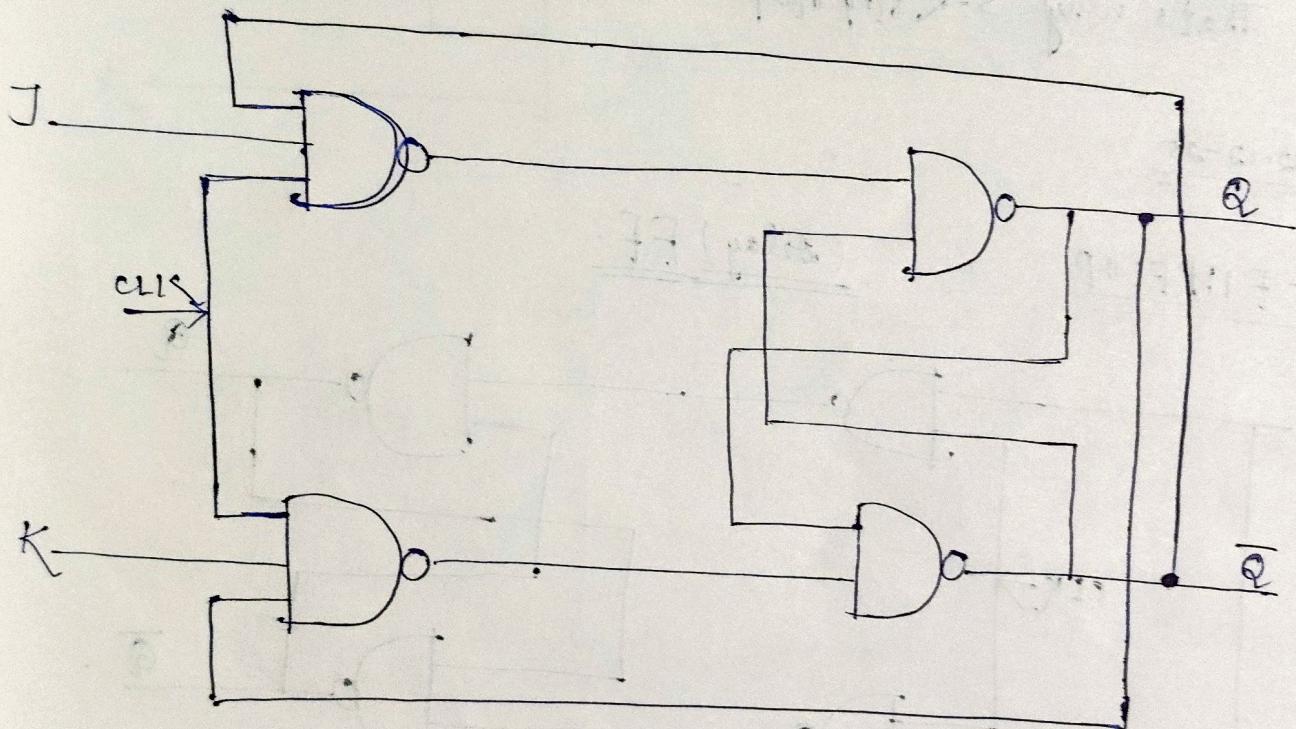


J	K	Q	\bar{Q}	comment ..
0	0	0/1	1/0	Last state
0	1	0	1	Reset
1	0	1	0	Set
1	1	0/1	1/0	complement of last state.

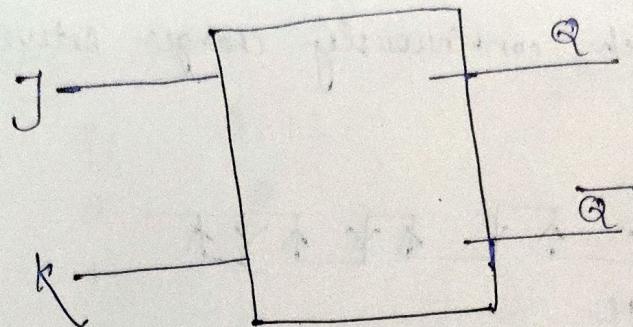

block diagram.

T- FLIPFLOP.

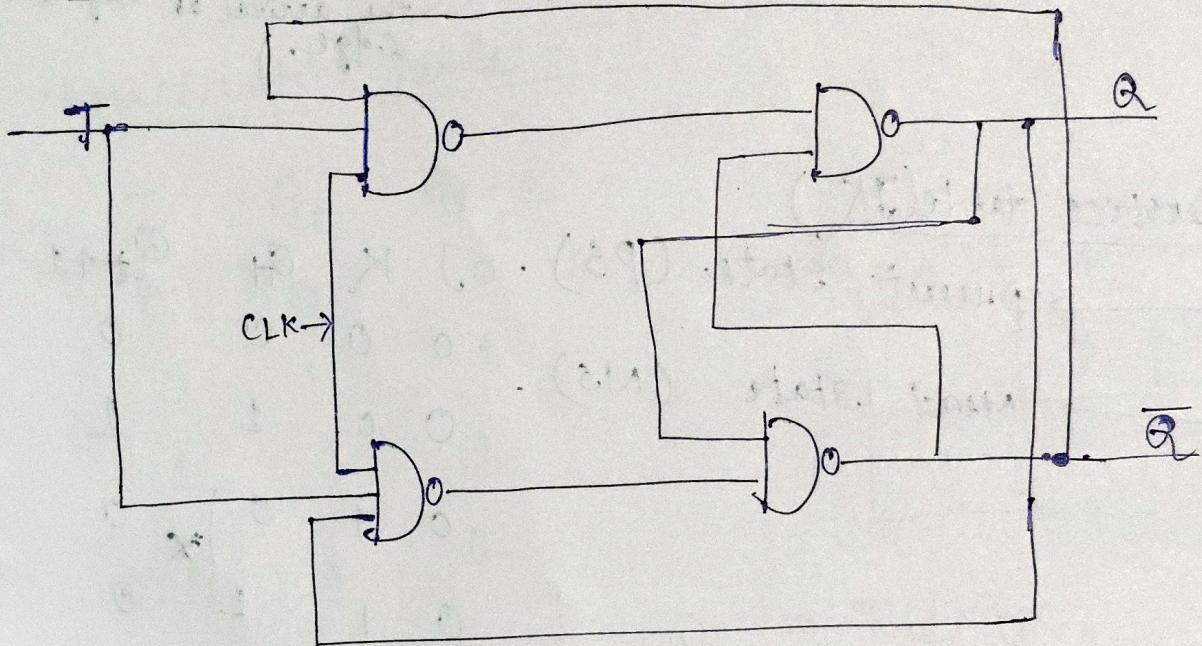


T	Q	\bar{Q}
0	0/1	1/0
1	1/0	0/1

complement
Last state,

complement of last
state or toggle.

CLOCK PULSE

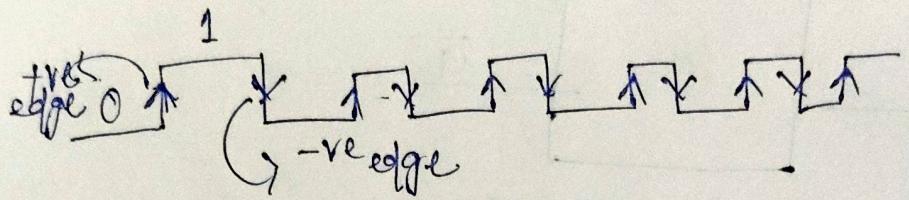→ Q_t is a signal which continuously changes between zero and one.




→ Flip flops are always edge triggered.

[-ve edge triggered] .

(Q_t changes state at the arrival of negative edge.)

Characteristics table (JK)

Q_t	J	K	Q_t	Q_{t+1}
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0 → 1	1
1	1	1	1 → 0	0

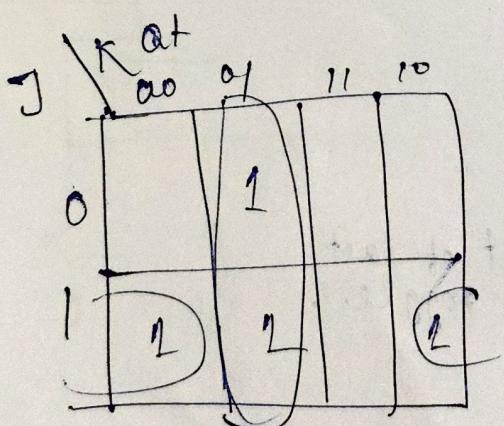


$$\hat{Q}_{t+1} = \bar{K}Q_t + J\bar{Q}_t$$

Characteristic equation for JK FF.

dt - 0.3 - 12-25

characteristics table - D.


D	Q _t	Q _{t+1}
0	0	0
0	1	0
1	0	1
1	1	1

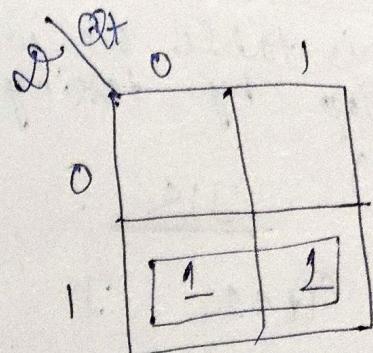

$$Q_{t+1} = D$$

characteristics table - T

T	Q _t	Q _{t+1}
0	0	0
0	1	1
1	0	1
1	1	0

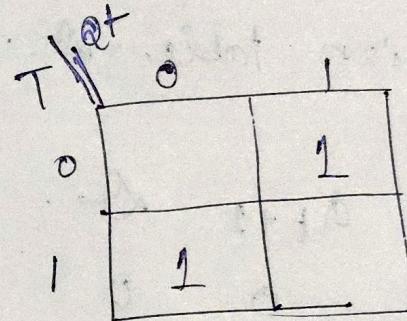

$$Q_{t+1} = T \oplus Q_t$$

Characteristic table SR

S	R	Q _t	Q _{t+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

Excitation table

→ In this table we will find the input to the flip flop by taking present state (PS) and next state (NS).

J K

Q_t	Q_{t+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Excitation table - D

Q_t	Q_{t+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

Excitation Table - T

Q_t	Q_{t+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

Excitation Table - SR

Q_t	Q_{t+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0


Convert SR FF to D FF

$$S \quad R \longrightarrow D$$


Excitation SR

D	Q_t	Q_{t+1}	S	R
0	0	0	0	X
0	1	0	0	1
1	0	1	1	0
1	1	1	X	0

K map for S

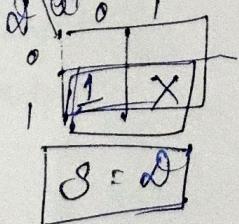

K map for R

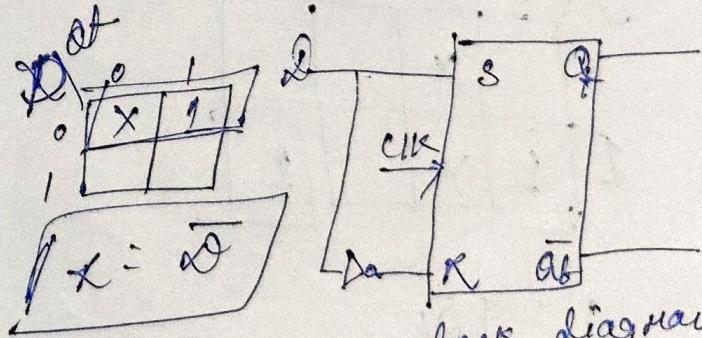


Block diagram
for SR to D

convert SR to JK

$SR \rightarrow JK$

J	K	Q_t	Q_{t+1}	S	R
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	X	0
1	1	0	1	1	0
1	1	1	0	0	1

K map of J

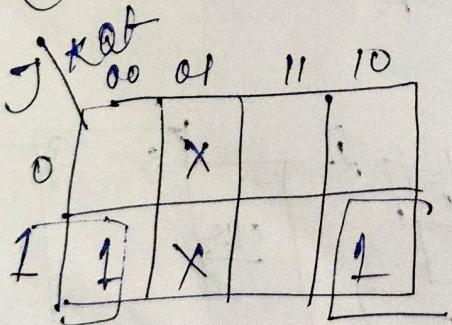


$$J = \bar{Q}_t Q_t$$

dt - 08-12-25.

Analysis of clocked sequential circuit (Cst)

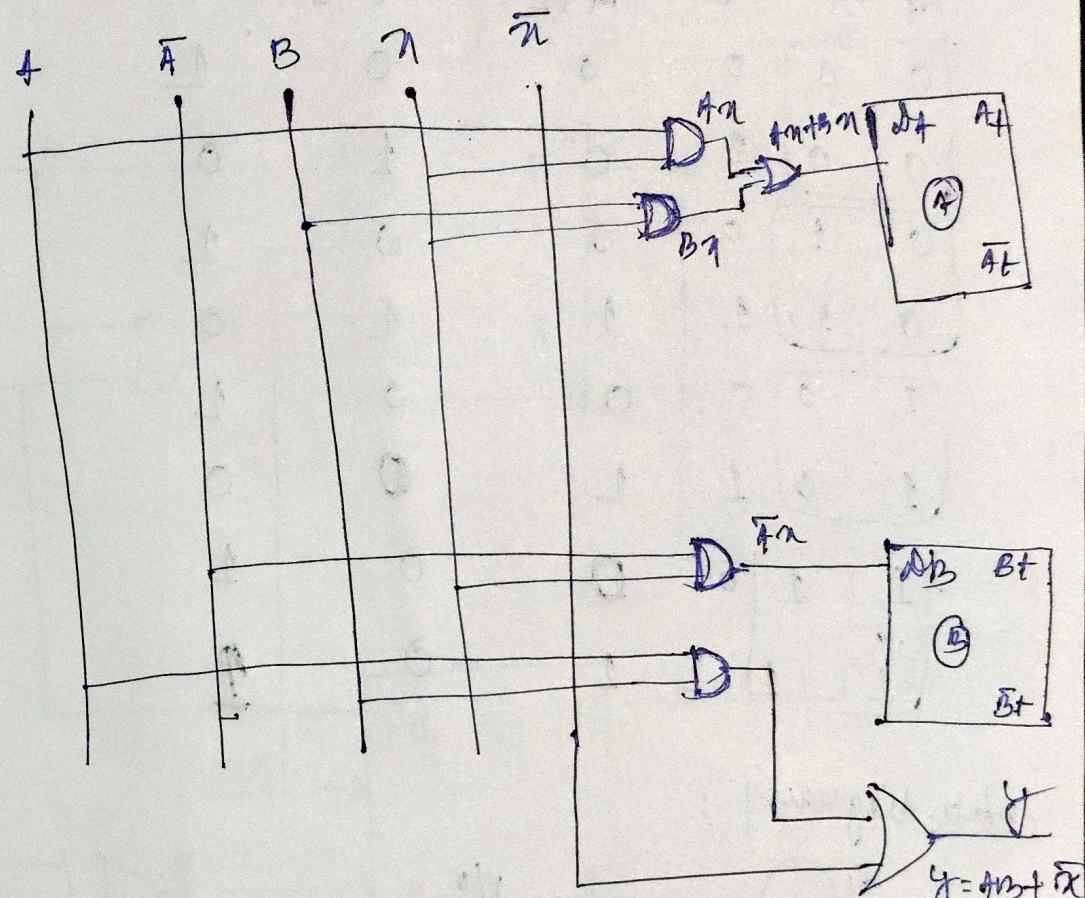- characteristics equation.
- state table.
- State diagram.



$$A_t \rightarrow P.S \quad A_t$$

$$B_t \rightarrow P.S \quad B_t$$

$$n \rightarrow \text{input}$$

$$y \rightarrow \text{output}$$

→ Characteristic equation


$$\rightarrow A_{t+1} = A_t \cdot q + B_t \cdot n$$

$$\rightarrow B_{t+1} = \bar{A}_t \cdot n$$

→ State table

A_t	B_t	γ	A_{t+1}	B_{t+1}	γ
$\begin{bmatrix} 0 & 0 \end{bmatrix}$	0	0	0	0	1
$\begin{bmatrix} 0 & 1 \end{bmatrix}$	1	1	0	1	0
$\begin{bmatrix} 0 & 1 \end{bmatrix}$	0	1	0	0	1
$\begin{bmatrix} 0 & 1 \end{bmatrix}$	1	1	1	1	0
$\begin{bmatrix} 1 & 0 \end{bmatrix}$	0	0	0	0	1
$\begin{bmatrix} 1 & 0 \end{bmatrix}$	1	1	1	0	0
$\begin{bmatrix} 1 & 1 \end{bmatrix}$	0	0	0	0	1
$\begin{bmatrix} 1 & 1 \end{bmatrix}$	1	1	1	0	1


State diagram:

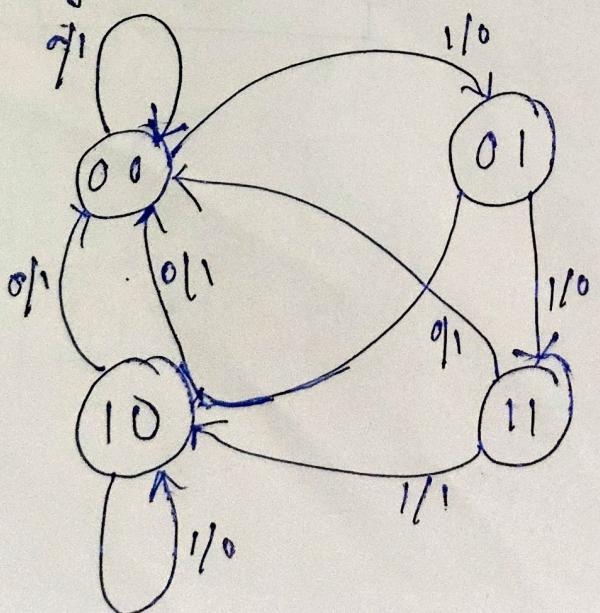

dt - 09-12-25

Ex - Analyze the given circuit

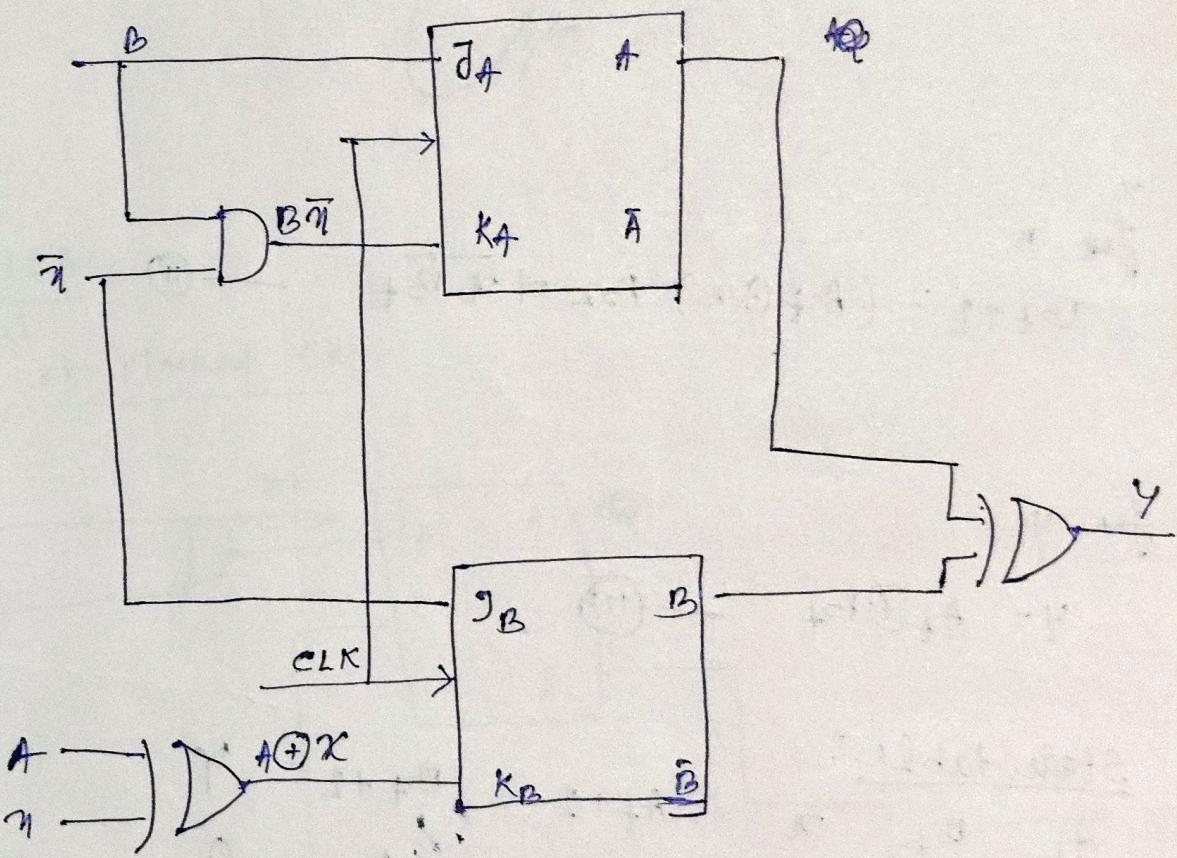- Write characteristic equation
- Write state table
- Draw state diagram.



$$A_t, B_t \rightarrow P.S$$

γ → input

y → output.

$$J_A = B_t, K_A = B_t \bar{A}$$

$$J_B = \bar{\gamma}, K_B = A_t \oplus \gamma$$

$$y = A_t \oplus B_t$$

characteristic equation:

$$Q_{t+1} = \bar{K}_A Q_t + J_A \bar{Q}_A$$

Characteristics equation:

$$\begin{aligned}
 A_{t+1} &= \overline{B_t \pi} \cdot A_t + B_t \bar{A}_t \\
 &= (\overline{B_t} + \alpha) A_t + B_t \bar{A}_t \\
 &= A_t \overline{B_t} + A_t \pi + \bar{A}_t B_t
 \end{aligned}$$

$$A_{t+1} = A_t \oplus \pi + A_t \alpha \quad \rightarrow \textcircled{1}$$

for B

$$B_{t+1} = (A_t \oplus \alpha) B_t + \pi \bar{B}_t \quad \rightarrow \textcircled{11}$$


for Y

$$Y = A_t \oplus B_t \quad \rightarrow \textcircled{111}$$

State table:


A_t	B_t	π	A_{t+1}	B_{t+1}	Y
$[0]$	$[0]$	0	0	1	0
$[0]$	$[0]$	1	0	0	0
$[0]$	$[1]$	0	1	1	1
$[0]$	$[1]$	1	1	0	1
$[1]$	$[0]$	0	1	1	1
$[1]$	$[0]$	1	1	0	1
$[1]$	$[1]$	0	0	0	0
$[1]$	$[1]$	1	1	1	0

State diagram:

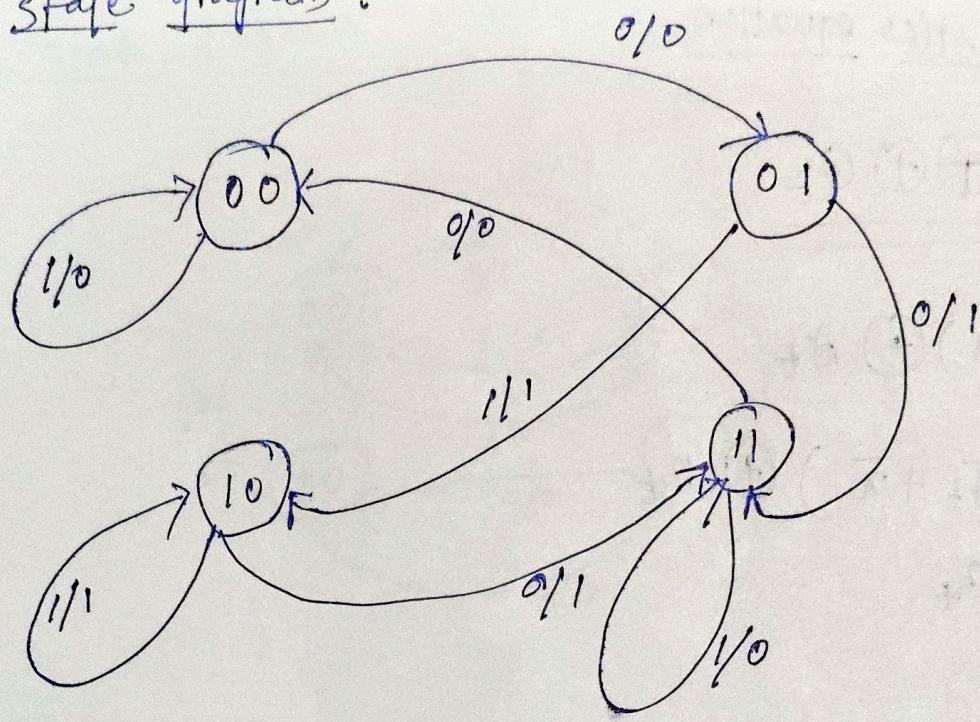

T-FLIP FLOP.

Sequential analysis of clocked ext.

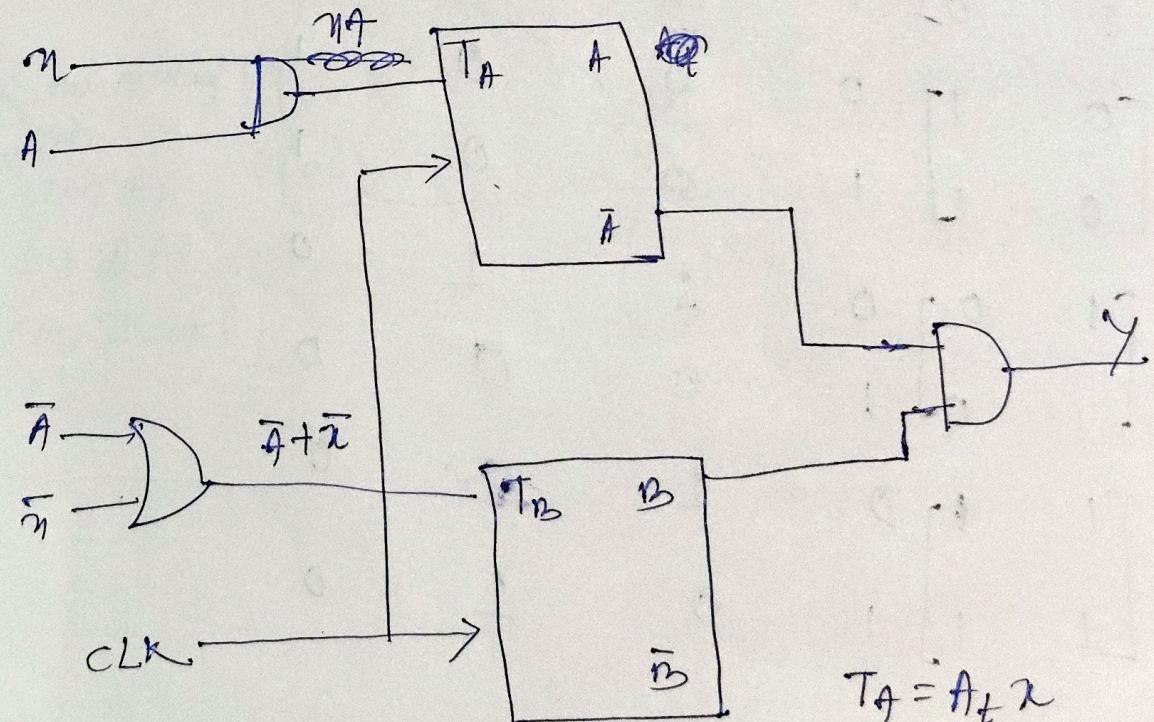

$$\begin{aligned} A_t, B_t &\rightarrow P_S \\ \bar{y} &\rightarrow \bar{Q}_t^P \\ y &\rightarrow Q_t^P \end{aligned}$$

$$\begin{aligned} T_A &= A_t \bar{x} \\ T_B &= \bar{A}_t + \bar{x} \\ y &= \bar{A}_t B_t \end{aligned}$$

characteristics equation

$$\underline{Q_{t+1} = \oplus \oplus Q_L}$$

$$A_{t+1} = (A_t \bar{x}) \oplus A_t$$


$$B_{t+1} = (A_t + \bar{x}) \oplus B_t$$

$$Y = \bar{A}_t B_t$$

state Table

A_t	B_t	\bar{x}	A_{t+1}	B_{t+1}	Y
$[0 \ 0]$	$[0 \ 0]$	0	0	1	0
$[0 \ 0]$	$[0 \ 1]$	1	0	1	0
$[0 \ 1]$	$[1 \ 0]$	0	0	0	1
$[0 \ 1]$	$[1 \ 1]$	1	0	0	1
$[1 \ 0]$	$[0 \ 0]$	0	1	1	0
$[1 \ 0]$	$[0 \ 1]$	1	0	0	0
$[1 \ 1]$	$[0 \ 0]$	0	1	0	0
$[1 \ 1]$	$[0 \ 1]$	1	0	1	0

state diagram

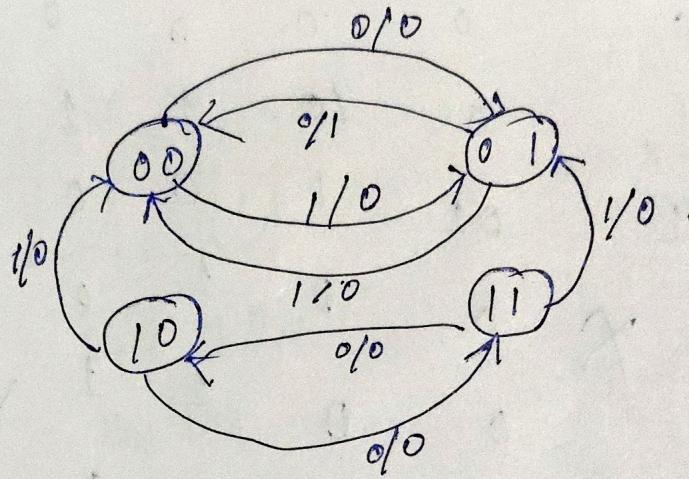


dt - 10-12-25

Design of clocked sequential circuit :
 (a') A sequential circuit has 1 g/f and 1 a/f.

the state diagram
is as shown in the
figure.

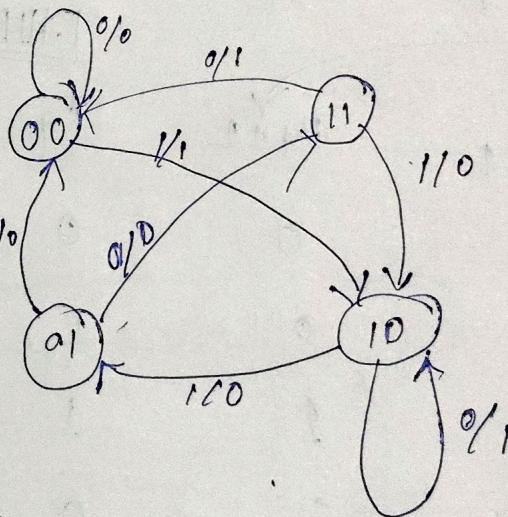- Design the sequential 1/o circuit with
 - (i) T FF
 - (ii) D FF
 - (iii) JK FF.



A_t	B_t	π	A_{t+1}, \dots	B_{t+1}, \dots	T_A	T_B	γ
0	0	0	0	0	0	0	0
0	0	1	1	0	1	0	1
0	1	0	1	1	1	0	0
0	1	1	0	0	0	1	0
1	0	0	1	0	0	0	1
1	0	1	0	1	1	1	0
1	1	0	0	0	1	1	1
1	1	1	1	0	0	2	0

T.EIPFDP

K map for T_A.

		Bt _n	00	01	11	10
		A _t	0	1	1	1
B _t	A _t	0	0	1	1	1
		1	1	1	1	1

$$\begin{aligned}T_A &= \bar{B} + \bar{A} + B\bar{t}^n \\&= B_t \oplus A\end{aligned}$$

K map for T_B.


		Bt _n	00	01	11	10
		A _t	0	0	1	1
B _t	A _t	0	0	0	1	1
		1	1	1	1	1

$$T_B = B\bar{t}^n + A\bar{t}^n + A_t B_t$$

K map for Y.

		Bt _n	00	01	11	10
		A _t	0	1	1	1
B _t	A _t	0	1	1	1	1
		1	1	1	1	1
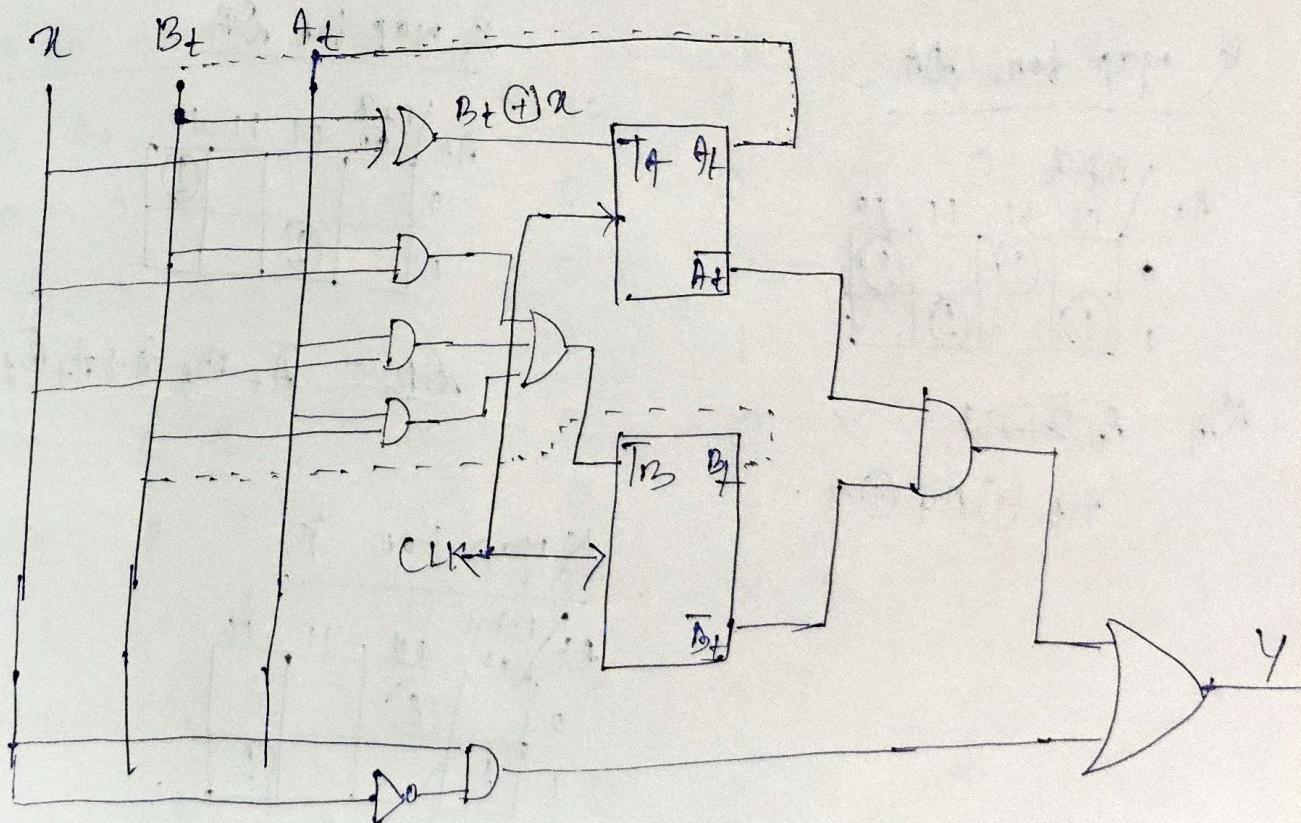
$$Y = A + \bar{t}^n + \bar{A} + B\bar{t}^n$$



D-F-F

A_t	B_t	χ	A_{t+1}	B_{t+1}	d_A	d_B	γ
0	0	0	0	0	0	0	0
0	0	1	1	0	1	0	1
0	1	0	1	1	1	1	0
0	1	1	0	0	0	0	0
1	0	0	1	0	1	0	1
1	0	1	0	1	0	1	0
1	1	0	0	0	0	0	1
1	1	1	1	0	1	0	0

K map for d_A .

A_t	$B_t \chi$	00	01	11	10
0	(1)	(1)			
1			(1)		

$$d_A = A_t \bar{B}_t \chi$$

$$A_t \oplus B_t \oplus \chi$$

K map for d_B .


A_t	$B_t \chi$	00	01	11	10
0					(1)
1		(1)			

$$d_B = \bar{A}_t B_t \bar{\chi} + A_t \bar{B}_t \chi$$

K map for γ .

A_t	$B_t \chi$	00	01	11	10
0			(1)		
1		(1)			(1)
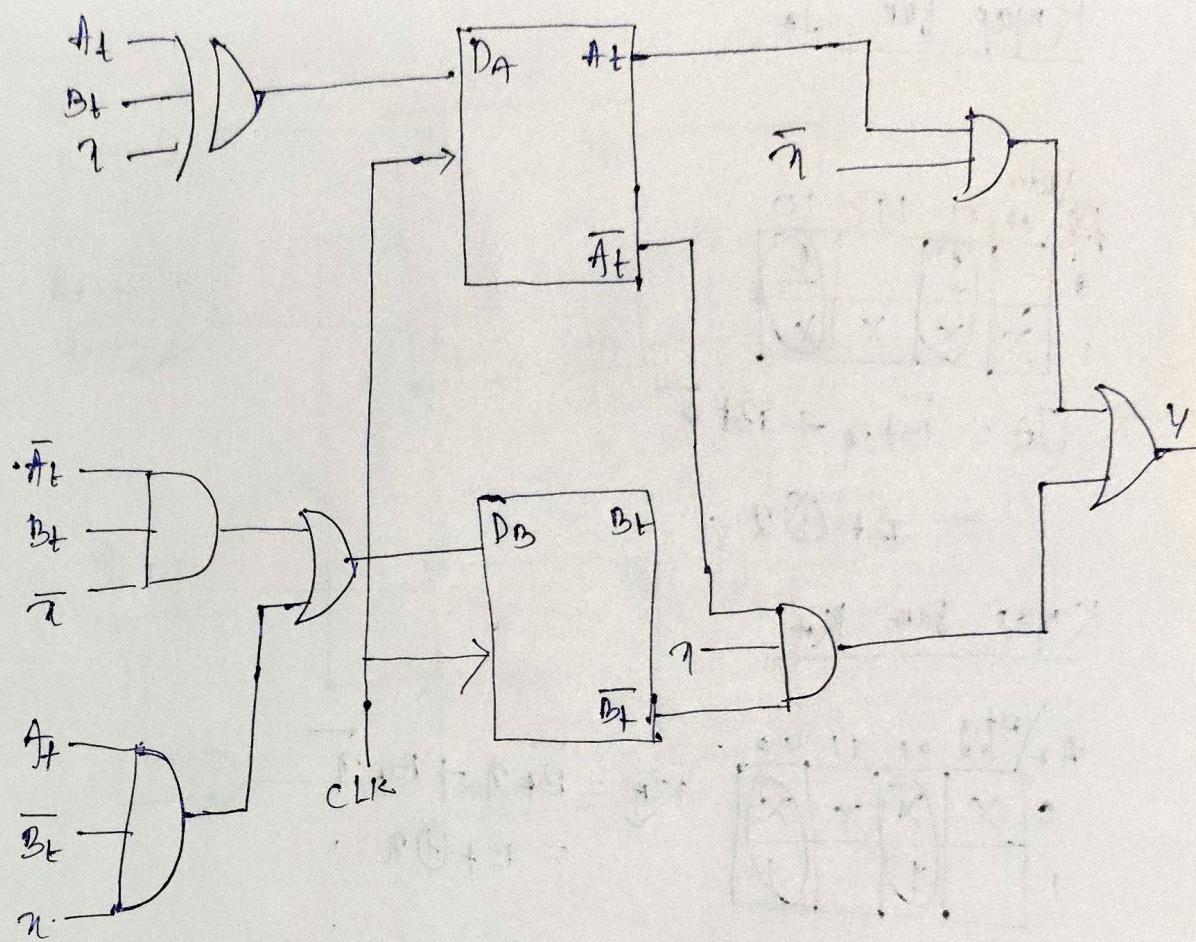
$$\gamma = A_t \bar{\chi} + \bar{A}_t \bar{B}_t \chi$$



dt - 12-12-25.

Design using JK FF:

A_t	B_t	γ	A_{t+1}	B_{t+1}	J_A	K_A	J_B	K_B	γ
0	0	0	0	0	0	x	0	$x \rightarrow 0$	
0	0	1	1	0	1	x	0	$x \rightarrow 1$	
0	1	0	1	1	1	x	x	$0 \rightarrow 0$	
0	1	1	0	0	0	x	x	$1 \rightarrow 1$	
1	0	0	1	0	x	0	0	$x \rightarrow 0$	
1	0	1	0	1	x	1	1	$x \rightarrow 1$	
1	1	0	0	0	x	1	x	$1 \rightarrow 0$	
1	1	1	1	0	x	0	x	$1 \rightarrow 1$	

K-map for J_A

$A_f \backslash B_t \bar{a}$	00	01	11	10
0	1	1		
1	x	x	x	x

$$J_A = \overline{B} + \overline{a} + Bt\bar{a}$$

$$= B + \overline{a}t$$

K-map for K_A

$A_f \backslash B_t \bar{a}$	00	01	11	10
0	x	x	x	x
1	1	1		

$$K_A = \overline{B} + \overline{a} + Bt\bar{a}$$

$$= B + \overline{a}t$$

K-map for J_B

$A_f \backslash B_t \bar{a}$	00	01	11	10
0			x	x
1		(L)	x	x

$$J_B = A_f \bar{a}$$

K-map for K_B


$A_f \backslash B_t \bar{a}$	00	01	11	10
0	x	x	1	
1	x	x	1	1

$$K_B = A_f + \bar{a}$$

K-map for Y

$A_f \backslash B_t \bar{a}$	00	01	11	10
0	1			
1	1	1	1	1
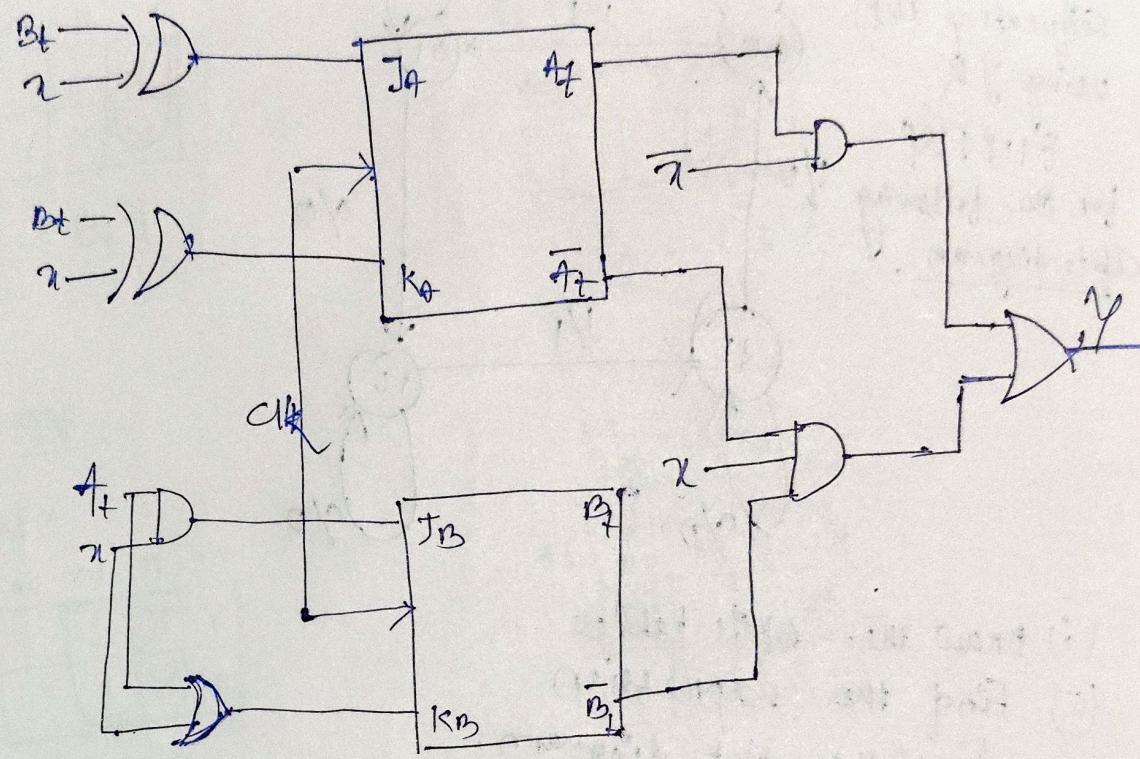
$$Y = A_f \bar{a} + \bar{A}_f B + \bar{a}$$




(Q).

Design the desired
sequential circuit
using JK

FIFO

for the following I/O
state diagram.

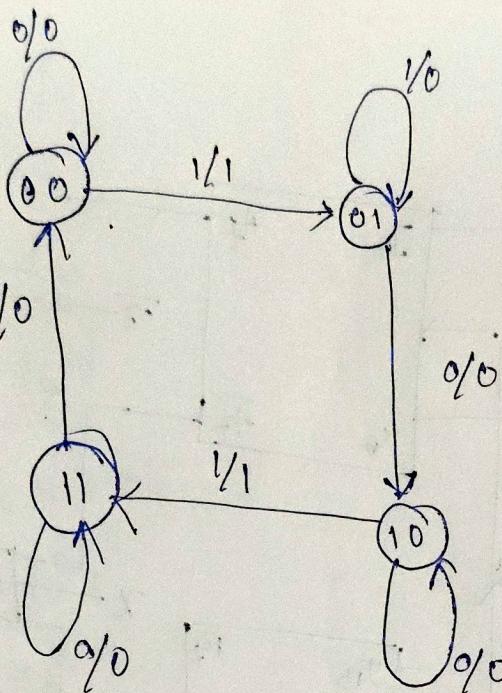

- (i) Draw the state table
- (ii) Find the expression
- (iii) Draw the ckt diagram.

State table

A_t	B_t	x	A_{t+1}	B_{t+1}	J_t	K_t	J_B	K_B	γ
0	0	0	0	0	0	X	0	X	0
0	0	1	0	1	0	X	1	X	01
0	1	0	10	00	1	X	X	1	0
0	1	1	0	1	0	X	X	0	0
1	0	0	1	0	X	0	0	X	0
1	0	1	1	1	X	0	1	X	1
1	1	0	1	1	X	0	X	0	0
1	1	1	0	0	X	1	X	1	0

Kmap for J_A

		B _t γ			
		00	01	11	10
A _t	0	X	X	X	(1)
	1	X	X	X	

$$J_A = B_t \bar{z}.$$

K_A Kmap

		B _t γ			
		00	01	11	10
A _t	0	X	X	(X)	X
	1			(1)	

$$K_A = B_t z.$$

J_B Kmap

		B _t γ			
		00	01	11	10
A _t	0	1	X	X	
	1	1	X	X	

$$J_B = z.$$

K_B Kmap


		B _t γ			
		00	01	11	10
A _t	0	X	X		(1)
	1	X	(X)	1	

$$\begin{aligned} K_B &= \bar{A}_t \bar{z} + A_t z. \\ &= A_t \odot z. \end{aligned}$$

Kmap for Y

		B _t γ			
		00	01	11	10
A _t	0	(1)	(1)		
	1	(1)			

$$Y = \odot \bar{B}_t z.$$

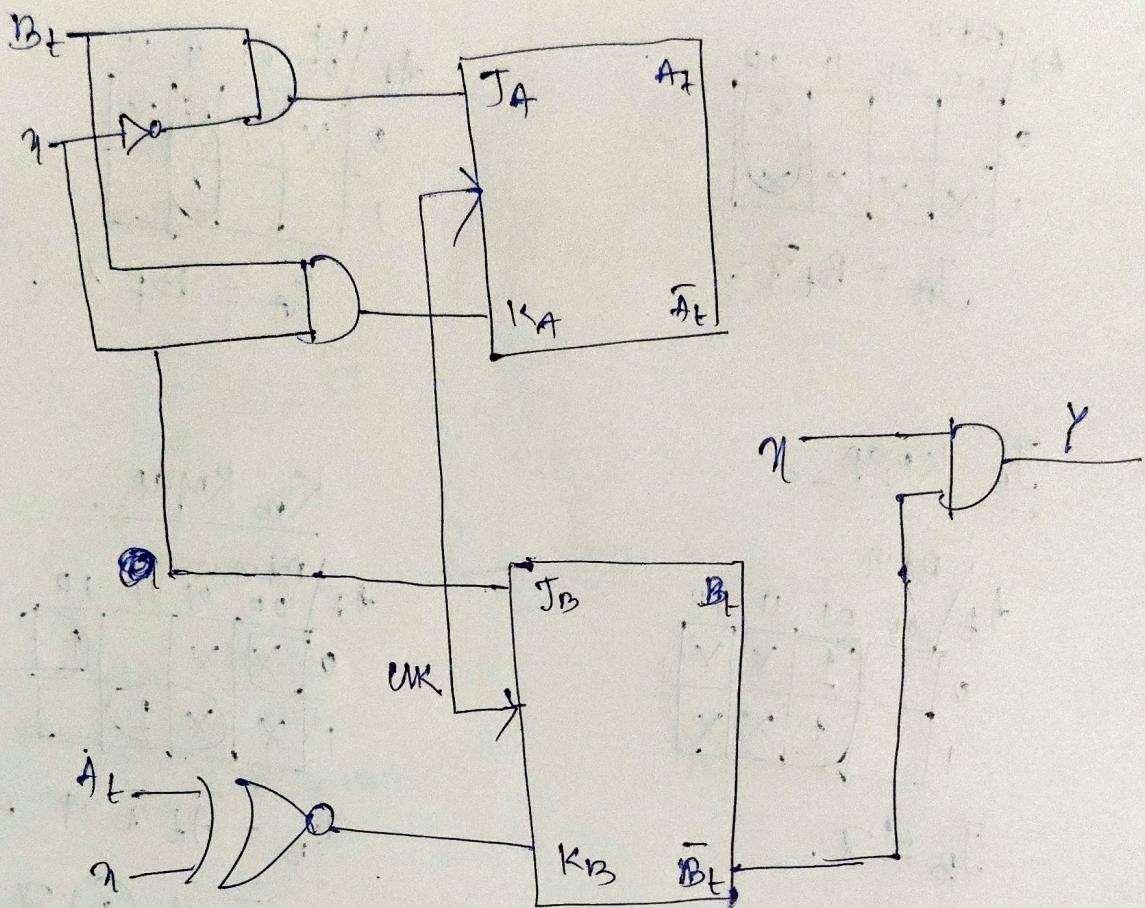

dt - 15-12-25 :-

Important

Analysis

- CKT given
- State equation
- State table
- State diagram

Design

- State diagram given
- State table
- Transition table
- K-map to find inputs to the ff
- Circuit diagram.


COUNTER :-

- It will count number of states.
- (Number of clock pulses).
- 'n' bit counter can count 2^n number of states
i.e. 0 to $2^n - 1$
- To design 'n' bit counter 'n' number of FFs are needed.
- Counters are two types.
 - * Asynchronous Counter
 - ** Synchronous Counter.


Asynchronous Counter :-

- When different clock pulses are given to different flip-flops then the counter is asynchronous counter.
- The output of 1st flip-flop is given as a clock pulse to second flip-flop and so on.
- An asynchronous counter can be designed by JK ff or T ff with $J=K=1$ or $T=1$.
- For n bit counter design we need 'n' number of ffs.
- Flip-flops are negative ~~edge~~ edge triggered i.e. it will change its state on the arrival of the -ve edge of the clock pulses.

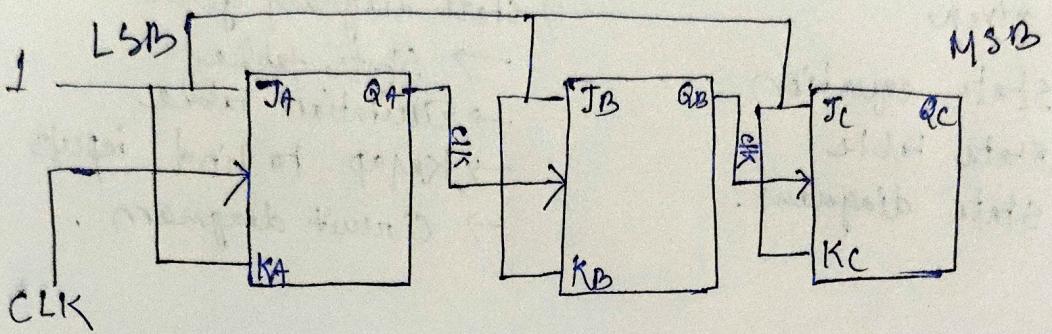Design a 3 bit asynchronous counter using JK FLIPFLOP.



<u>CLK</u>	Q _C	Q _B	Q _A
1	0	0	0
2	0	0	1
3	0	1	0
4	0	1	1
5	1	0	0
6	1	0	1
7	1	1	0
8	1	1	1

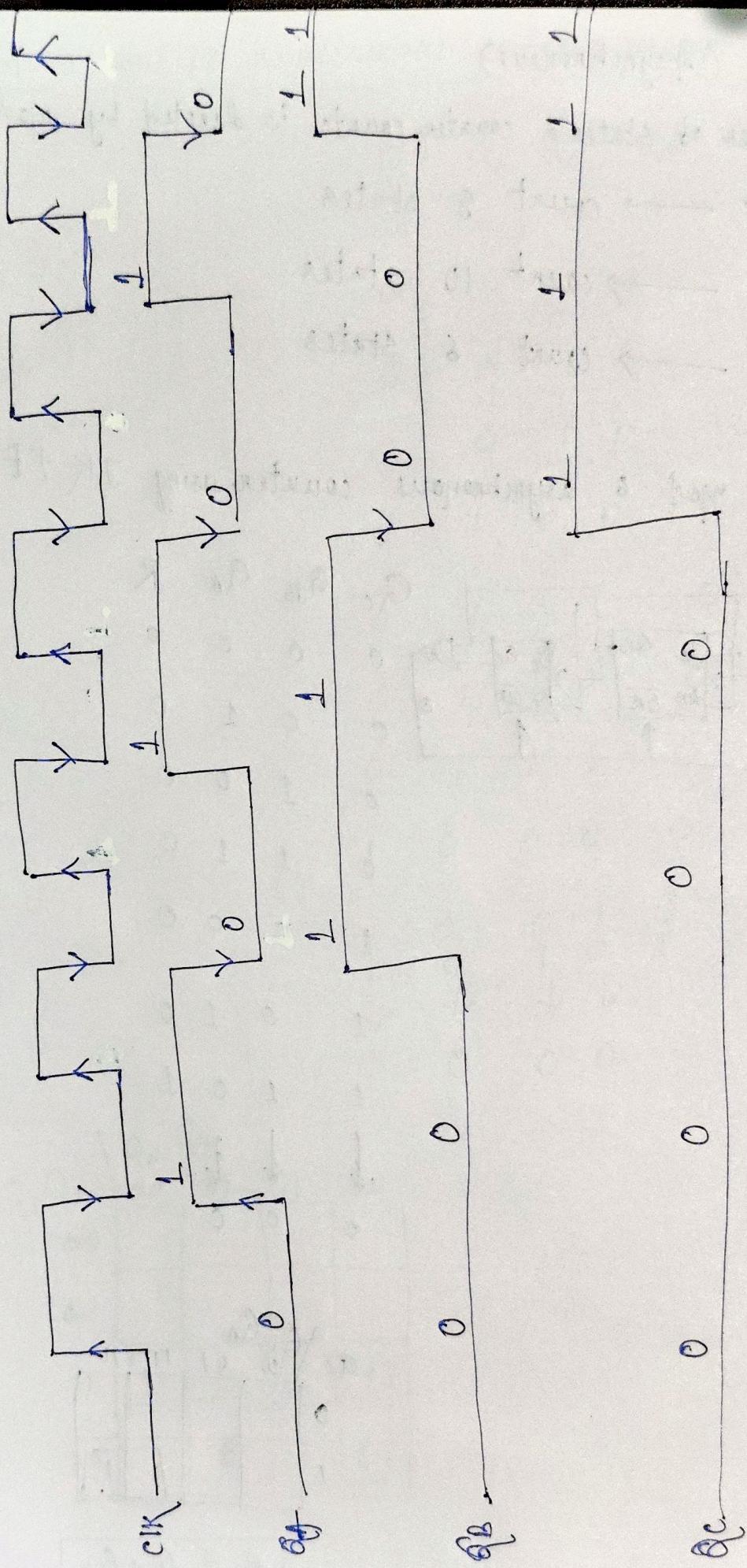

Timing diagram

Mod counter (Asynchronous)


→ The number of states a counter counts, is denoted by modulus (mod).

mod-8 → count 8 states

mod-10 → count 10 states

mod-6 → count 6 states

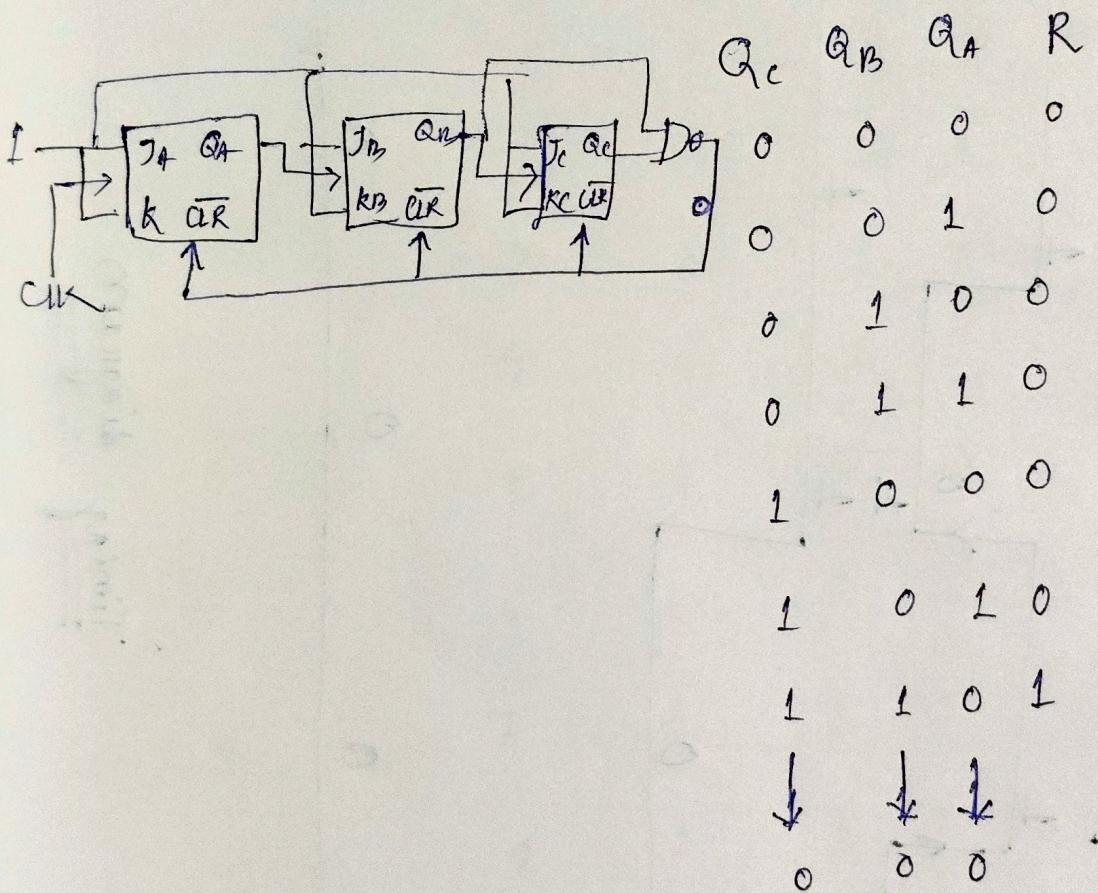→ Design a mod 6 asynchronous counter using JK FF



Q_c	Q_B	Q_A	0	1	11	10
0						
1					1	1


$$R = Q_c Q_B$$

Design a mod-10 asynchronous counter using JK FF.

Q_D	Q_C	Q_B	Q_A	R
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	1	0	0	1
0	0	0	0	0

$Q_D Q_C$	Q_B	Q_A	Q_0	Q_1	Q_2	Q_3
00						
01						
11	1	1	1	1		
10		1	1	1		

$$R = Q_C Q_D + Q_B Q_A$$

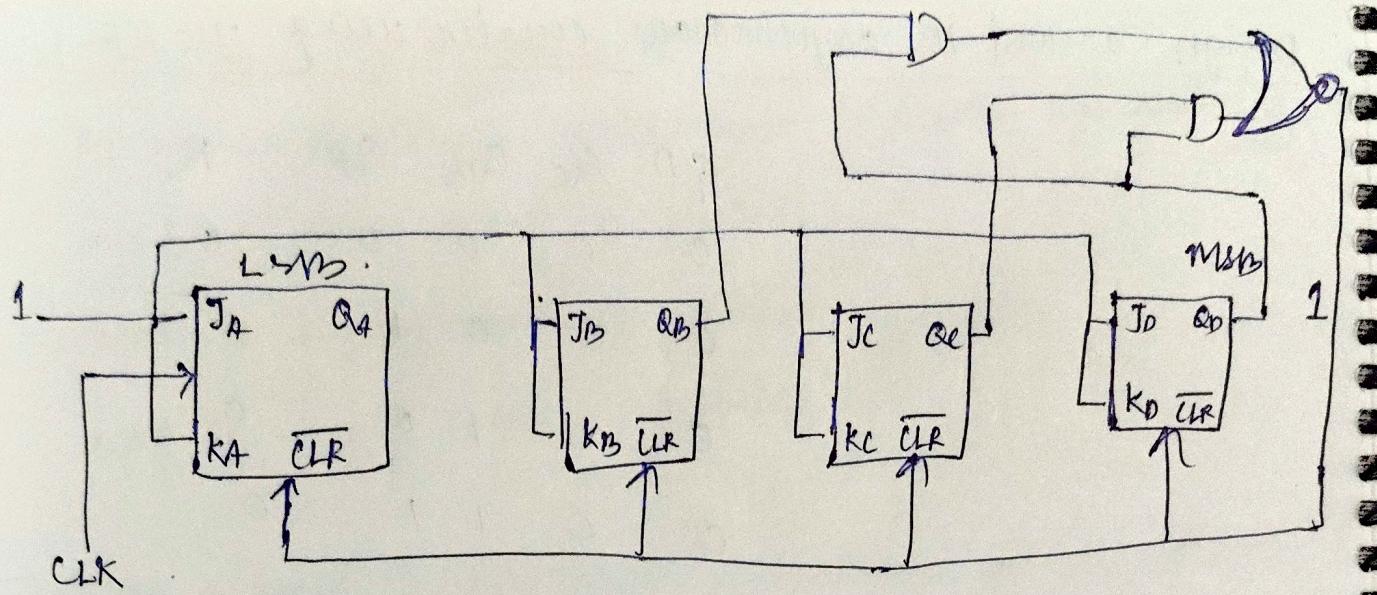


BCD
Decimal.

Synchronous Counter

- * The same clock pulse is given to all the flipflops.
 → JK, D, T
- PS and NS and system excitation table.
- state diagram.
- K map to find input to the ff.
- circuit diagram.

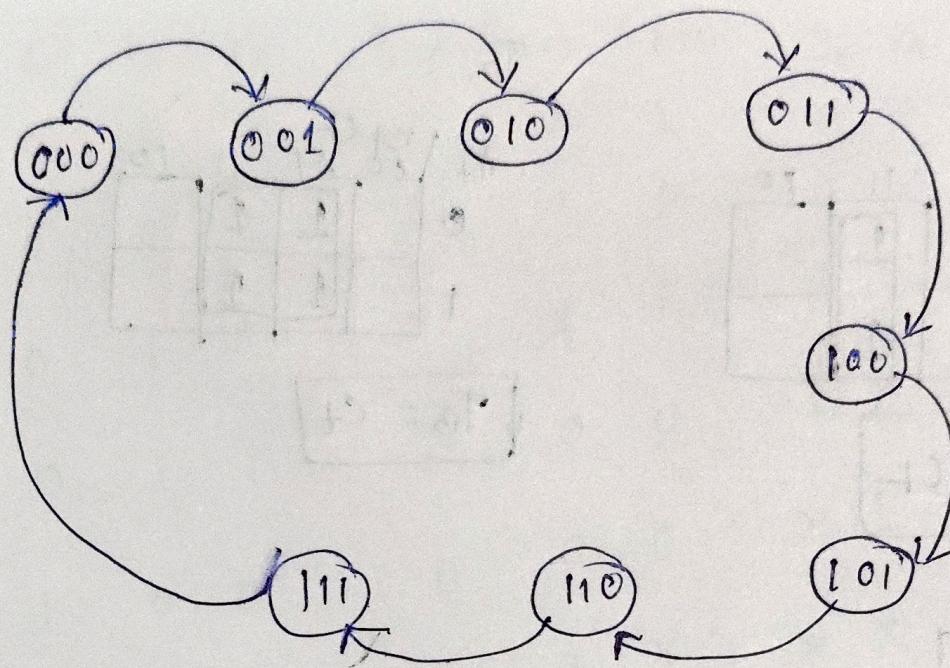→ Design a 3 bit synchronous counter using T flip-flops.



A_t	B_t	C_t	A_{t+1}	B_{t+1}	C_{t+1}	T_A	T_B	T_C
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

Kmap T_A =

A_t	B_t	C_t	00	01	11	10
0	0	0	0	0	1	1
1	1	1	1	1	0	0


$$T_A = B_t C_t$$

Kmap T_B =

A_t	B_t	C_t	00	01	11	10
0	0	0	0	0	1	1
1	1	1	1	1	0	0

$$T_B = C_t$$

$$T_C = 1$$

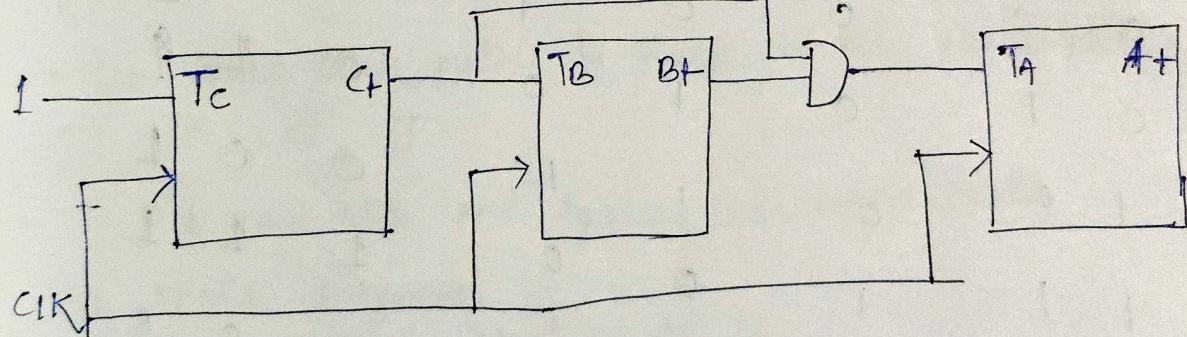

Design a Mod-5 Synchronous Counter using JK FF

A_t	B_t	C_t	A_{t+1}	B_{t+1}	C_{t+1}	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	0	1	0	x	0	x	1	x
0	0	1	0	1	0	0	x	1	x	x	1
0	1	0	0	1	1	0	x	x	0	1	x
0	1	1	1	0	0	1	x	x	1	x	1
1	0	0	0	0	0	x	1	0	x	0	x
1	0	1	x	x	x	x	x	xx	xx		
1	1	0	x	x	x	x	x	xx	xx		
1	1	1	x	x	x	x	x	xx	xx		

K map - J_A

A_t	$B_t C_t$			
	00 01 11 10			
0			1	
1	x	x	x	x

K_A

A_t	$B_t C_t$	00	01	11	10
0	x	x	x	x	
1	1	x	x	x	

$$K_A = \overline{A} \overline{B} \overline{C} + 1$$

$$J_A = B_t C_t$$

J_B

		Bt Ct			
		00	01	11	10
A _t	0	X	X	X	X
	1	X	X	X	X

$$J_B = Ct \cdot X$$

K_B

		Bt Ct			
		00	01	11	10
A _t	0	X	X	1	X
	1	X	X	X	X

$$K_B = Ct$$

J_C


		Bt Ct			
		00	01	11	10
A _t	0	1	X	X	1
	1	X	X	X	X

$$J_C = \overline{A_t}$$

K_C

		Bt Ct			
		00	01	11	10
A _t	0	X	1	1	X
	1	X	X	X	X


$$K_C = 1$$

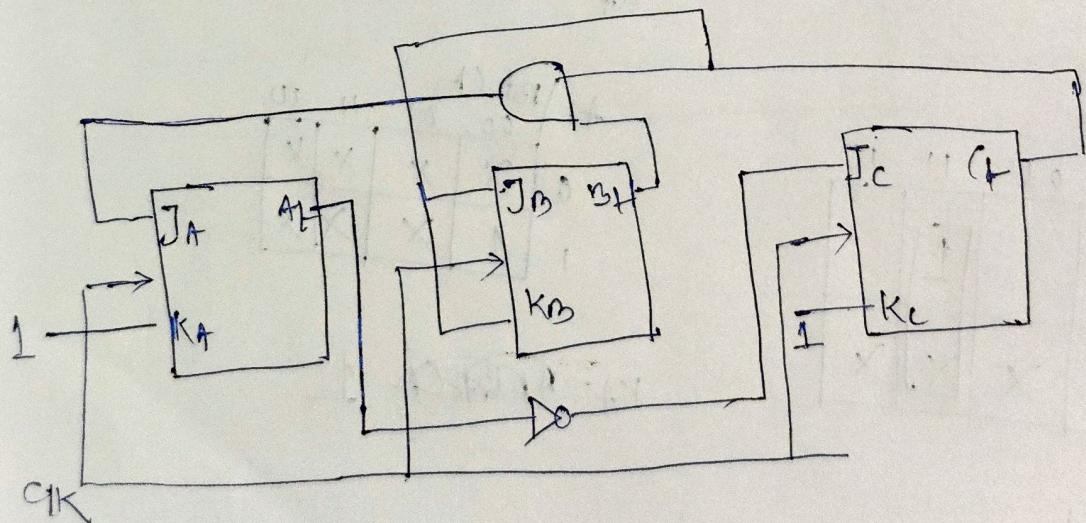

Skipping state

Design the counter having following state diagram.

using TFF

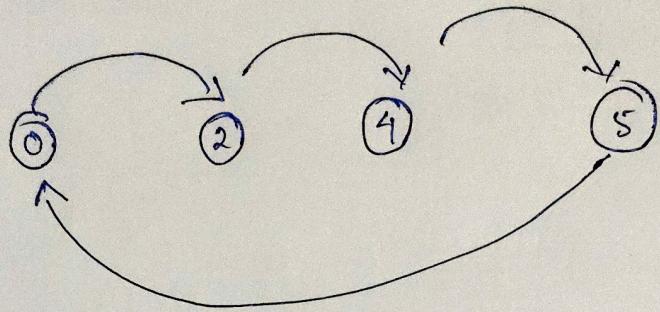

A_t	B_t	C_t	A_{t+1}	B_{t+1}	C_{t+1}	T_A	T_B	T_C
0	0	0	0	1	0	0	1	0
0	0	1	x	x	x	x	x	x
0	1	0	1	0	0	1	1	0
0	1	1	x	x	x	x	x	x
1	0	0	1	0	1	0	0	1
1	0	1	0	0	0	1	0	1
1	1	0	x	x	x	x	x	x
1	1	1	x	x	x	x	x	x

$$T_A = \begin{array}{c} A_t \\ \backslash \\ \begin{array}{c} B_t + C_t \\ \hline 00 & 01 & 11 & 10 \end{array} \end{array} = \begin{array}{c} C_t + B_t \\ \hline \end{array}$$


	x	x	1
0	1	x	x
1		x	x

$$T_B = \begin{array}{c} A_t \\ \backslash \\ \begin{array}{c} B_t + C_t \\ \hline 00 & 01 & 11 & 10 \end{array} \end{array} = \overline{A_t}$$


1	x	x	1
0	1		
1		x	x

$$T_C = \begin{array}{c} A_t \\ \backslash \\ \begin{array}{c} B_t + C_t \\ \hline 00 & 01 & 11 & 10 \end{array} \end{array} = A_t$$

	x	x	
0			
1	1	1	x

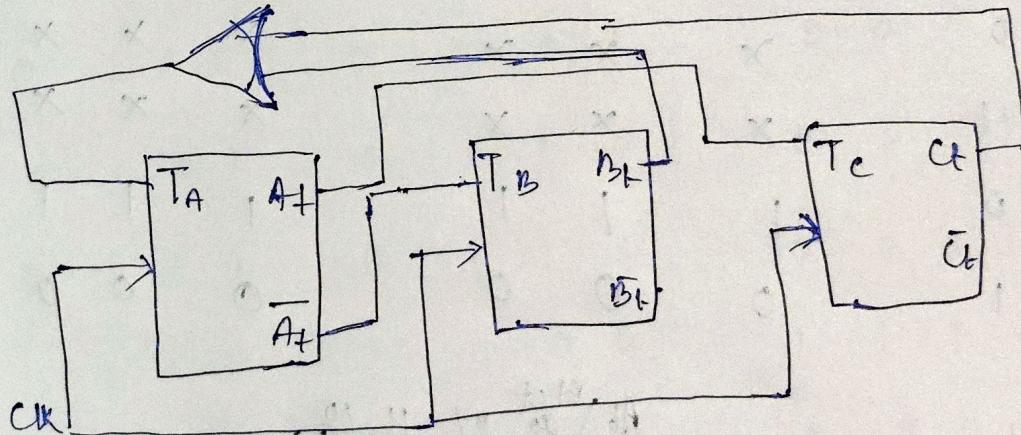

Using D. flip flop

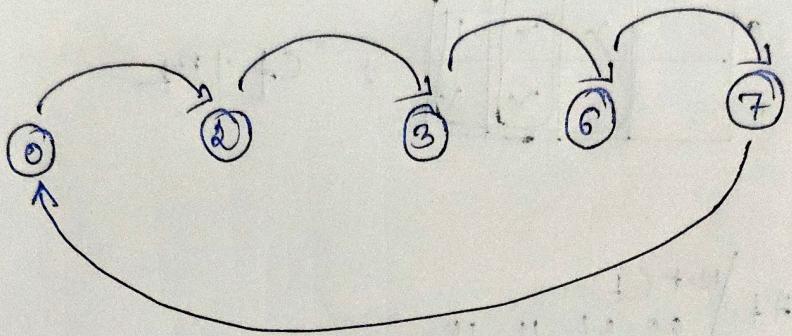

State table.

A_t	B_t	C_t	A_{t+1}	B_{t+1}	C_{t+1}	D_A	D_B	D_C
0	0	0	0	1	0	0	1	0
0	0	1	x	x	x	x	x	x
0	1	0	0	1	1	0	1	1
0	1	1	1	1	0	1	1	0
1	0	0	x	x	x	-x	x	x
1	0	1	-x	x	x	-x	x	x
1	1	0	-1	1	1	-1	1	1
1	1	1	0	0	0	0	0	0

$$D_A = A_t \begin{vmatrix} B_t C_t \\ 00 & 01 & 11 & 10 \end{vmatrix}$$

	0	1	1	
0	x	x		1
1	x	x		1

$$= A_t \oplus C_t$$

$$D_B = A_t \begin{vmatrix} B_t C_t \\ 00 & 01 & 11 & 10 \end{vmatrix}$$


	0	1	1	1
0	1	x	1	1
1	x	x	1	1

$$= \bar{A}_t + \bar{C}_t$$

$$D_C = A_t \begin{vmatrix} B_t C_t \\ 00 & 01 & 11 & 10 \end{vmatrix}$$

	0	1	x	
0	x	x		1
1	x	x		1

$$= B_t C_t$$

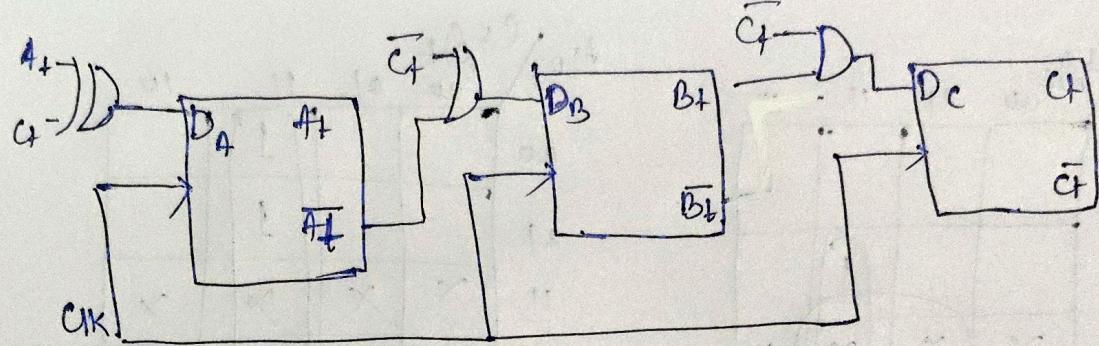

Q. Design a modulo Synchronous counter using T-FlipFlop.

$$A_t \ B_t \ C_t \ D_t \quad A_{t+1} \ B_{t+1} \ C_{t+1} \ D_{t+1} \quad T_A \ T_B \ T_C \ T_D$$

0	0	0	0	0	0	0	1	0	0	0	1
---	---	---	---	---	---	---	---	---	---	---	---

0	0	0	1	0	0	1	0	0	0	1	1
---	---	---	---	---	---	---	---	---	---	---	---

0	0	1	0	0	0	1	1	0	0	0	1
---	---	---	---	---	---	---	---	---	---	---	---

0	0	1	1	0	1	0	0	0	1	1	1
---	---	---	---	---	---	---	---	---	---	---	---

0	1	0	0	0	1	0	1	0	0	0	1
---	---	---	---	---	---	---	---	---	---	---	---

0	1	0	1	0	1	1	0	0	0	1	1
---	---	---	---	---	---	---	---	---	---	---	---

0	1	1	0	1	0	0	0	1	1	1	1
---	---	---	---	---	---	---	---	---	---	---	---

0	1	1	1	1	0	0	0	0	0	0	1
---	---	---	---	---	---	---	---	---	---	---	---

1	0	0	0	1	0	0	1	0	0	0	1
---	---	---	---	---	---	---	---	---	---	---	---

1	0	0	1	0	0	0	0	1	0	0	1
---	---	---	---	---	---	---	---	---	---	---	---

1	0	1	0	x	x	x	x	x	x	x	x
---	---	---	---	---	---	---	---	---	---	---	---

1	0	1	1	x	x	x	x	x	x	x	x
---	---	---	---	---	---	---	---	---	---	---	---

1	1	0	0	x	x	x	x	x	x	x	x
---	---	---	---	---	---	---	---	---	---	---	---

1	1	0	1	x	x	x	x	x	x	x	x
---	---	---	---	---	---	---	---	---	---	---	---

1	1	1	0	x	x	x	x	x	x	x	x
---	---	---	---	---	---	---	---	---	---	---	---

1	1	1	1	x	x	x	x	x	x	x	x
---	---	---	---	---	---	---	---	---	---	---	---

K-map

	$A + B\bar{F}$	$C + D\bar{F}$	a_1'	$11'$	$10'$
a_0					
a_1			1		
11	x	x	(x)	x	
10	x	1	x	x	

$$T_A = A + B\bar{F} + C + D\bar{F}$$


	$A + B\bar{F}$	$C + D\bar{F}$	a_0'	a_1'	$11'$	$10'$
a_0					1	
a_1					1	
11	x	x	x	x	x	x
10					x	x

$$T_B = C + D\bar{F}$$

	$A + B\bar{F}$	$C + D\bar{F}$	a_0'	a_1'	$11'$	$10'$
a_0					1	1
a_1					1	1
11	x	x	x	x	x	x
10						

$$T_C = \overline{A}_1 \overline{D}_1$$

$$T_D = 1$$

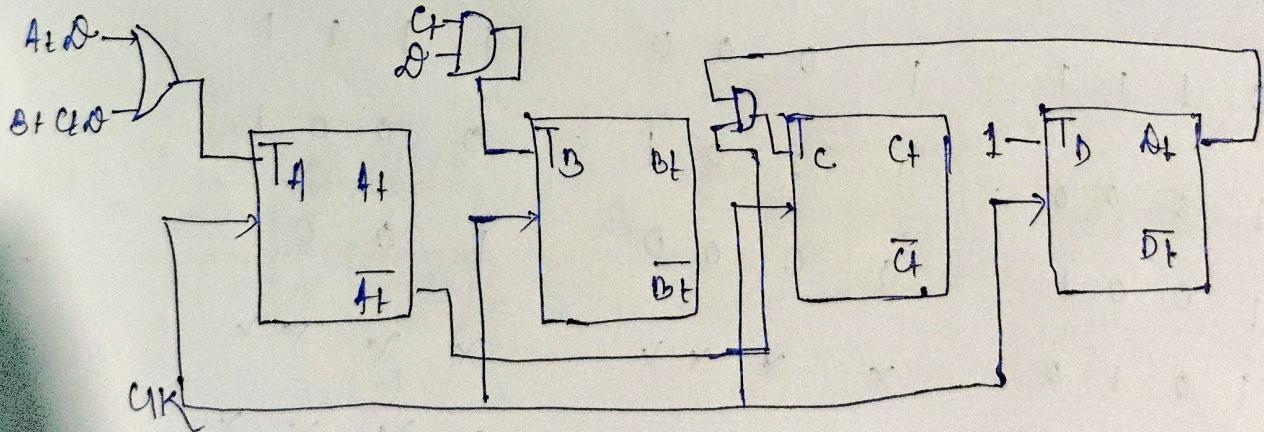

dt- 22-12-25

Design an up down 3 bit synchronous counter using T flip-flops.

Y	t_t	B_t	C_t	t_{t+1}	B_{t+1}	C_{t+1}	T_A	T_B	T_C
up	0	0	0	0	0	1	0	0	1
	0	0	0	1	0	1	0	0	1
	0	0	1	0	0	1	0	0	1
	0	0	1	1	1	0	0	1	1
	0	1	0	0	1	0	1	0	1
	0	1	0	1	1	0	0	1	1
	0	1	0	1	1	1	0	0	1
	0	1	1	0	1	1	1	1	1
	0	1	1	1	0	0	1	1	1
	1	0	0	0	1	1	1	1	1
down	1	0	0	1	0	0	0	0	1
	1	0	1	0	0	0	0	0	1
	1	0	1	0	0	0	1	0	1
	1	0	1	1	0	1	0	0	1
	1	1	0	0	0	1	1	1	1
	1	1	0	1	1	0	0	0	1
	1	1	1	0	1	0	1	0	1
	1	1	1	1	1	1	0	0	1
	1	1	1	1	1	0	0	0	1
	1	1	1	1	1	0	0	0	1

$$T_C = 1$$

$$T_A =$$

M_{AT}	$B+C_f$	00	01	11	10
00			1		
01				1	
11	1				
10	1				

$$= M\overline{B}fC_f + \overline{M}BfC_f$$

$$T_B =$$

M_{BT}	$B+C_f$	00	01	11	10
00		1	1		
01		1	1		
11	1				1
10	1				1

$$\overline{M}C_f + M\overline{C_f}$$


$$= M \oplus C_f$$

$$M\overline{B}fC_f$$


$$\overline{M}BfC_f$$

$$M \rightarrow C_f$$

$$1 \rightarrow T_C$$

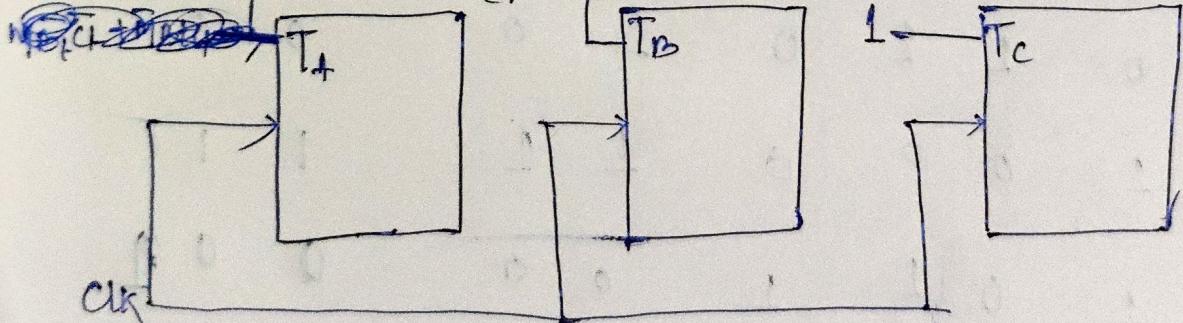

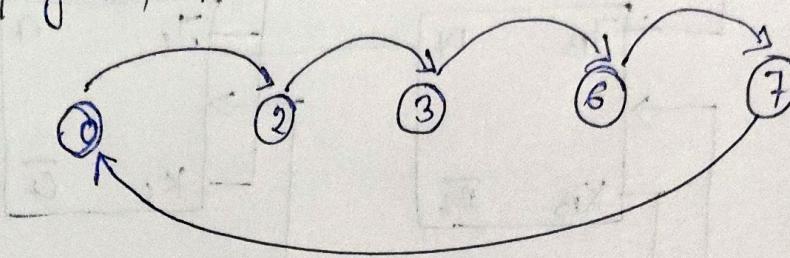Design a Synchronous counter using JK FF for the following state diagrams.



A_t	B_t	C_t	A_{t+1}	B_{t+1}	C_{t+1}	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	1	0	0	X	1	X	0	X
0	0	1	X	X	X	X	X	X	X	X	X
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	1	0	1	X	X	0	X	1
1	0	0	X	X	X	X	X	X	X	XX	
1	0	1	X	X	X	X	X	X	0	X	
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	0	0	X	1	X	0	X	1

$$J_B = 1, \quad K_C = 1.$$

$$J_A = A_t \begin{array}{c} B_t C_t \\ \hline \text{---} & \text{---} \\ 00 & 01 & 11 & 10 \\ \hline 0 & X & | & 1 \\ 1 & X & X & X \end{array}$$

$$= C_t$$

$$K_A = A_t \begin{array}{c} B_t C_t \\ \hline \text{---} & \text{---} \\ 00 & 01 & 11 & 10 \\ \hline 0 & X & | & X \\ 1 & X & X & 1 \end{array}$$


$$= C_t$$

$$J_B = A_t \begin{array}{c} B_t C_t \\ \hline \text{---} & \text{---} \\ 00 & 01 & 11 & 10 \\ \hline X & X & | & \\ 1 & X & X & 1 \end{array}$$

$$= A_t \bar{C}_t$$

$$J_C = A_t \begin{array}{c} B_t C_t \\ \hline \text{---} & \text{---} \\ 00 & 01 & 11 & 10 \\ \hline | & X & | & 1 \\ 1 & X & X & X \end{array}$$

$$= B_t$$

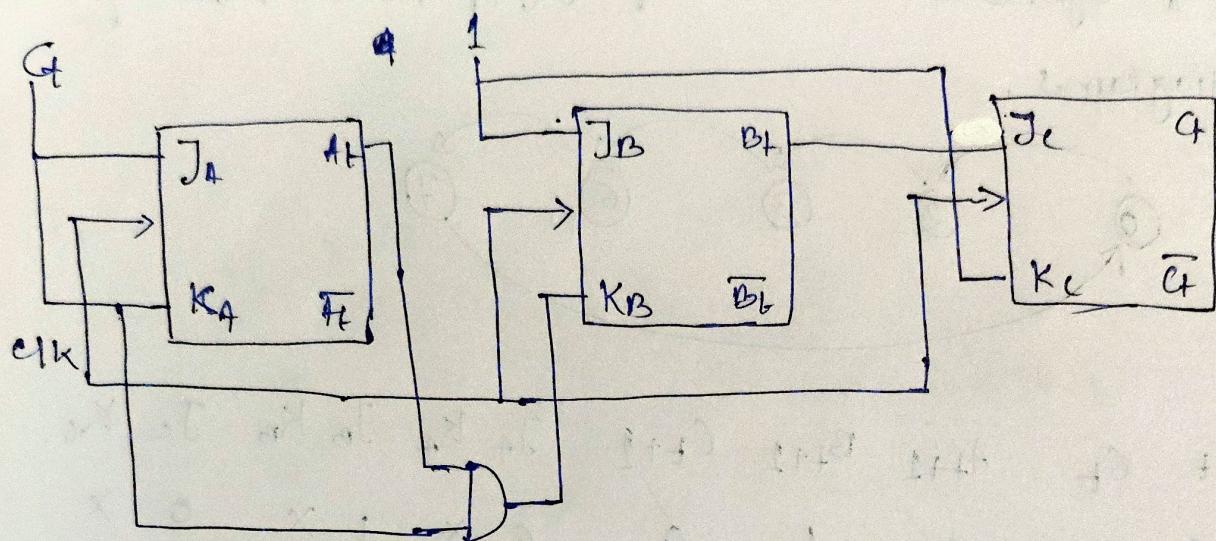

dt - 23 - 12 - 25

design combinational ckt w/ 4 bits and 4 outputs. Input represents decimal digit in BCD and output is the q's complement of the input.

BCD \rightarrow Binary Coded Decimal

\rightarrow Here each decimal digit will be represented by its 4 bit binary numbers.

$$\text{g. } 26 \rightarrow 00100110$$

design a combinational ckt which converts binary code to Gray code.

Binary code

Gray code

B_3	B_2	B_1	B_0	G_3	G_2	G_1	G_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0